

Chapter 3 - Resistive Circuits

Lecture 6 Section 3.3

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 3 -
Resistive Circuits

MEMS 0031

Learning Objectives

3.3 Series Resistors


Summary

At the end of the lecture, students should be able to:

- ▶ Understand how resistors in series divide voltage
- ▶ Formulate an expression for the voltage across a resistor in series with other resistors



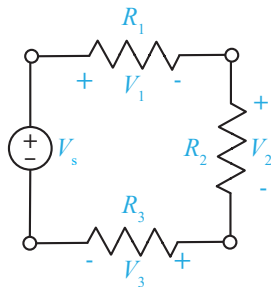- Considering the following circuit. What is the voltage drop across each resistor?




Learning Objectives

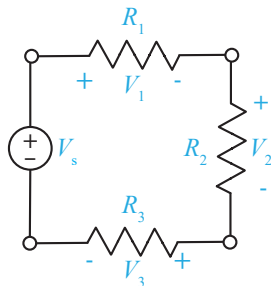3.3 Series Resistors

Summary



- Can we formulate a general expression for the voltage drop across a resistor that exists in series?



Learning Objectives


3.3 Series Resistors

Summary



Equivalent Resistance

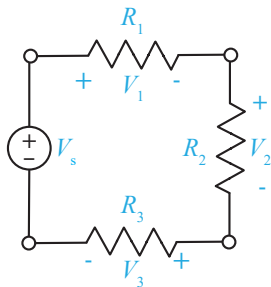- Replace the resistors in series as one resistor.



Learning Objectives


3.3 Series Resistors

Summary




Equivalent Resistance

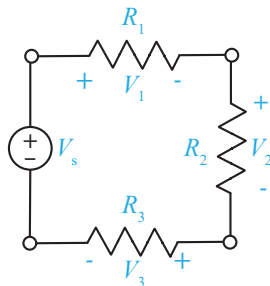- Does the equivalent resistor satisfy the conservation of electrical power and Ohm's law?



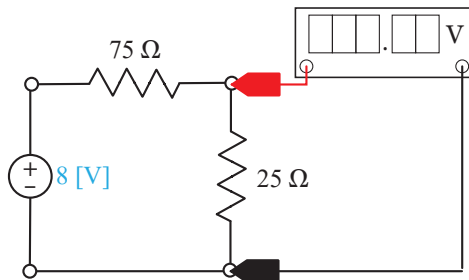
Example #1

- Determine the voltage measured by the voltmeter:



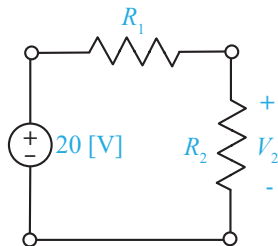Example #2

- Design a voltage divider such that $V_2=0.8V_s$ and no more than 1 [mW] of power is supplied by the source, given $V_s=20$ [V].



Learning Objectives


3.3 Series Resistors

Summary



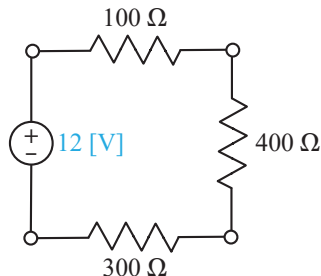Example #3

- Find the voltage drop across each resistor:



Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Understand how resistors in series divide voltage
 - ▶ Resistors in series carry the same current.
However, there exists a potential to drive the current through all the resistors. Thus, the voltage drop across a resistor in series with other resistors is a proportion of the total potential.
- ▶ Formulate an expression for the voltage across a resistor in series with other resistors

$$V_j = \left(\frac{R_j}{\sum_{i=1}^N R_i} \right) V_s$$



Suggested Problems

Chapter 3 -
Resistive Circuits

MEMS 0031

► 3.3-1, 3.3-2, 3.3-3, 3.3-5, 3.3-6, 3.3-7

Learning Objectives

3.3 Series Resistors

Summary

