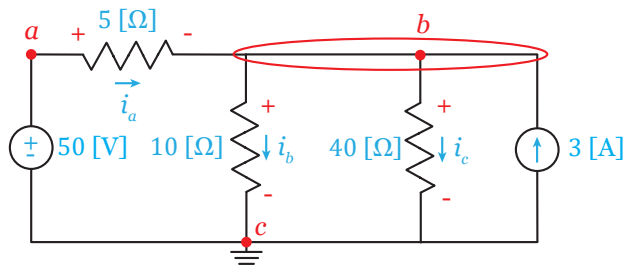


MEMS 0031 - Electrical Circuits
Quiz #4

Name: Solutions

Problem #1

Determine the branch currents i_a , i_b and i_c using NVA.



Step 1:

Identify number of nodes (3, shown in red), number of voltage sources (1) and number of KCL equations (1, which will be applied at node b)

Step 2:

Apply passive sign convention to sinks (shown in red)

Step 3:

Apply KCL equation to most logical node (b , for c is ground, $V_c=0$, and a is known, $V_a=50$ [V])

$$i_a + 3 = i_b + i_c$$

Step 4:

Apply Ohm's Law to KCL equation in terms of node voltages

$$\frac{V_a - V_b}{5 [\Omega]} + 3 [\text{A}] = \frac{V_b - V_c}{10 [\Omega]} + \frac{V_b - V_c}{40 [\Omega]} \implies V_b = 40 [\text{V}]$$

Therefore,

$$i_a = 2 [\text{A}]; \quad i_b = 4 [\text{A}]; \quad i_c = 1 [\text{A}]$$