


# NVA Worksheet

MEMS 0031 - Electrical Circuits

June 4, 2020
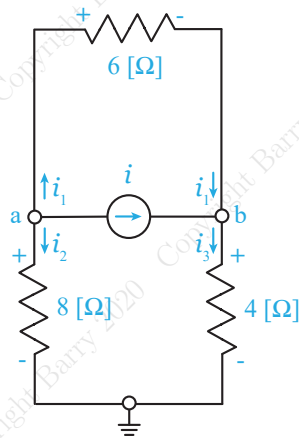
## Problem #1

Use NVA to solve for the nodal voltage given a source current of 1 [A].



Step 1: Assign nodes ( $N$ ) and leg currents to all branches/elements:  
 $N = 3$  and we define  $i_1$ ,  $i_2$  and  $i_3$  as shown.

Step 2: Assign voltage potential consistent with PSC:  
 Voltage potentials assigned as shown.

Step 3:  $N - 1$  KCL equations, applied at non-zero nodes:  
 Applying KCL at node a:

$$i_1 + i_2 = -1 \text{ [A]}$$

Applying KCL at node b:

$$1 \text{ [A]} + i_1 = i_3 \implies i_3 - i_1 = 1 \text{ [A]}$$

Step 4: Apply Ohm's law in terms of node voltages:

KCL at node a:

$$\frac{V_a - V_b}{6 \text{ [}\Omega\text{]}} + \frac{V_a}{8 \text{ [}\Omega\text{]}} = -1 \text{ [A]} \implies V_a \left( \frac{7}{24} \right) - V_b \left( \frac{1}{6} \right) = -1$$

KCL at node b:


$$\frac{V_b}{4 \text{ [}\Omega\text{]}} - \frac{V_a - V_b}{6 \text{ [}\Omega\text{]}} = 1 \text{ [A]} \implies -V_a \left( \frac{1}{6} \right) + V_b \left( \frac{5}{12} \right) = 1$$

In matrix form:

$$\begin{bmatrix} 7/24 & -1/6 \\ -1/6 & 5/12 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} -1 \\ 1 \end{bmatrix} \implies \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} -2.6667 \\ 1.3333 \end{bmatrix}$$
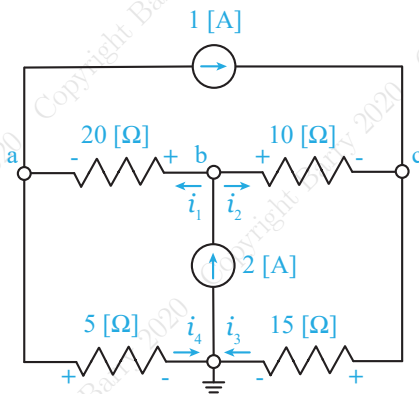
## Problem #2

Use NVA to solve for  $v_1$ ,  $v_2$  and  $v_3$  in the circuit shown below.



Step 1: Assign nodes ( $N$ ) and leg currents to all branches/elements:

$N = 4$  and we define  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  as shown.

Step 2: Assign voltage potential consistent with PSC:  
Voltage potentials assigned as shown.

Step 3:  $N - 1$  KCL equations, applied at non-zero nodes:  
KCL at node a:

$$i_1 = i_4 + 1 \text{ [A]} \implies i_1 - i_4 = 1 \text{ [A]}$$

KCL at node b:

$$i_1 + i_2 = 2 \text{ [A]}$$

KCL at node c:

$$1 \text{ [A]} + i_2 = i_3 \implies i_2 - i_3 = -1 \text{ [A]}$$

Step 4: Apply Ohm's law in terms of node voltages:

KCL at node a:

$$\frac{V_b - V_a}{20 \text{ } [\Omega]} - \frac{V_a}{5 \text{ } [\Omega]} = 1 \text{ [A]}$$

KCL at node b:

$$\frac{V_b - V_a}{20 \text{ } [\Omega]} + \frac{V_b - V_c}{10 \text{ } [\Omega]} = 2 \text{ [A]}$$

KCL at node c:


$$\frac{V_b - V_c}{10 \text{ } [\Omega]} - \frac{V_c}{15 \text{ } [\Omega]} = -1 \text{ [A]}$$

In matrix form:

$$\begin{bmatrix} -1/4 & 1/20 & 0 \\ -1/20 & 3/20 & -1/10 \\ 0 & 1/10 & -1/6 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \\ -1 \end{bmatrix} \implies \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 2 \\ 30 \\ 24 \end{bmatrix}$$
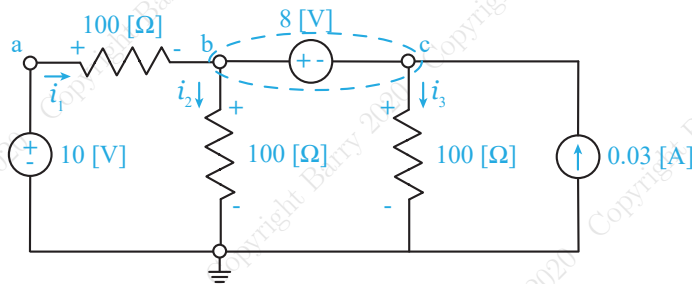
### Problem #3

Use NVA to find the node voltages in the circuit shown below.



Step 1: Assign nodes ( $N$ ) and leg currents to all branches/elements:

$N = 4$  and we define  $i_1$ ,  $i_2$  and  $i_3$  as shown.

Step 2: Assign voltage potential consistent with PSC:

Voltage potentials assigned as shown.

Step 3:  $N - 1 - \#VS$  KCL equations, applied at non-zero nodes:

We only need one KCL equation, which is applied at the supernode:

$$i_1 + 0.03 \text{ [A]} = i_2 + i_3$$

Step 4: Apply Ohm's law in terms of node voltages:

KCL at supernode:

$$\frac{V_a - V_b}{100 \text{ } [\Omega]} + 0.03 \text{ [A]} = \frac{V_b}{100 \text{ } [\Omega]} + \frac{V_c}{100 \text{ } [\Omega]}$$

The voltage at node a is specified as 10 [V]. Thus, the KCL equation at the supernode becomes:

$$0.1 - \frac{V_b}{100} + 0.03 = \frac{V_b}{100} + \frac{V_c}{100}$$

The supernode provides us with one additional equation:


$$V_b - V_c = 8 \text{ [V]}$$

In matrix form:

$$\begin{bmatrix} 2/100 & 1/100 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 0.13 \\ 8 \end{bmatrix} \Rightarrow \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 7 \\ -1 \end{bmatrix}$$
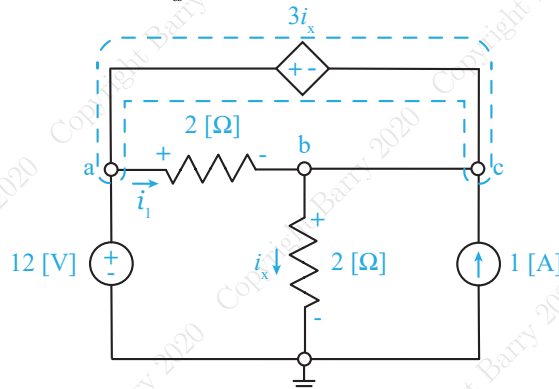
## Problem #4

Use NVA to find  $i_x$  in the circuit shown below.



Step 1: Assign nodes ( $N$ ) and leg currents to all branches/elements:

$N = 3$  and we define  $i_1$  as shown.

Step 2: Assign voltage potential consistent with PSC:

Voltage potentials assigned as shown.

Step 3:  $N - 1 - \#VS$  KCL equations, applied at non-zero nodes:

We see we do not need any KCL equations. The voltage sources provide enough equations.

The supernode provides the following equation:

$$V_a - V_b = 3i_x \implies V_a - V_b = 3\left(\frac{V_b}{2[\Omega]}\right)$$

The voltage at node a is specified as 12 [V]. Thus, the supernode equation can be solved for in terms of  $V_b$ :

$$V_b\left(\frac{3}{2} + 1\right) = 12 \implies V_b = 4.8 [\text{V}]$$

The leg current  $i_x$  can be found via Ohm's law:

$$i_x = \frac{4.8 [\text{V}]}{2 [\Omega]} = 2.4 [\text{A}]$$