

# Chapter 8 - The Complete Response of RL and RC Circuits

## Lecture 26 Sections 8.2-8.3

### MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department  
University of Pittsburgh



# Student Learning Objectives

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Construct and apply the constitutive equations of RC and RL circuits to determine the natural and forced response of a circuit


Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary



- Consider the following RC Circuit:

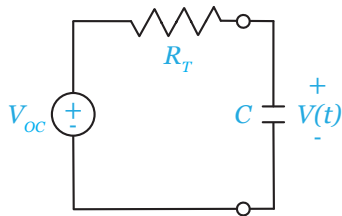

Recall the current through  
a capacitor:

$$i(t) = C \frac{dV(t)}{dt}$$

Applying KVL around the  
loop:

$$V_{oc} = i(t)R_T + V(t) = C \frac{dV(t)}{dt} R_T + V(t)$$

or

$$\frac{dV(t)}{dt} + \frac{V(t)}{R_T C} = \frac{V_{oc}}{R_T C}$$


Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary



► Now consider the following RL Circuit:

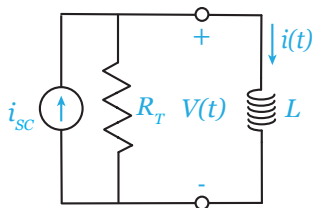

Recall the voltage through  
an inductor:

$$V(t) = L \frac{di(t)}{dt}$$

Applying KCL at the top  
node:

$$i_{sc} = \frac{V(t)}{R_T} + i(t) = \frac{L}{R_T} \frac{di(t)}{dt} + i(t)$$

or

$$\frac{di(t)}{dt} + \frac{R_T}{L} i(t) = \frac{R_T}{L} i_{sc}$$

Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary



# Response of RC and RL Circuits

- ▶ The solution to these following equations is found as follows:
- ▶ Note the RC and RL circuits have a response in the same form, a 1<sup>st</sup> order differential equation:

$$\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = k$$

- ▶  $\tau$  is a time constant,  $k$  is a constant
- ▶ We solve this by separation of variables

$$\frac{dx}{dt} = \frac{(k\tau - x)}{\tau} \implies \frac{dx}{x - k\tau} = -\frac{dt}{\tau}$$

- ▶ Integrate with respect to each derivative

$$\int \frac{1}{x - k\tau} dx = -\frac{1}{\tau} \int dt$$



# Response of RC and RL Circuits Cont'd

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary

- ▶ Evaluating the indefinite integrals

$$\ln(x - k\tau) = \frac{-t}{\tau} + c$$

- ▶ Exponentiating

$$x(t) = k\tau + Ae^{\frac{-t}{\tau}}$$

- ▶  $k\tau$  is the steady-state response (not dependent on time)
- ▶  $Ae^{\frac{-t}{\tau}}$  is the transient response (function of time)
- ▶ An initial condition must be supplied to the system:

$$\begin{aligned}x(t=0) = 0 &\implies x(0) = k\tau + Ae^{0} \xrightarrow{1} \\&\implies A = x(0) - k\tau\end{aligned}$$



# Response of RC and RL Circuits Cont'd

- Therefore, the solution can be expressed as

$$x(t) = k\tau + [x(0) - k\tau]e^{\frac{-t}{\tau}}$$

- As  $t \rightarrow \infty$ , we would reach the steady-state process

$$x(\infty) = \lim_{t \rightarrow \infty} = k\tau$$

- We still have an unknown variable, our time constant  $\tau$ . What other information do we have about our system?
- The solution, as  $t \rightarrow \infty$  is

$$x(t) = x(\infty) + [x(0) - x(\infty)]e^{\frac{-t}{\tau}}$$



# Response of RC and RL Circuits Cont'd

- If we differentiate  $x(t)$  w.r.t.  $t$ , we can isolate  $\tau$

$$\frac{dx(t)}{dt} = \frac{-1}{\tau}[x(0) - x(\infty)]e^{-\frac{t}{\tau}}$$

- At  $t = 0$ , we know our response should be that of the initial

$$\left. \frac{dx(t)}{dt} \right|_{t=0} = \frac{-1}{\tau}[x(0) - x(\infty)]$$

- Rearranging for  $\tau$

$$\tau = \frac{x(\infty) - x(0)}{\left. \frac{dx(t)}{dt} \right|_{t=0}}$$





# Evaluation of $\tau$ for RC Circuit

- ▶ For a RC circuit,  $x(t)=V(t)$ , it follows (by comparison)

$$\frac{dV(t)}{dt} + \frac{V(t)}{R_TC} = \frac{V_{oc}}{R_TC}$$

- ▶ i.e.  $\tau=R_TC$  and  $k=\frac{V_{oc}}{R_TC}$
- ▶ Our governing equation becomes

$$V(t) = V_{oc} + [V(0) - V_{oc}]e^{\frac{-t}{R_TC}}$$

- ▶ The forced response is  $V_{oc}$  and the natural response is the remainder



# Evaluation of $\tau$ for RL Circuit

- ▶ For a RL circuit,  $x(t)=i(t)$ , it follows (by comparison)

$$\frac{di(t)}{dt} + \frac{R_T}{L}i(t) = \frac{R_T}{L}i_{SC}$$

- ▶ i.e.  $\tau = \frac{L}{R_T}$  and  $k = \frac{L}{R_T}i_{SC}$
- ▶ Our governing equation becomes


$$i(t) = i_{SC} + [i(0) - i_{SC}]e^{-\frac{t}{\tau}}$$

- ▶ The forced response is  $i_{SC}$  and the natural response is the remainder



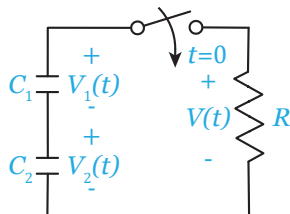
# Example #1

- Given  $R=250 \text{ [k}\Omega\text{]}$ ,  $C_1=5 \text{ [}\mu\text{F]}$ ,  $C_2=20 \text{ [}\mu\text{F]}$ ,  
 $V_1(t<0)=-4 \text{ [V]}$  and  $V_2(t<0)=24 \text{ [V]}$ , determine  
 $V_1(t)$ ,  $V_2(t)$ ,  $V(t)$  and  $i(t)$  for  $t \geq 0 \text{ [s]}$ .



# Example #1

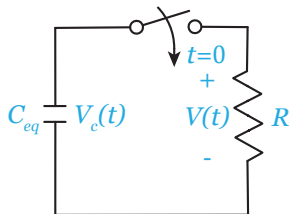

# Example #1

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary



# Example #1

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary



# Example #1

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary



# Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Construct and apply the constitutive equations of RC and RL circuits to determine the natural and forced response of a circuit
- ▶ A series RC and parallel RL circuit behavior is described as

$$\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = k$$

where  $\tau$  is the time constant,  $R_TC$  for RC and  $L/R_T$  for RL circuits, and  $k$  is the forcing constant,  $V_{oc}/R_TC$  for RC and  $Li_{sc}/R_T$  for RL circuits.





# Suggested Problems

- ▶ 8.3-1, 8.3-4, 8.3-5, 8.3-7, 8.3-10, 8.3-11, 8.3-17, 8.3-25

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

Learning Objectives

8.3 The Response of  
a First-Order  
Circuit to a  
Constant Input

Summary

