

Chapter 6 - The Operational Amplifier

Lecture 21

Section 6.7

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 6 - The
Operational
Amplifier

At the end of the lecture, students should be able to:

- ▶ Use the offsets model, finite gain model, and both the offsets and finite gain model to model the practical behavior of an operational amplifier
- ▶ Apply the CMRR model to the finite gain model to increase model fidelity

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Practical Op-amps

Chapter 6 - The
Operational
Amplifier

MEMS 0031

- ▶ The non-ideal parameters of op-amps that we have thus ignored include:
 1. Non-zero bias currents
 2. Non-zero input offset voltage
 3. Finite input resistance
 4. Non-zero output resistance
 5. Finite voltage gain
- ▶ Including these increases the fidelity of our models, but the question we must ask: “is it worth it?”

Learning Objectives


6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Offsets Model

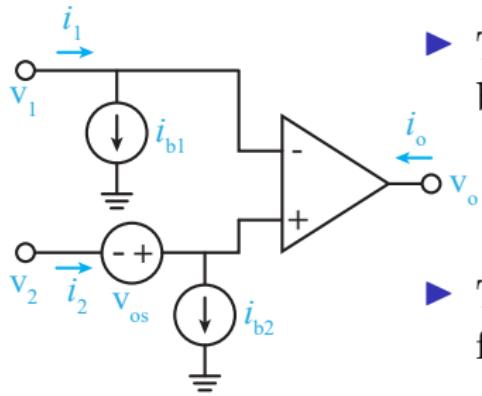- ▶ The offsets model accounts for non-zero bias current (i_{b1} and i_{b2}) and non-zero input offset voltage (V_{os}), as shown below:



- ▶ The equations of behavior become:
 $i_1 = i_{b1}; \quad i_2 = i_{b2};$
 $V_1 - V_2 = V_{os}$
- ▶ This model does not account for finite input resistance

- ▶ The input offset current is defined as:

$$i_{os} = i_{b1} - i_{b2}$$

- ▶ The input offset bias current is typically on the order of tens of [pA] to tens of [nA], and V_{os} on the order tens of [nV] to tens of [mV]

Learning Objectives


6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



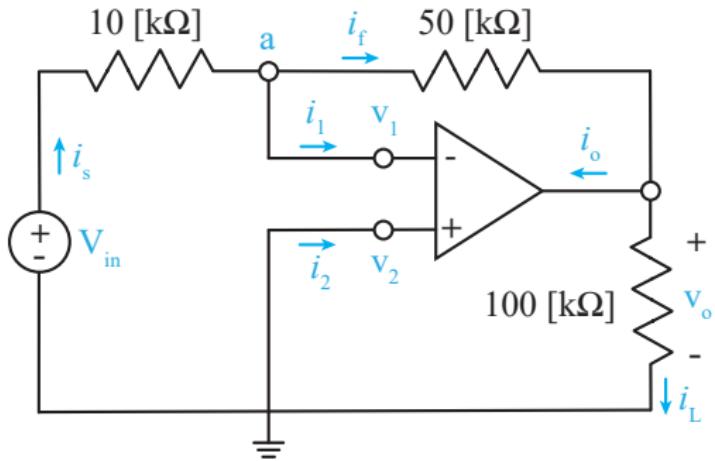Example #1

- ▶ Consider a μ A741 op-amp in an inverting configuration, where the gain is 5. Model as an ideal op-amp, and then use the offsets model.



Learning Objectives


6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



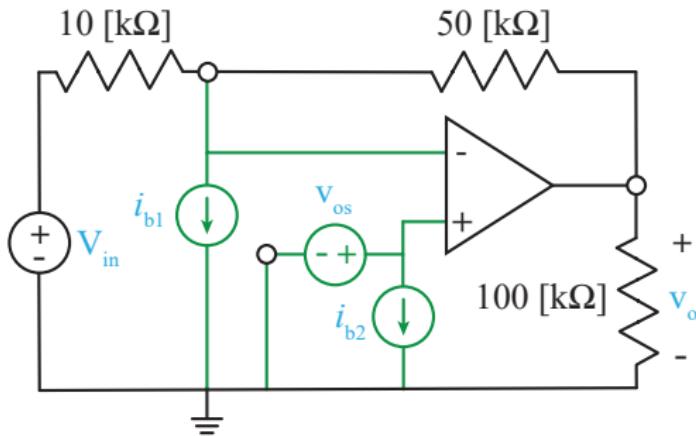Example #1

- ▶ Consider a μ A741 op-amp in an inverting configuration, where the gain is 5. Model as an ideal op-amp, and then use the offsets model.



Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary




Example #1


Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary

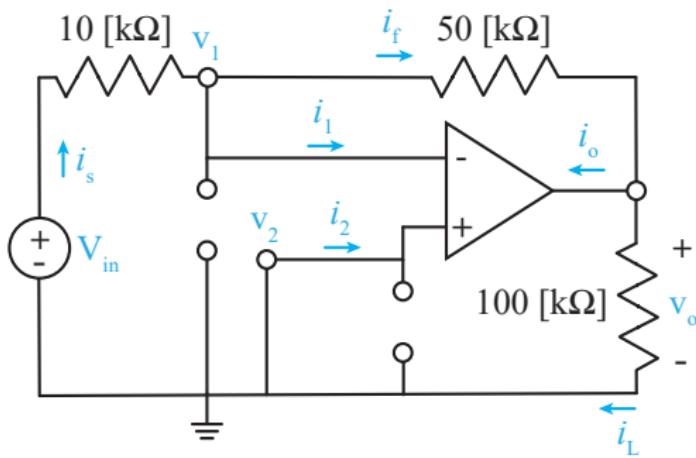

Example #1

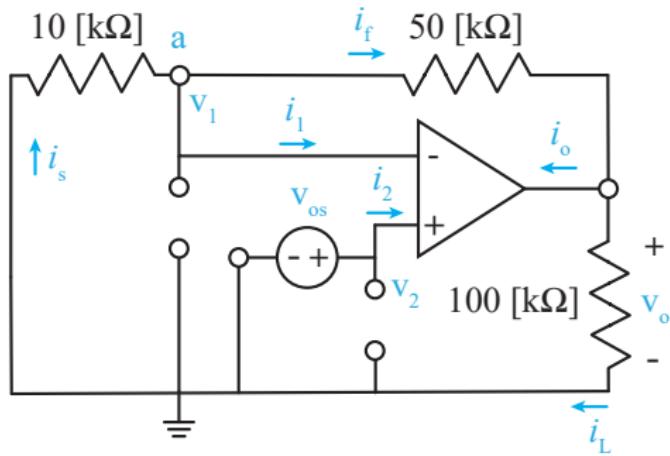

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary




Example #1


Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary

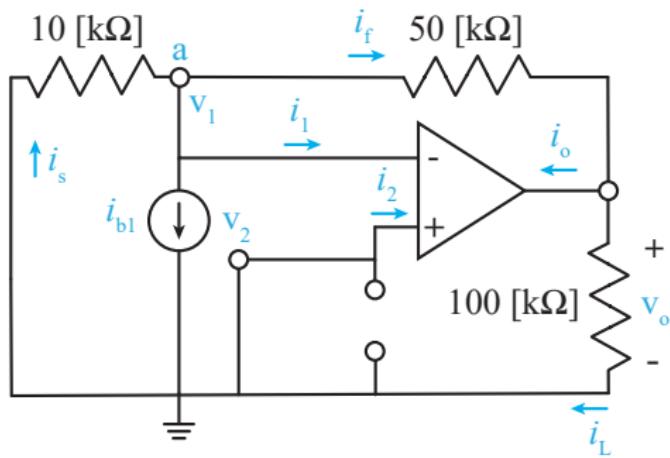

Example #1

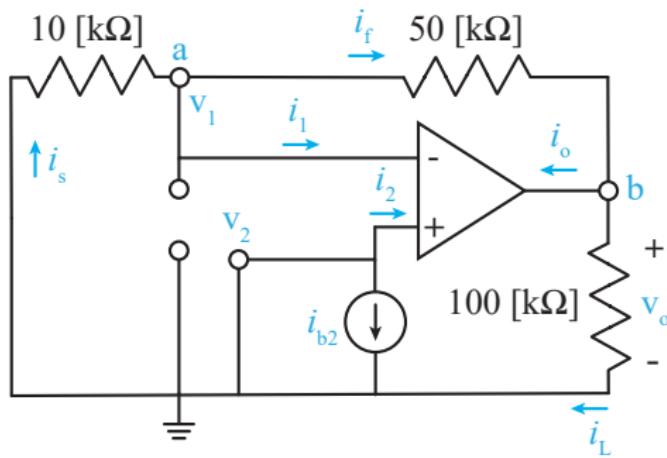


Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Example #1

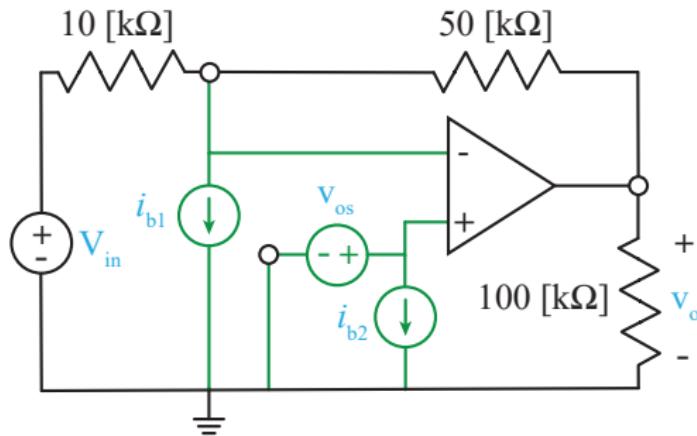

Learning Objectives


6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Finite Gain Model

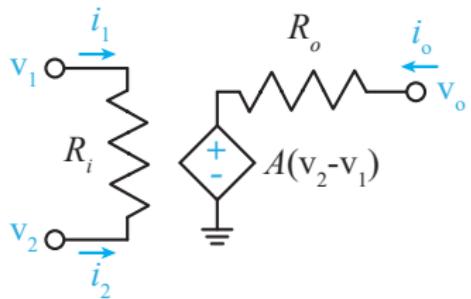- ▶ The finite gain model accounts for:
 1. Finite input resistance, R_i ;
 2. Non-zero output resistance, R_o ;
 3. Finite voltage gain, V_o
- ▶ However, it does not include non-zero bias current nor non-zero input offset voltage
- ▶ The schematic of the finite gain model is shown below, with governing equations



$$V_o = A(V_2 - V_1) + R_o i_o$$

$$i_1 = \frac{V_1 - V_2}{R_i}$$

$$i_2 = \frac{V_2 - V_1}{R_i}$$

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers


Summary

Example #2

- ▶ A voltage follower (see Fig. 6.5-1 c) on pg. 217 acts as a buffer amplifier. The gain associated with a follower is unity. Model this type of amplifier using the finite gain model to quantify the effect of R_i and R_o on V_o , in comparison to the ideal model.

Givens:

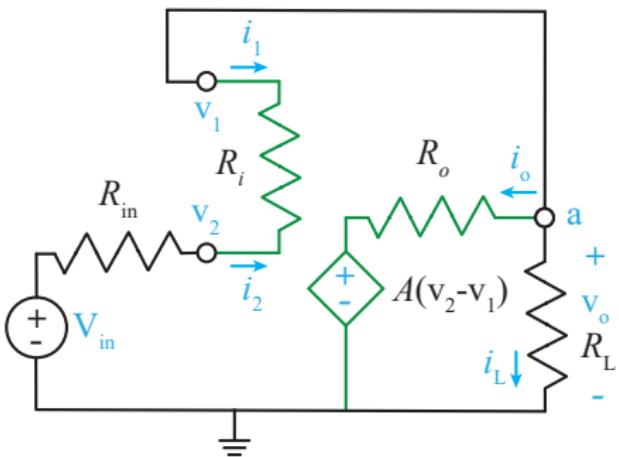- ▶ $R_{in}=1 \text{ [k}\Omega\text{]}$
- ▶ $R_L=10 \text{ [k}\Omega\text{]}$
- ▶ $R_i=100 \text{ [\kappa}\Omega\text{]}$
- ▶ $R_o=100 \text{ [\Omega]}$
- ▶ $A=10^5$




Example #2

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary

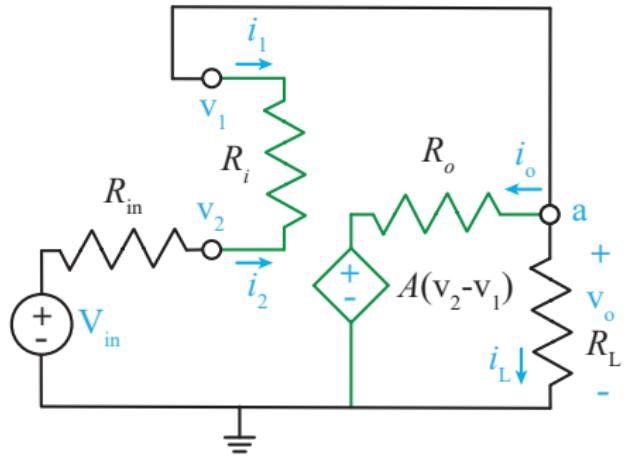


Example #2

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary

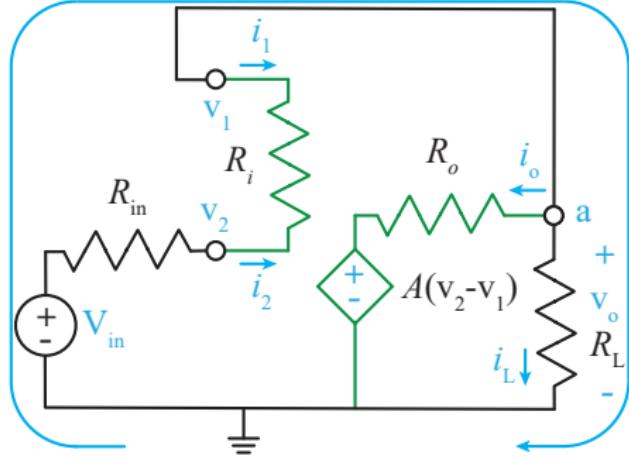

- ▶ Another important parameter is the Common Mode Rejection Ratio (CMRR), which modifies the output of the op-amp in the finite gain model such that

$$A(V_2 - V_1) \rightarrow A(V_2 - V_1) + A_{\text{cm}} \left(\frac{V_1 + V_2}{2} \right)$$

- ▶ The third term is the common mode gain times the common mode input voltage
- ▶ Thus, the CMRR is:

$$\text{CMRR} = \frac{A}{A_{\text{cm}}}$$

- ▶ Thus, we can modify the finite gain model with

$$A(V_2 - V_1) \rightarrow A \left(\left(1 + \frac{1}{2\text{CMRR}} \right) V_2 - \left(1 - \frac{1}{2\text{CMRR}} \right) V_1 \right)$$

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Example #3

- ▶ Consider a μ A741 op-amp. Determine the output of the VCVS using the finite gain model and compare to that using the finite gain model with CMRR.

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Student Learning Objectives

Chapter 6 - The
Operational
Amplifier

At the end of the lecture, students should be able to:

- ▶ Use the offsets model, finite gain model, and both the offsets and finite gain model to model the practical behavior of an operational amplifier
 - ▶ The offsets model includes provisions for non-zero bias currents (on the order of pico- to nano-amps), and an offset voltage, on the order of nano- to milli-volts
 - ▶ The finite gain model considers device resistance and limits the voltage output of the Op-amp
- ▶ Apply the CMRR model to the finite gain model to increase model fidelity
 - ▶ The CMRR model is a way to quantify the rejection of simultaneous terminal inputs

MEMS 0031

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary



Suggested Problems

Chapter 6 - The
Operational
Amplifier

- ▶ 6.7-1, 6.7-2, 6.7-3, 6.7-4

MEMS 0031

Learning Objectives

6.7 Characteristics
of Practical
Operational
Amplifiers

Summary

