

Chapter 9 - The Complete Response of Circuits with Two Energy Storage Elements

Lecture 29 Sections 9.1-9.6

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary



Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Describe the behavior or RLC circuits using second-order, ordinary differential equations

Chapter 9 - The Complete Response of Circuits with Two Energy Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.

9.4 - Over-damped Response

9.6 - Under-damped Response

9.5 - Critically Damped Response

Summary



Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.

9.4 - Over-damped Response

9.6 - Under-damped Response

9.5 - Critically Damped Response

Summary

- ▶ We will work with the general second-order, ordinary differential equation

$$\frac{d^2x(t)}{dt^2} + 2\alpha\frac{dx(t)}{dt} + \omega_0^2x(t) = f(t)$$

- ▶ $x(t)$ is the output of the circuit (i.e. $i(t)$ or $v(t)$)
- ▶ $f(t)$ is the input, either a constant or can vary with time



The RLC Circuit

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.


9.4 - Over-damped Response

9.6 - Under-damped Response

9.5 - Critically Damped Response

Summary

- Consider the RLC circuit

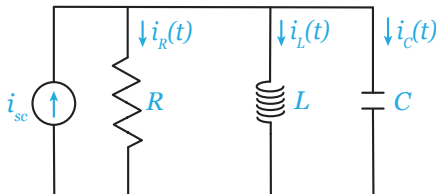

- Constructing a KCL equation at the top node

$$i_{sc} = i_R + i_L + i_C$$

- Employing the constitutive equations for each component in terms of node voltages

$$i_{sc} = \frac{v}{R} + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i_0 + C \frac{dv}{dt}$$



The *RLC* Circuit

Chapter 9 - The Complete Response of Circuits with Two Energy Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.

9.4 - Over-damped Response

9.6 - Under-damped Response

9.5 - Critically Damped Response

Summary

- ▶ To eliminate the integral, we differentiate the equation

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = 0$$

- ▶ Dividing by C and arranging in order of derivatives

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

- ▶ Thus, we have the natural response for an *RLC* circuit



Natural Response of RLC Circuit

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
 RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary

- ▶ The response is going to be that of the homogeneous

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

- ▶ The characteristic equation is

$$\lambda^2 + \frac{1}{RC} \lambda + \frac{1}{LC} = 0$$

- ▶ Using the quadratic equation and solving for λ

$$\lambda_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

- ▶ Thus, our solution takes the form

$$v(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$$



Natural Response of RLC Circuit

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.

9.4 - Over-damped Response

9.6 - Under-damped Response

9.5 - Critically Damped Response

Summary

- ▶ For simplicity, we will define α , the Neper frequency, as

$$\alpha = \frac{1}{2RC}$$

- ▶ We will also define ω_0 , the resonant radian frequency, as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- ▶ Thus, the roots becomes

$$\lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

- ▶ Thus, we are back at the original form

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = f(t)$$



Example #1

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.


9.4 - Over-damped Response

9.6 - Under-damped Response

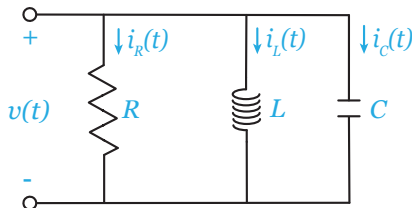9.5 - Critically Damped Response

Summary

- Consider an RLC circuit where $v(0^+)=12$ [V] and $i_L(0^+)=30$ [mA]



- Given $C=0.2$ [μF], $L=50$ [mH], $R=200$ [Ω], determine the initial current value in each branch and $v(t)$.



Example #1

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary



Example #1

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary



Example #1

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary



Example #1

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response


9.5 - Critically
Damped Response

Summary



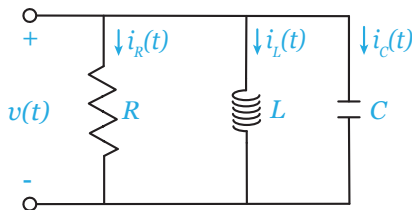Example #2

- Consider an RLC circuit where $v(0^+) = 12$ [V] and $i_L(0^+) = 30$ [mA]



- Given $C = 0.2$ [μF], $L = 50$ [mH], $R = 400$ [Ω], determine the initial current value in each branch and $v(t)$.

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary



Example #2

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

**9.6 - Under-damped
Response**

9.5 - Critically
Damped Response

Summary



Example #2

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

**9.6 - Under-damped
Response**

9.5 - Critically
Damped Response

Summary



Example #2

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary



Example #2

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

**9.6 - Under-damped
Response**

9.5 - Critically
Damped Response

Summary



Example #3

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.


9.4 - Over-damped
Response

9.6 - Under-damped
Response

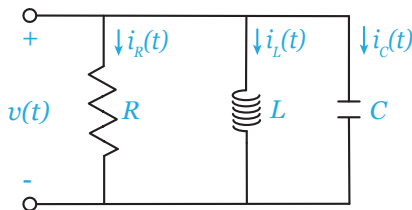9.5 - Critically
Damped Response

Summary

- Consider an RLC circuit where $v(0^+)=12$ [V] and $i_L(0^+)=30$ [mA]



- Given $C=0.2$ [μF], $L=50$ [mH], $R=250$ [Ω], determine the initial current value in each branch and $v(t)$.



Example #3

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

**9.5 - Critically
Damped Response**

Summary



Example #3

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

**9.5 - Critically
Damped Response**

Summary



Example #3

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

**9.5 - Critically
Damped Response**

Summary



Example #3

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

**9.5 - Critically
Damped Response**

Summary



Student Learning Objectives

Chapter 9 - The
Complete Response
of Circuits with
Two Energy
Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for
RLC Circuits

9.3 - Soln. of 2nd
Order Diff. Eqn.

9.4 - Over-damped
Response

9.6 - Under-damped
Response

9.5 - Critically
Damped Response

Summary

At the end of the lecture, students should be able to:

- ▶ Describe the behavior of *RLC* circuits using second-order, ordinary differential equations
 - ▶ A second-order ordinary differential equation is used to describe the behavior of parallel *RLC* circuits.
 - ▶ If $\alpha^2 > \omega_0^2$, the circuit is overdamped
 - ▶ If $\alpha^2 < \omega_0^2$, the circuit is underdamped
 - ▶ If $\alpha^2 = \omega_0^2$, the circuit is critically damped



Suggested Problems

- ▶ 9.2-1, 9.2-2, 9.2-5, 9.2-6, 9.2-7, 9.2-9, 9.2-10, 9.2-11, 9.2-15, 9.3-4, 9.4-5, 9.5-1, 9.5-3, 9.6-2

Chapter 9 - The Complete Response of Circuits with Two Energy Storage Elements

MEMS 0031

Learning Objectives

9.1 - Introduction

9.2 - Diff. Eqn. for RLC Circuits

9.3 - Soln. of 2nd Order Diff. Eqn.

9.4 - Over-damped Response

9.6 - Under-damped Response

9.5 - Critically Damped Response

Summary

