

NVA Worksheet

MEMS 0031 - Electrical Circuits

February 23, 2021

Problem #1

- Use NVA to solve for the current i from the current source for the circuit shown in Fig. 1.

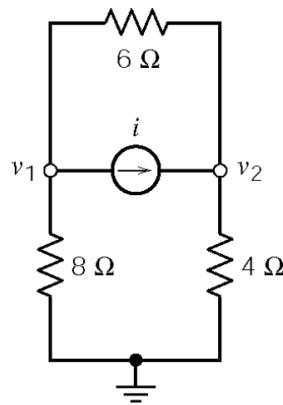


Figure 1: Schematic for Problem #1.

Problem #2

- Use NVA to solve for v_1 , v_2 and v_3 in the circuit shown in Fig. 2.

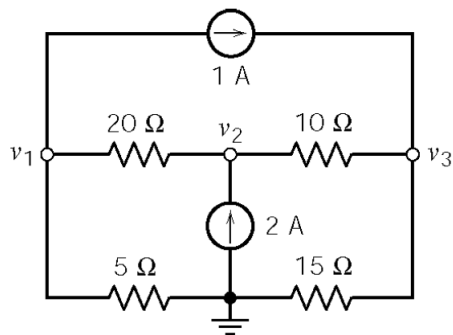


Figure 2: Schematic for Problem #2.

Problem #3

- Use NVA to find v_a , v_b and v_c of the circuit shown in Fig. 3. Determine the voltage potential v_c across the $8\ \Omega$ resistor.

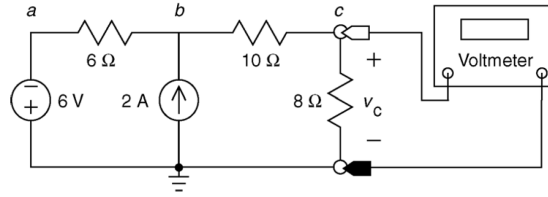


Figure 3: Schematic for Problem #3.

Problem #4

- Use NVA to find the voltage drop v_a across the $100\ \Omega$ resistor the circuit shown in Fig. 4. Hint: the supernode is highlighted in blue.

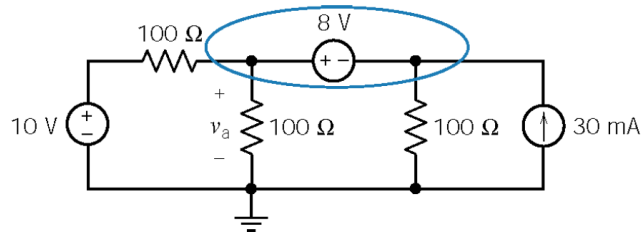


Figure 4: Schematic for Problem #4.

Problem #5

- Use NVA to find i_1 , i_2 and the gain of the CCCS in the circuit shown in Fig. 5.

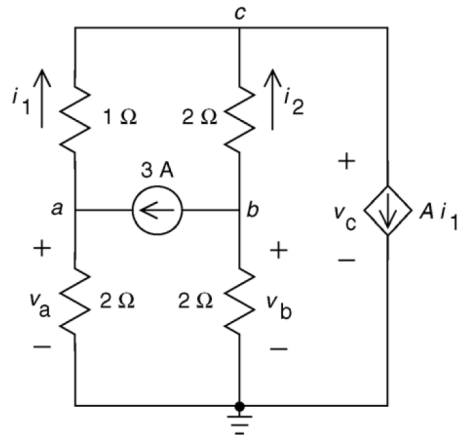


Figure 5: Schematic for Problem #5.

Problem #6

- Use NVA to find i_x in the circuit shown in Fig. 6.

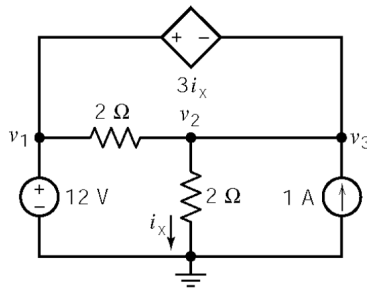


Figure 6: Schematic for Problem #6.