

Chapter 5 - Circuit Theorems

Lecture 17

Sections 5.6

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 5 - Circuit
Theorems

MEMS 0031

Learning Objectives

5.6 Maximum
Power Transfer

Summary


At the end of the lecture, students should be able to:

- ▶ Construct an expression that relates the maximum power transferred by a circuit to the load resistance



Maximum Power Transfer

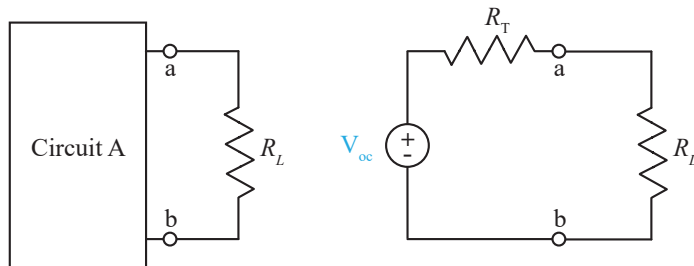- ▶ Choose R_L to maximize P of the circuit
- ▶ Or, given R_L , design a circuit to provide maximum P



- ▶ Remember the expression for Power:

$$P = i^2 R_L = \left(\frac{V_{oc}}{R_t + R_L} \right)^2 R_L$$



Maximum Power Transfer

Chapter 5 - Circuit
Theorems

MEMS 0031

Learning Objectives

5.6 Maximum
Power Transfer


Summary

- ▶ How do we mathematically determine which value of R_t maximizes R_L ?



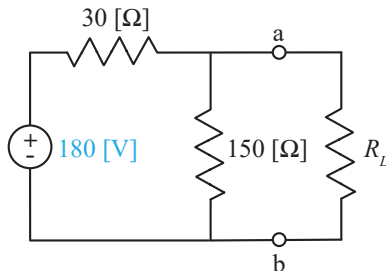Example #1

- Find R_L that maximizes P , and determine P



Learning Objectives


5.6 Maximum
Power Transfer

Summary



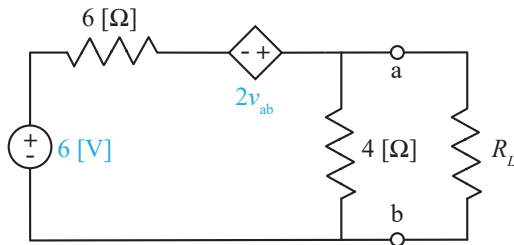Example #2

- Find R_L that maximizes P , and determine P



Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Construct an expression that relates the maximum power transferred by a circuit to the load resistance
- ▶ Maximum power transfer occurs when the load resistance is equal to the internal resistance of the circuit.



Suggested Problems

Chapter 5 - Circuit
Theorems

MEMS 0031

► 5.6-1, 5.6-2, 5.6-3, 5.6-5, 5.6-6, 5.6-7, 5.6-8

Learning Objectives

5.6 Maximum
Power Transfer

Summary

