

# Op-amp Worksheet


MEMS 0031 - Electrical Circuits

June 17<sup>th</sup>, 2020
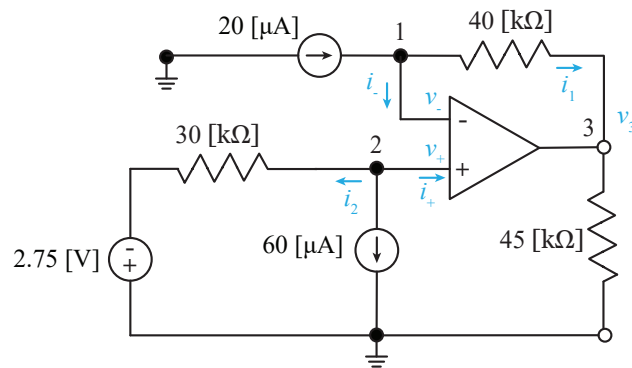
## Problem #1

Determine the reading of the voltmeter in the circuit shown below.

To find the reading of the voltmeter, NVA will need to be used to determine the nodal voltage at the output of the op-amp. Node voltages are defined as 1, 2, and 3 in the circuit shown.



The op-amp is assumed to be ideal. Therefore, it can be said that:

$$(v_+) = (v_-); \quad i_+ = 0; \quad i_- = 0$$

Nodes 1 and 2 have nodal voltage values of  $v_-$  and  $v_+$  respectively. Applying KCL to node 1:

$$20 [\mu\text{A}] = i_1 + i_- \implies 20 [\mu\text{A}] = \frac{V_1 - V_3}{40 [\text{k}\Omega]} + \cancel{i_-}^0$$

Applying KCL to node 2:

$$i_+ + i_2 + 60 [\mu\text{A}] = 0 \implies \cancel{i_+}^0 + \frac{V_2 - (-2.75 [\text{V}])}{30 [\text{k}\Omega]} + 60 [\mu\text{A}] = 0$$

We see the  $V_2$  is found directly from our second KCL equation to be:

$$V_2 = -4.55 [\text{V}]$$

And we know  $V_1 = V_2 = -4.55 [\text{V}]$ .


$$(v_+) - (v_-) = 0$$

With  $V_1$  known, we can solve  $V_3$  from our first KCL equation:  $V_3 = -5.35 [\text{V}]$
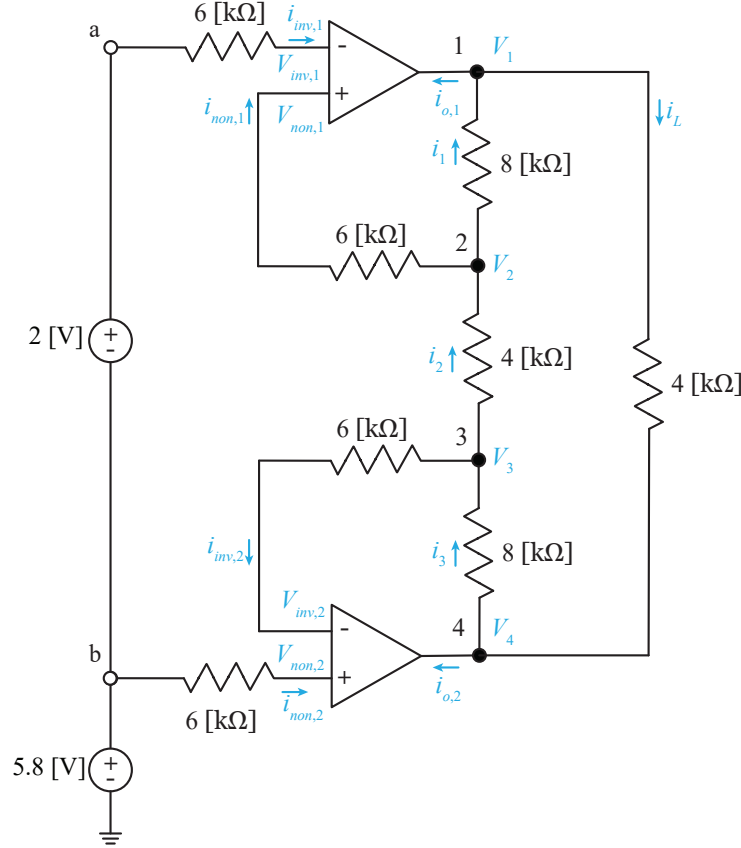
## Problem #2

In the circuit shown below, determine the current  $i_o$ . Assume that the operational amplifiers are ideal. To do such, we need to determine the node voltages  $V_1$  and  $V_4$ .

The current  $i_L$  can be determine by finding the voltage drop across the 4 [k $\Omega$ ] resistor.



The op-amps used are assumed to be ideal. Therefore:

$$V_{non,1} = V_{inv,1}; \quad V_{non,2} = V_{inv,2}; \quad i_{non,1} = i_{inv,1} = 0; \quad i_{non,2} = i_{inv,2} = 0$$

We note the node voltage  $V_b = 5.8$  [V], and that:

$$V_a - V_b = 2 \text{ [V]} \implies V_a = 7.8 \text{ [V]}$$

Top op-amp:

Since  $i_{inv,1}$  is equal to zero,  $V_{inv,1} = V_a$ . This also means  $V_{non,1} = V_{inv,1} = V_a$ . Since  $i_{non,1}$  is equal to zero,  $V_2 = V_{non,1} = V_a$ . Therefore, the voltage at node 2 is 7.8 [V].

Bottom op-amp:

Since  $i_{non,2}$  is equal to zero,  $V_{non,2} = V_b$ . This also means  $V_{inv,2} = V_{non,2} = V_b$ . Since  $i_{inv,2}$  is equal to zero,  $V_3 = V_{inv,2} = V_b$ . Therefore, the voltage at node 3 is 5.8 [V].

With the  $V_2$  and  $V_3$  known, we can work toward solving  $V_1$  and  $V_4$ . First, we will find  $i_2$ :

$$i_2 = \frac{V_3 - V_2}{4 \text{ [k}\Omega\text{]}} = \frac{(5.8 - 7.8) \text{ [V]}}{4 \text{ [k}\Omega\text{]}} = -0.5 \text{ [mA]}$$

Applying KCL at node 2:

$$i_2 = \cancel{i_{\text{res},1}} + \overset{0}{i_1} \implies i_1 = -0.5 \text{ [mA]}$$

Solving for  $V_1$ :

$$i_1 = \frac{V_2 - V_1}{8 \text{ [k}\Omega]} \implies V_1 = V_2 - i_1(8 \text{ [k}\Omega]) = 7.8 \text{ [V]} - (-0.5 \text{ [mA]})(8 \text{ [k}\Omega]) = 11.8 \text{ [V]}$$

Applying KCL at node 3:

$$i_3 = \cancel{i_{\text{res},2}} + \overset{0}{i_2} \implies i_3 = -0.5 \text{ [mA]}$$

Solving for  $V_4$ :

$$i_3 = \frac{V_4 - V_3}{8 \text{ [k}\Omega]} \implies V_4 = V_3 + i_3(8 \text{ [k}\Omega]) = 5.8 \text{ [V]} + (-0.5 \text{ [mA]})(8 \text{ [k}\Omega]) = 1.8 \text{ [V]}$$

Therefore, the current  $i_L$  can be found via Ohm's law:

$$i_L = \frac{V_1 - V_4}{4 \text{ [k}\Omega]} = \frac{(11.8 - 1.8) \text{ [V]}}{4 \text{ [k}\Omega]} = 2.5 \text{ [mA]}$$