

## Homework #2


MEMS 0031 - Electrical Circuits

Assigned: May 15<sup>th</sup>, 2020

Due: May 20<sup>th</sup>, 2020 at 11:59 pm

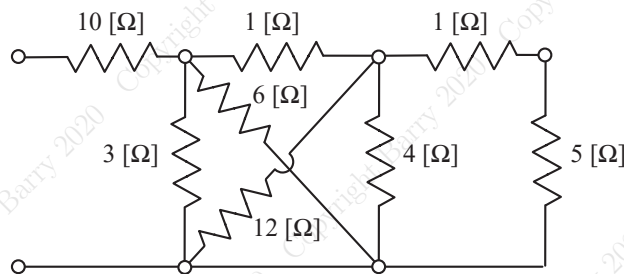
### Problem #1

Given the circuit below, determine the equivalent resistance,  $R_{eq}$ . Note the bridge.



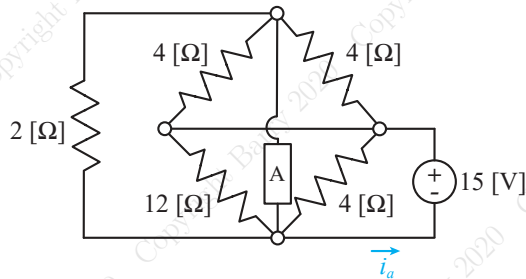
### Problem #2

Given the circuit below, determine the current,  $i_a$  by using equivalent resistances. *Element A* has a resistance of 2 Ω. Note the bridge.


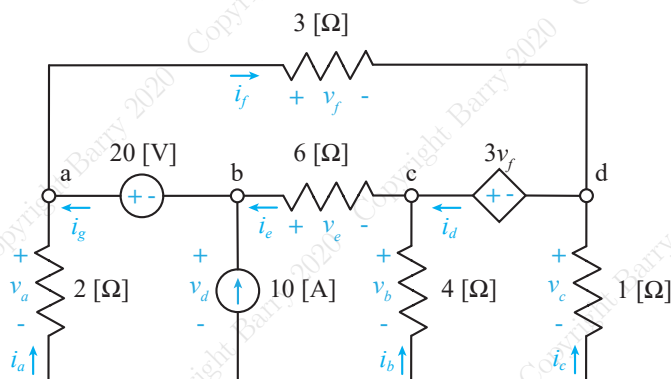
### Problem #3

Using a combination of KCL and KVL, determine the currents  $i_a$  through  $i_g$ , and the voltage potentials  $v_a$  through  $v_f$  across each resistor and current source. Note: if a necessary current or voltage potential is not specified, please denote it with the next variable in alphabetical sequence.



### Problem #4

Using a combination of KCL and KVL, determine the currents  $i_a$  through  $i_j$ , and the voltage potentials  $v$  through  $v$  across each resistor and current source. Note: if a necessary current or voltage potential is not specified, please denote it with the next variable in alphabetical sequence.

