

Homework #2

MEMS 0031 - Electrical Circuits

Assigned January 21st, 2019
Due January 25th, 2019

Problem #1

- In the circuits shown below, (a)-(e), determine:
 - The unknown value(s) of i and/or v .
 - The power dissipated by each resistor.
- For the circuit shown in (f), develop a system of equations that would allow you to determine the current in each element, and solve for the current i_a symbolically in terms of all other circuit variables.

Solutions:


Part (a):

Using Ohm's law to find the voltage drop across the $8 \text{ } [\Omega]$ resistor:

$$v_a = iR = (1 \text{ [A]})(8 \text{ } [\Omega]) = 8 \text{ [V]}$$

Note the resistor is in accordance with the passive sign convention. The power dissipated is calculated as either a function of current and resistance, or voltage and current, and is found as:
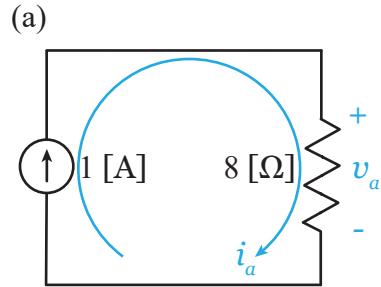
$$P_{dis} = i^2 R = iV = (1 \text{ [A]})^2(8 \text{ } [\Omega]) = (1 \text{ [A]})(8 \text{ [V]}) = 8 \text{ [W]}$$




Part (b):

Using Ohm's law to find the current through the $25 \text{ } [\Omega]$ resistor:

$$v_a = i_a R \implies i_a = \frac{v_a}{R} = \frac{50 \text{ [V]}}{25 \text{ } [\Omega]} = 2 \text{ [A]}$$


Note the resistor is in accordance with the passive sign convention. The power dissipated is calculated as either a function of current and resistance, or voltage and current, and is found as:
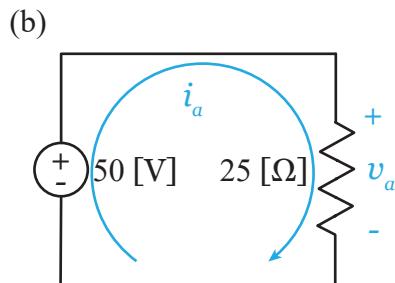
$$P_{dis} = i^2 R = iV = (2 \text{ [A]})^2(25 \text{ } [\Omega]) = (2 \text{ [A]})(50 \text{ [V]}) = 100 \text{ [W]}$$



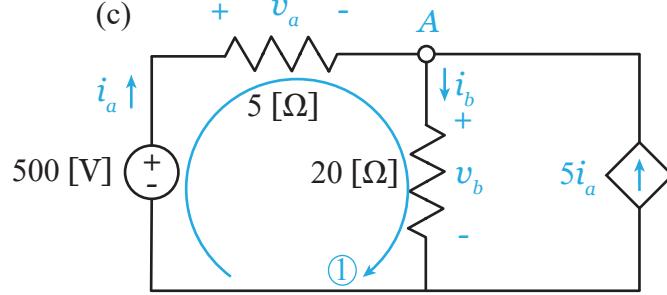Part (c):

We have a variety of unknowns within the system: v_a , v_b , and most importantly, i_a . To generate an equation that relates i_a to the two sources, we can use KVL around ①, expressing the voltage drop across the resistors using Ohm's law, denoting the current through the $20 \text{ } [\Omega]$ resistor as i_b :



$$\text{KVL around Loop ① : } -500 \text{ [V]} + v_a + v_b = 0$$

Expressing v_a and v_b using Ohm's law:

$$\begin{aligned} &\Rightarrow -500 \text{ [V]} + i_a(5 \text{ } [\Omega]) + i_b(20 \text{ } [\Omega]) = 0 \\ &\Rightarrow i_a(5 \text{ } [\Omega]) + i_b(20 \text{ } [\Omega]) = 500 \text{ [V]} \end{aligned}$$

Now, we have one equation and two unknowns. Defining node A at the junction of the two resistors and CCCS, we can apply KCL at said node:

$$\text{KCL at Node } A : i_a + 5i_a = i_b \Rightarrow i_b = 6i_a$$

We can substitute this back into the KVL equation such that:

$$\begin{aligned} i_a(5 \text{ } [\Omega]) + (6i_a)(20 \text{ } [\Omega]) &= 500 \text{ [V]} \Rightarrow i_a(125 \text{ } [\Omega]) = 500 \text{ [V]} \\ \therefore i_a &= 4 \text{ [A]} \end{aligned}$$

Thus, we can solve for i_b from the KCL equation such that:

$$i_b = 6i_a \Rightarrow i_b = 24 \text{ [A]}$$

The voltages across each resistor can be found via Ohm's law, which was expressed in the original KVL equation:

$$\begin{aligned} v_a &= i_a(5 \text{ } [\Omega]) = (4 \text{ [A]})(5 \text{ } [\Omega]) \Rightarrow v_a = 20 \text{ [V]} \\ v_b &= i_b(20 \text{ } [\Omega]) = (24 \text{ [A]})(20 \text{ } [\Omega]) \Rightarrow v_b = 480 \text{ [V]} \end{aligned}$$


The power dissipated by each resistor is found as a function of current and resistance or current and voltage. Note, the resistors are already represented in PSC.

$$P_{dis, 5 \text{ } [\Omega]} = (i_a)^2(5 \text{ } [\Omega]) = i_a v_a = (4 \text{ [A]})^2(5 \text{ } [\Omega]) = (4 \text{ [A]})(20 \text{ [V]}) \Rightarrow P_{dis, 5 \text{ } [\Omega]} = 80 \text{ [W]}$$

$$P_{dis, 20 \text{ } [\Omega]} = (i_b)^2(20 \text{ } [\Omega]) = i_b v_b = (24 \text{ [A]})^2(20 \text{ } [\Omega]) = (24 \text{ [A]})(480 \text{ [V]}) \Rightarrow P_{dis, 20 \text{ } [\Omega]} = 11,520 \text{ [W]}$$

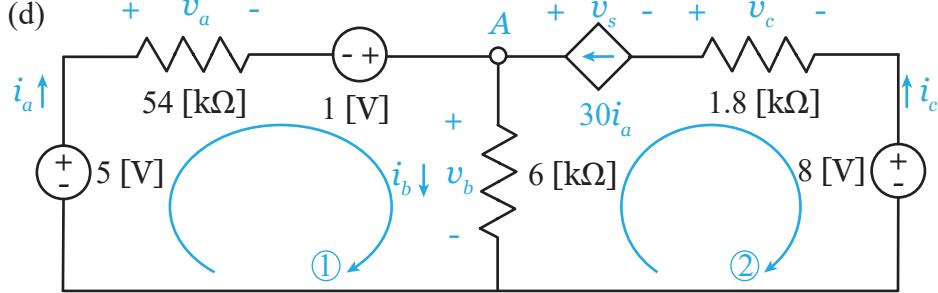Part (d):

We recognize there are two independent loops in the circuit, ① and ②. We can apply two separate KVL equation around these loops to determine pertinent system parameters.



Starting with the first loop:

$$-5 \text{ [V]} + v_a - 1 \text{ [V]} + v_b = 0$$

Applying Ohm's law:

$$-5 \text{ [V]} + i_a(54 \text{ [k}\Omega\text{]}) - 1 \text{ [V]} + i_b(6 \text{ [k}\Omega\text{]}) = 0$$

We have two unknowns, i_a and i_b . We will relate these two by applying KCL at node A:

$$i_a + 30i_a = i_b \implies i_b = 31i_a$$

We have two equations for two unknowns. Solving for i_a :

$$i_a = 25 \text{ [\mu A]}$$

Solving for i_b :

$$i_b = 775 \text{ [\mu A]}$$

The voltages across each resistor can be found via Ohm's law, which was expressed in the original KVL equation:

$$v_a = i_a(54 \text{ [k}\Omega\text{]}) = (25 \text{ [\mu A]})(54 \text{ [k}\Omega\text{]}) \implies v_a = 1.35 \text{ [V]}$$

$$v_b = i_b(6 \text{ [k}\Omega\text{]}) = (775 \text{ [\mu A]})(6 \text{ [k}\Omega\text{]}) \implies v_b = 4.65 \text{ [V]}$$

The power dissipated by the two resistors encircled by the first loop is found as:

$$P_{dis, 54 \text{ [k}\Omega\text{]}} = (i_a)^2(54 \text{ [k}\Omega\text{]}) = (25 \text{ [\mu A]})^2(54 \text{ [k}\Omega\text{]}) \implies P_{dis, 54 \text{ [k}\Omega\text{]}} = 33.75 \text{ [\mu W]}$$

$$P_{dis, 6 \text{ [k}\Omega\text{]}} = (i_b)^2(6 \text{ [k}\Omega\text{]}) = (775 \text{ [\mu A]})^2(6 \text{ [k}\Omega\text{]}) \implies P_{dis, 6 \text{ [k}\Omega\text{]}} = 3,603.75 \text{ [\mu W]}$$

Moving to the second loop, we recognize that i_c must be equal to $i_b - i_a$, or $30i_a$. Solving for i_c :

$$i_c = 30i_a \implies i_c = 750 \text{ [\mu A]}$$

The voltage across the $1.8 \text{ [k}\Omega\text{]}$ is found via Ohm's law. It is noted that the resistor is depicted having an active sign convention. Solving for v_c as it is represented:

$$\nu_c = i_c(1.8 \text{ [k}\Omega\text{]}) = (750 \text{ [\mu A]})(1.8 \text{ [k}\Omega\text{]}) \implies \nu_c = -1.35 \text{ [V]}$$

Applying KVL and recognizing there exists a voltage drop across the CCCS:

$$-v_b + v_s + v_c + 8 \text{ [V]} = 0$$

Applying Ohm's law, and recognizing the 1.8 [kΩ] resistor is depicted having an active sign convention:

$$-i_b(6 \text{ [k}\Omega\text{]}) + v_s + (30i_a)(1.8 \text{ [k}\Omega\text{]}) + 8 = 0$$


$$\Rightarrow v_s = (6 \text{ [k}\Omega\text{]})(775 \text{ [\mu A]}) + (1.8 \text{ [k}\Omega\text{]})(30(25 \text{ [\mu A]})) - 8 \text{ [V]} \Rightarrow v_s = -2 \text{ [V]}$$

The power dissipated in the 1.8 [kΩ] resistor is found as:

$$P_{dis, 1.8 \text{ [k}\Omega\text{]}} = (i_c)^2(1.8 \text{ [k}\Omega\text{]}) = (750 \text{ [\mu A]})^2(1.8 \text{ [k}\Omega\text{]}) \Rightarrow P_{dis, 1.8 \text{ [k}\Omega\text{]}} = 1,012.5 \text{ [\mu W]}$$

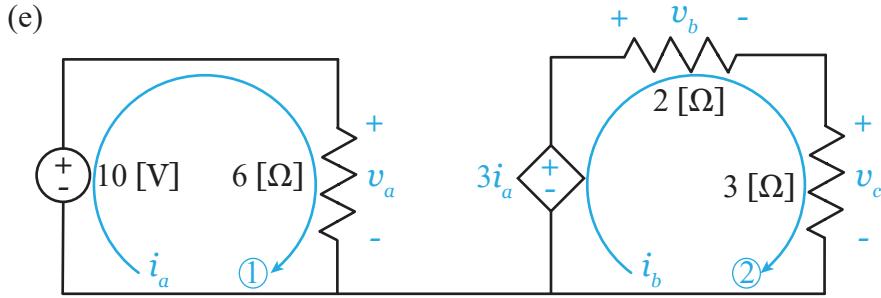Part (e):

We recognize there are two independent loops in the circuit, ① and ②. We can apply two separate KVL equation around these loops to determine pertinent system parameters.



Starting with the first loop:

$$\text{KVL around Loop ①} : -10 \text{ [V]} + v_a = 0$$

Applying Ohm's law:

$$i_a(6 \text{ [\Omega]}) = 10 \text{ [V]} \Rightarrow i_a = \frac{10 \text{ [V]}}{6 \text{ [\Omega]}} \Rightarrow i_a = 1.6 \text{ [A]}$$

Therefore, v_a can be determined via Ohm's law or the previous KVL equation:

$$\therefore v_a = 10 \text{ [V]}$$

Continuing with the second loop, applying KVL:

$$-3i_a + v_b + v_c = 0$$

Applying the value for i_a and Ohm's law:

$$-3(1.6 \text{ [V]}) + i_b(5 \text{ [\Omega]}) = 0 \Rightarrow i_b = 1 \text{ [A]}$$

Thus, the voltage across the 2 and 3 [Ω] resistors is found as:

$$v_b = i_b R = (1 \text{ [A]})(2 \text{ [\Omega]}) \Rightarrow v_b = 2 \text{ [V]}$$

$$v_c = i_b R = (1 \text{ [A]})(3 \text{ [\Omega]}) \Rightarrow v_c = 3 \text{ [V]}$$

The power dissipated by each resistor is as follows:


$$P_{dis, 6 \text{ [\Omega]}} = (i_a)^2(6 \text{ [\Omega]}) = i_a v_a = (1.6 \text{ [A]})^2(6 \text{ [\Omega]}) = (1.6 \text{ [A]})(10 \text{ [V]}) \Rightarrow P_{dis, 6 \text{ [\Omega]}} = 16.6 \text{ [W]}$$

$$P_{dis, 2 \text{ [\Omega]}} = (i_b)^2(2 \text{ [\Omega]}) = i_b v_b = (1 \text{ [A]})^2(2 \text{ [\Omega]}) = (1 \text{ [A]})(2 \text{ [V]}) \Rightarrow P_{dis, 2 \text{ [\Omega]}} = 2 \text{ [W]}$$

$$P_{dis, 3 \text{ [\Omega]}} = (i_b)^2(3 \text{ [\Omega]}) = i_b v_c = (1 \text{ [A]})^2(3 \text{ [\Omega]}) = (1 \text{ [A]})(3 \text{ [V]}) \Rightarrow P_{dis, 3 \text{ [\Omega]}} = 3 \text{ [W]}$$

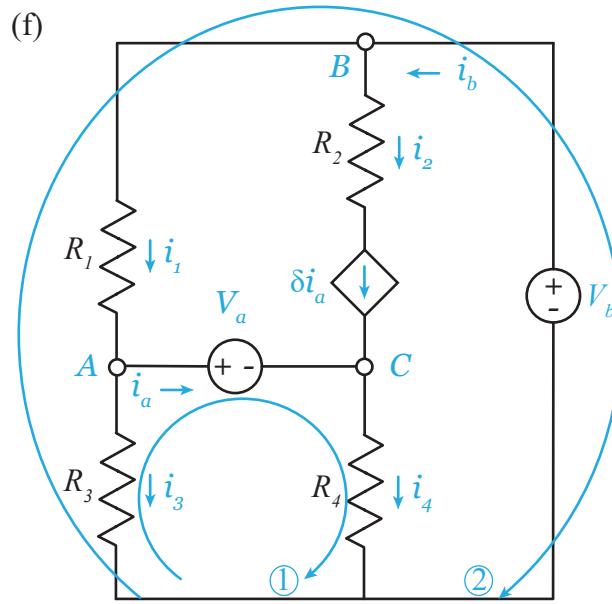Part (f):

We want to put the currents in terms of system variables, i.e. resistances and sources. The first step is to apply KCL at nodes A , B and C .



Starting at node A :

$$i_1 = i_a + i_3$$

On to node B :

$$i_b = i_1 + i_2$$

On to node C , recognizing $i_2 = \delta i_a$:

$$i_2 + i_a = i_4 \implies i_a(\delta + 1) = i_4$$

Thus, we have the current in relation to one another, however, not in terms of the sources. We will select two loops that do not contain a dependent source, ① and ②. Around the first loop:

$$-i_3 R_3 + V_a + i_4 R_4 = 0$$

Around the second loop:

$$-i_3 R_3 - i_1 R_1 + V_b = 0$$

Thus, we have enough independent equations to solve each current, as well as i_b .