

# Chapter 7 - Energy Storage Elements

## Lecture 23

### Sections 7.5-7.7

## MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department  
University of Pittsburgh



# Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Analyze the behavior of an inductor as a function of time
- ▶ Construct an expression for the behavior of inductors connected in series and parallel

## Learning Objectives

### 7.5 Inductors


### 7.6 Energy Stored in Inductors

### 7.7 Series and Parallel Inductors
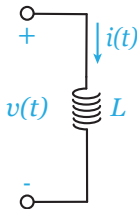
### Summary



- ▶ A conductor is schematically shown as follows:



- ▶ An insulated wire is wrapped around a magnetic core
- ▶ Energy is stored in the generated magnetic field

- ▶ The strength of the magnetic field is proportional to  $N$  - the number of turns of the wire
- ▶ The inductance  $L$  has units of a henry [H]



- ▶ The voltage potential across the inductor is a function of  $L$  and  $i(t)$

$$v(t) = L \frac{di(t)}{dt}$$

- ▶ Thus, the current flowing through an inductor is

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

- ▶ For the time interval  $-\infty < t \leq 0$

$$i(t) = i(t_0) + \frac{1}{L} \int_0^t v(\tau) d\tau$$

- ▶ It is noted that since  $i(t)$  is bounded,  $v(t)$  must be continuous



- ▶ If we compare the constitutive equations for a capacitor and inductor:

$$i(t) = C \frac{d}{dt} v(t)$$


$$v(t) = L \frac{d}{dt} i(t)$$

- ▶ These equations, coupled with Ohm's law, gives a complete description of the passive devices covered in this course


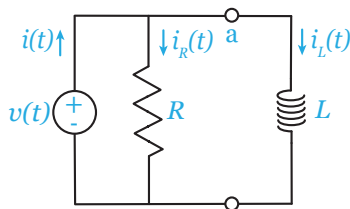
# Example #1

- The input to the circuit is  $v(t)=4\exp(-20t)$  [V] for  $t > 0$ . The output current is  $i(t)=-1.2\exp(-20t)-1.5$  [A] for  $t > 0$ . The initial inductor current is  $i_L(0)=-3.5$  [A]. Determine the inductance  $L$  and resistance  $R$  of the circuit.



## Learning Objectives

### 7.5 Inductors

### 7.6 Energy Stored in Inductors

### 7.7 Series and Parallel Inductors

## Summary



# Example #1

Chapter 7 - Energy  
Storage Elements

MEMS 0031

Learning Objectives

**7.5 Inductors**

7.6 Energy Stored  
in Inductors

7.7 Series and  
Parallel Inductors

Summary



# Example #1

Chapter 7 - Energy  
Storage Elements

MEMS 0031

Learning Objectives

**7.5 Inductors**

7.6 Energy Stored  
in Inductors

7.7 Series and  
Parallel Inductors

Summary





# Energy Stored in an Inductor

- ▶ Recall energy is the time integral of power. Power is expressed as

$$P(t) = v(t)i(t)$$

- ▶ Substituting in  $v(t)$  for an inductor

$$P(t) = \left( L \frac{di(t)}{dt} \right) i(t)$$

- ▶ The energy in an inductor is then

$$\begin{aligned} E_I &= \int_{t_0}^t P(\tau) d\tau = L \int_{t_0}^t \frac{di(\tau)}{d\tau} i(\tau) d\tau \\ &= L \int_{t_0}^t i(\tau) di(\tau) = \frac{L}{2} \left( i^2(t) - i^2(t_0) \right) \\ \therefore E_I(t) &= \frac{Li^2(t)}{2} \end{aligned}$$



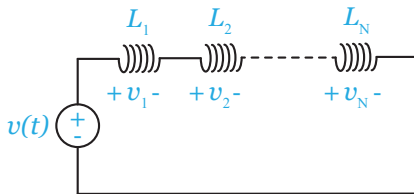
## Example #2

- Find the power and energy stored in a 0.1 [H] inductor given  $i(t)=20(t)\exp(-2t)$  [A] and  $v(t)=2\exp(-2t)(1-2t)$  [V] for  $t \geq 0$ , if  $i(t)=0$  for  $t < 0$




- Consider the following. What is the equivalent inductance?


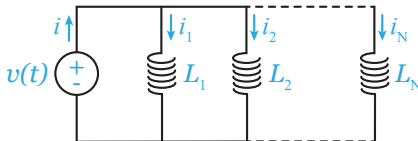
# Inductors in Parallel

- Consider the following. What is the equivalent inductance?



## Learning Objectives

### 7.5 Inductors

### 7.6 Energy Stored in Inductors


### 7.7 Series and Parallel Inductors

## Summary



## Example #3

- Determine the equivalent inductance

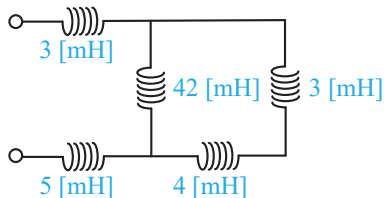

### Learning Objectives

#### 7.5 Inductors

#### 7.6 Energy Stored in Inductors

#### 7.7 Series and Parallel Inductors

### Summary



At the end of the lecture, students should be able to:

- ▶ Analyze the behavior of an inductor as a function of time
  - ▶ The voltage potential across an inductor is the inductance (ability to store charge) times the time rate of change of current running through the inductor
- ▶ Construct an expression for the behavior of inductors connected in series and parallel
  - ▶ Inductors in series sum arithmetically; an equivalent inductance of inductors in parallel is the reciprocal of the sum of the reciprocals of the individual inductances



# Suggested Problems

- ▶ 7.5-1, 7.5-2, 7.5-3, 7.5-4, 7.5-6, 7.5-12, 7.5-13,  
7.5-14, 7.6-1, 7.6-2, 7.7-1, 7.7-3, 7.7-5, 7.7-7, 7.7-10

