

MEMS 0031 - Electrical Circuits

Quiz #3


Assigned: June 4th, 2020

Due: June 7th, 2020, 9:00 pm

Name: _____

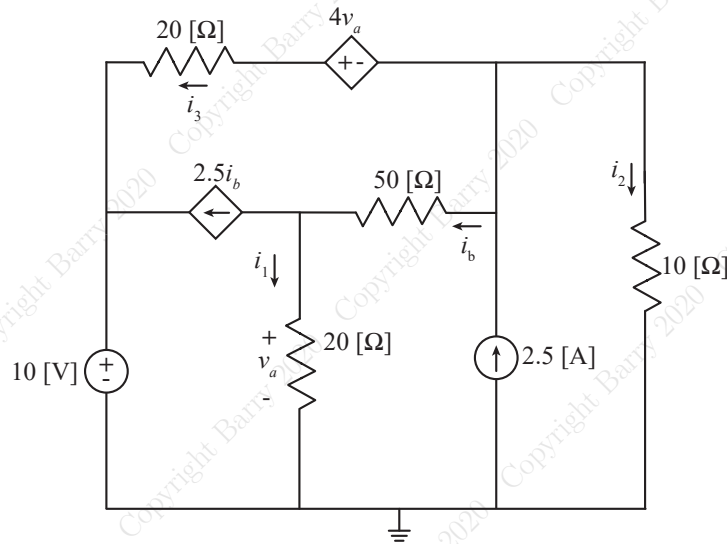Problem #1

Using Node Voltage Analysis, determine the branch currents i_1 through i_3 , and i_b .



Academic Integrity Statement:

I hereby attest that I have received no assistance (from a friend, from another student, from an on-line resource, such as Chegg, etc.), and that I have provided no assistance to another student, during this exam. All the work presented within is solely my own work.

Signature: _____

Date: _____