

Chapter 1 - Electric Circuit Variables

Lecture 1

Sections 1.2-1.5

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



- ▶ The following scheme will be used within our notes:
 1. **Bold** words are definitions
 2. *Italic* words or letters represent variables
 3. Underlined words or phrases represent a law, theorem and/or hypothesis
- ▶ Each section (number and title) is displayed on the right navigation pane, following our text
- ▶ Important equations will be boxed

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



Student Learning Objectives

Chapter 1 - Electric
Circuit Variables

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Understand the concept and formulation of charge and current
- ▶ Understand the concept and formulation of voltage
- ▶ Recognize and understand active and passive sign conventions
- ▶ Understand and apply the formulation of power
- ▶ Understand and apply the conservation of energy

[Learning Objectives](#)

[1.3 Systems of Units](#)

[1.2 Electric Circuits and Current](#)

[1.4 Voltage](#)

[1.5 Power and Energy](#)

[Summary](#)



- The units we will use in this course are as follows:

Quantity	Name	Formula	Symbol
Time	second		s
Electric Current	Ampere		A
Frequency	Hertz	s^{-1}	Hz
Energy or Work	Joule	N-m	J
Power	Watt	J/s	W
Electric Charge	Coulomb	A-s	C
Electric Potential	Volt	W/A	V
Electric Resistance	Ohm	V/A	Ω
Electric Conductance	Siemens	A/V	S
Electric Capacitance	Farad	C/V	F
Magnetic Flux	Weber	V-s	Wb
Inductance	Henry	Wb/A	H

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage


1.5 Power and
Energy

Summary



Electric Circuit

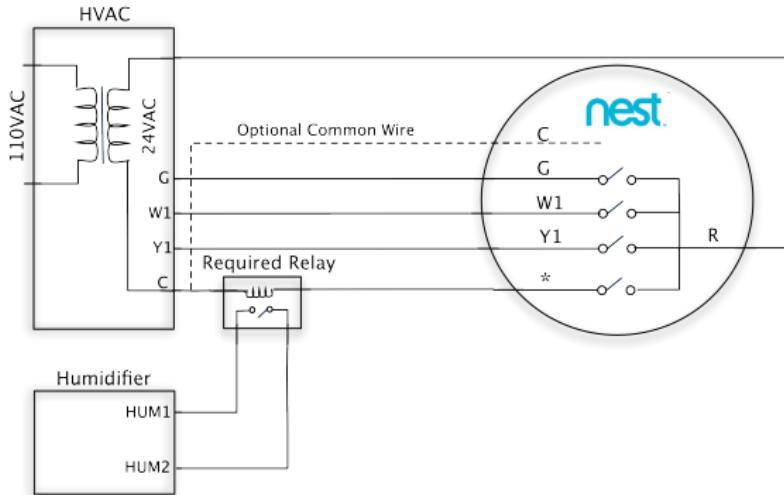- An **electric circuit**, or electric network, is an interconnection of electrical elements linked together in a closed path so that electric current may flow



Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



Charge and Current

- ▶ **Charge** (q , [C] (Coulomb), [A-s]) is the “quantity” of electricity, i.e. electrons, responsible for electrical phenomena

$$q(t) = \int_{-\infty}^t i d\tau = q(0) + \int_0^t i d\tau$$

- ▶ **Current** (i , [A], [C/s]) is the time rate of flow of charge past a point

$$i = \frac{dq}{dt}$$

- ▶ Current must be conserved! Charge carriers cannot be created nor destroyed.

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



Example #1

- ▶ For $t < 0$, no charge exists at the terminal of a device. At $t = 0$, a 5 [A] current begins to flow into the device.
- ▶ Determine:
 1. The charge accumulated for $t > 0$
 2. If the current stopped after 10 [s], how much charge has accumulated?
- ▶ Solution:

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage


1.5 Power and
Energy

Summary



Current in an Element

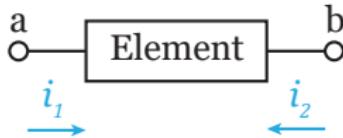- ▶ **Current** has direction and magnitude - it is a vector - and can exist in, or through, an element
- ▶ The direction is indicated by either \rightarrow , \leftarrow , \uparrow or \downarrow , and the magnitude is represented by a variable i_1 , i_2 , etc. The units are assumed [A] unless otherwise noted.
- ▶ Consider a circuit element that exists between nodes a and b, carrying current i_1



- ▶ Based upon the opposing direction of i_1 and i_2 , we can say:

$$i_1 = -i_2$$




Voltage in an Element

- ▶ **Voltage** (V , [V]) is a potential that drives a current across or through an element
- ▶ The voltage across an element, ΔV , is the work (w) required to move a unit positive charge (q) from the $-$ to the $+$ terminal

$$V = \frac{dw}{dq}$$

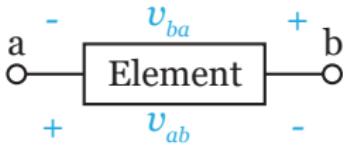- ▶ Note: our unit charge in this convention is positive, although an electron has a negative charge (Thanks Ben Franklin)



- ▶ We first have to define a consistent convention based on the direction of current through, and direction of a voltage potential across, an element
- ▶ The **Passive Sign Convention** refers to an element that is a **Power Sink**
- ▶ The **Active Sign Convention** refers to an element that is a **Power Source**
- ▶ Let us look at each of these conventions individually

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage


1.5 Power and
Energy

Summary



Passive Sign Convection

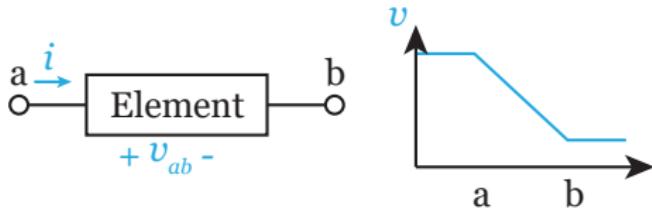- ▶ the **Passive Sign Convention** (PSC) means the circuit component is dissipating power within the circuit - if current is conserved, a decrease in power manifests through a decrease in potential
- ▶ Therefore, a passive component is decreasing the potential, i.e. voltage, of the charge carries
- ▶ The PSC is depicted as follows:



Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits and Current

1.4 Voltage


1.5 Power and Energy

Summary



Active Sign Convention

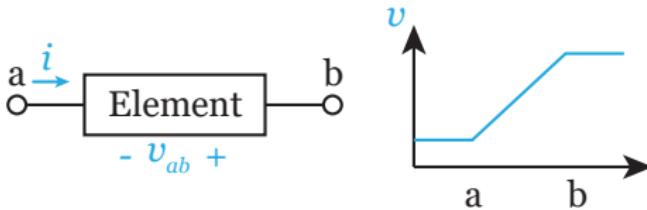- ▶ The **Active Sign Convention** (ASC) means the circuit component is providing energy to the circuit - if current is conserved, an increase in power manifests through an increase in potential
- ▶ Therefore, an active component is increasing the potential, i.e. voltage, of the charge carries
- ▶ The ASC is depicted as follows:



Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits and Current

1.4 Voltage

1.5 Power and Energy





Summary



Example #2

- ▶ For the four circuits shown, determine if they are active (i.e. a source), or passive (i.e. a sink):

- i)
- ii)
- iii)
- iv)

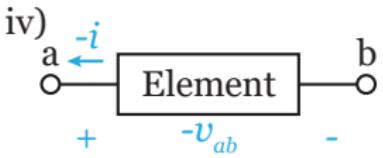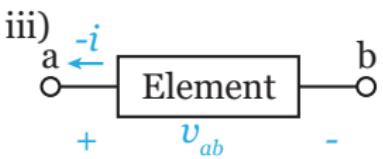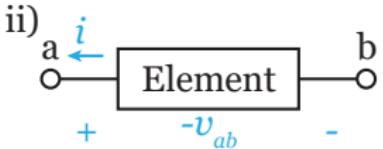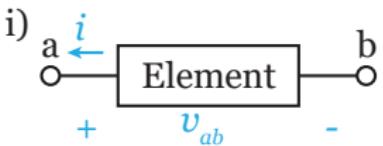

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits and Current

1.4 Voltage

1.5 Power and Energy

Summary



- ▶ **Power** (P , [W]) is the time rate of expending or absorbing energy (work)

$$P = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = Vi$$

- ▶ To determine the work of an element (either dissipated or supplied)

$$w = \int_{t_1}^{t_2} P d\tau$$

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



Example #3

- ▶ Assume the current into the terminal of an element is $20e^{-5,000t}$ [A] and the voltage across the element is $10e^{-5,000t}$ [kV] for $t \geq 0$
- ▶ Determine
 1. The power supplied to the element at 1 [ms]
 2. The energy delivered to the element
- ▶ Solution:

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage


1.5 Power and
Energy

Summary



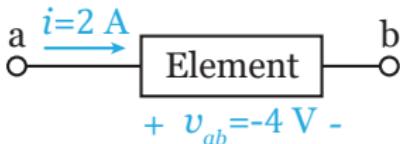Example #4

- ▶ Given the element below, determine
 1. The power dissipated
 2. The power supplied
 3. If this is a source or sink



- ▶ Solution:

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



Conservation of Power

- ▶ The **Conservation of Energy**, or **Conservation of Electrical Power**, states the power dissipated must be equal to the power supplied:

$$P_{\text{supplied}} = P_{\text{dissipated}}$$

- ▶ The circuit cannot supply more energy than it is dissipating, nor can it dissipate more energy than is supplied

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy


Summary



Example #5

- ▶ Using the passive sign convention, determine if the circuit obeys **conservation of energy**

	[V]	[A]
a	120	-10
b	120	9
c	10	10
d	10	1
e	-10	-9
f	-100	5
g	120	4
h	-220	-5

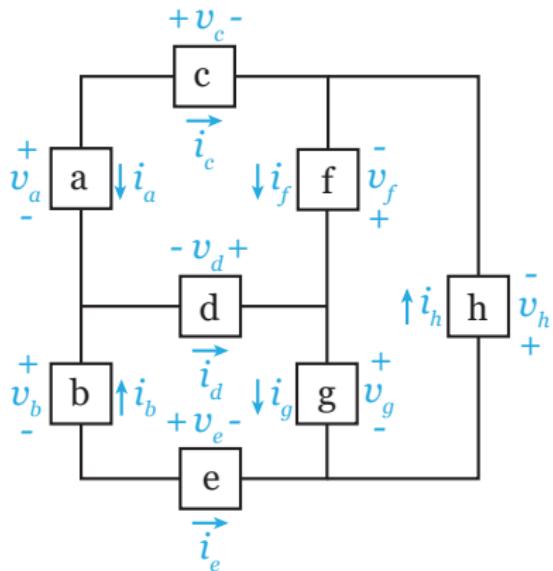

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits and Current

1.4 Voltage


1.5 Power and Energy

Summary



Example #5

► Solution:

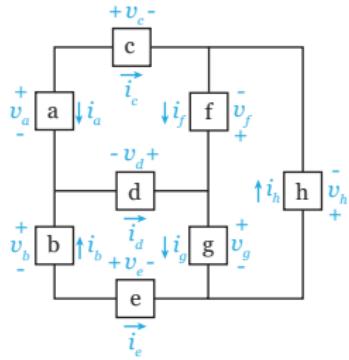

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage


1.5 Power and
Energy

Summary



Example #5

► Solution:

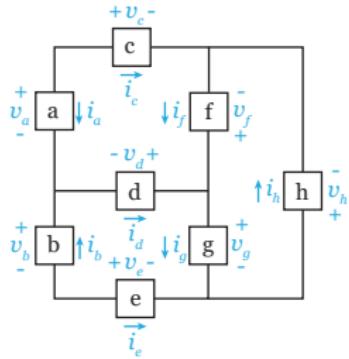

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary



Student Learning Objectives

Chapter 1 - Electric Circuit Variables

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Understand the concept and formulation of charge and current
 - ▶ Electric charge is the time-integral of electric current. Current is the flow of charge carriers (i.e. electrons) per unit time.
- ▶ Understand the concept and formulation of voltage
 - ▶ Voltage is a potential that is able to drive current through an element.
- ▶ Recognize and understand active and passive sign conventions
 - ▶ An active element is supplying power to the circuit - the potential is increasing as current runs through the device. The opposite for a passive element.

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits and Current

1.4 Voltage

1.5 Power and Energy

Summary



Student Learning Objectives

Chapter 1 - Electric Circuit Variables

MEMS 0031

- ▶ Understand and apply the formulation of power
 - ▶ Power is the time-rate of supplying or dissipating energy. Power is simply the voltage potential across an element times the current running through it.
- ▶ Understand and apply the conservation of energy
 - ▶ Energy can neither be created nor destroyed. The amount of energy supplied to a circuit is equal to the amount of energy dissipated by a circuit.

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits and Current

1.4 Voltage

1.5 Power and Energy

Summary



Suggested Problems

Chapter 1 - Electric
Circuit Variables

MEMS 0031

- ▶ 1.2-3, 1.2-5, 1.3-4, 1.5-1, 1.5-2, 1.7-3

Learning Objectives

1.3 Systems of Units

1.2 Electric Circuits
and Current

1.4 Voltage

1.5 Power and
Energy

Summary

