

## Quiz #2


**Assigned: May 29<sup>st</sup>, 2020**

**Due: May 31<sup>st</sup>, 2020, 9:00 pm**

Name: \_\_\_\_\_

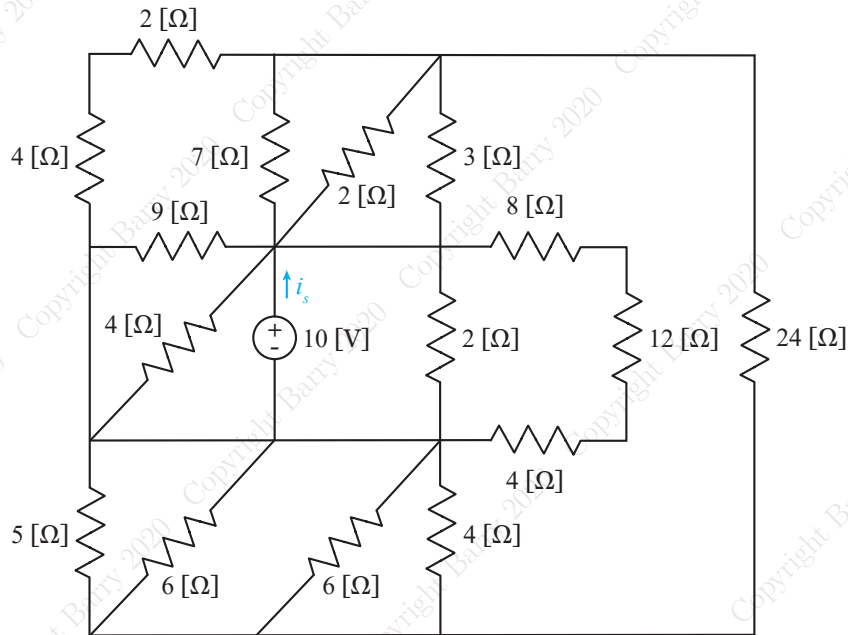
## Problem #1

Using series and parallel resistors, determine the source current  $i_s$ . Note: KVL and KCL are not needed. The use of KVL and KCL will result in your answer being marked incorrect.



Thee 8, 12 and 4  $[\Omega]$  resistors are in series, yielding an equivalent of  $R_{eq,1} = 24 [\Omega]$ . This equivalence is in parallel with the 2  $[\Omega]$  resistor, yielding an equivalence of
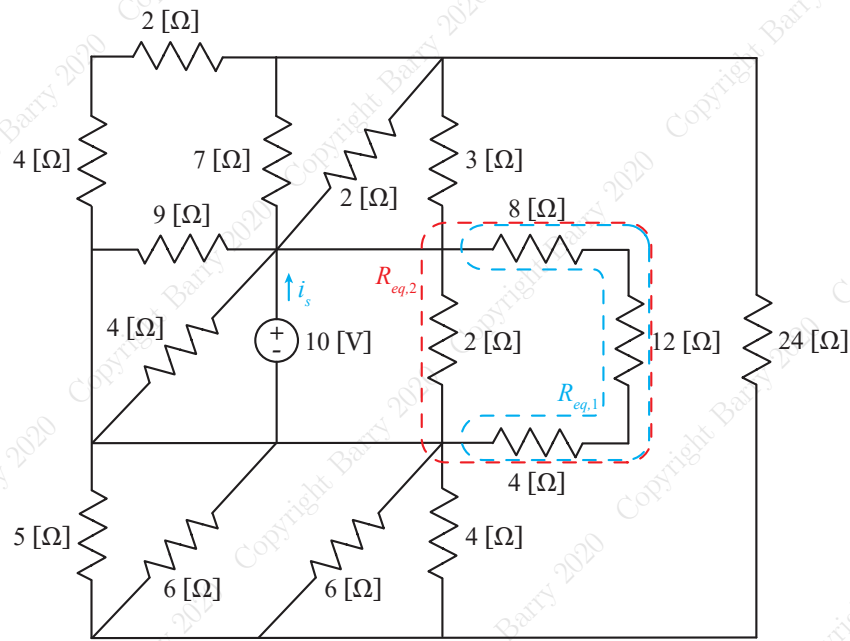
$$R_{eq,2} = \frac{(24 [\Omega])(2 [\Omega])}{(24 + 2) [\Omega]} = 24/13 [\Omega]$$




The 2 and 4  $[\Omega]$  resistors are in series, yielding an equivalent of  $R_{eq,3}=6$   $[\Omega]$ . The 7, 2 and 3  $[\Omega]$  resistors are in parallel, yielding an equivalent resistance of

$$R_{eq,4} = \left( \frac{1}{7[\Omega]} + \frac{1}{2[\Omega]} + \frac{1}{3[\Omega]} \right)^{-1} = 42/41 [\Omega]$$


The 5, 6, 6, and 4  $[\Omega]$  resistors are in parallel, yielding an equivalent resistance of
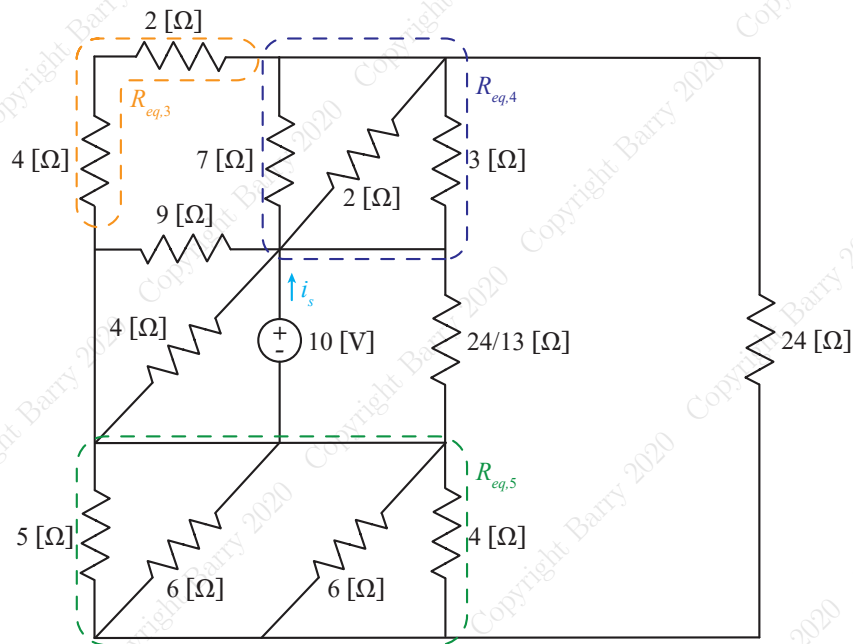
$$R_{eq,5} = \left( \frac{1}{5[\Omega]} + \frac{1}{6[\Omega]} + \frac{1}{6[\Omega]} + \frac{1}{4[\Omega]} \right)^{-1} = 60/47 [\Omega]$$




The 9 and 4  $[\Omega]$  resistor are in parallel, yielding an equivalence of
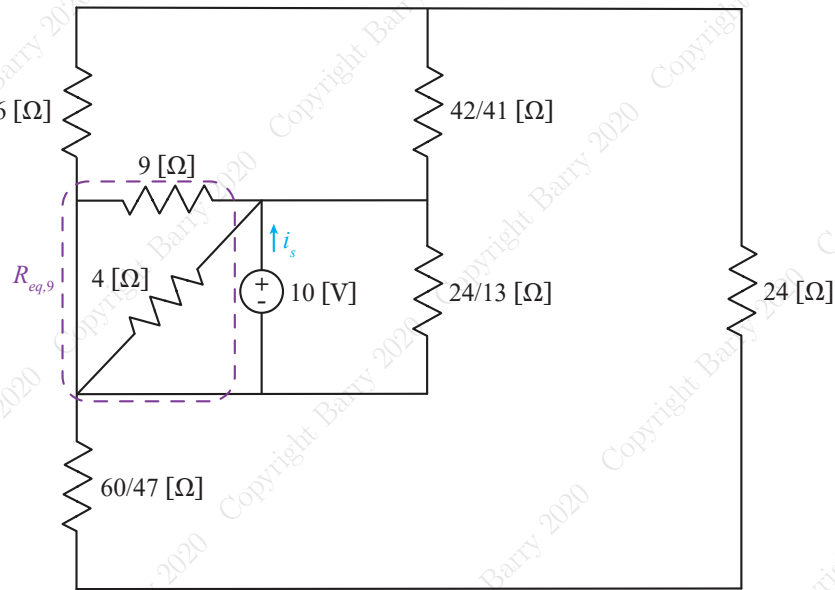
$$R_{eq,9} = \frac{(9[\Omega])(4[\Omega])}{(9+4)[\Omega]} = 36/13 [\Omega]$$




We recognize the  $60/47$  and  $24$   $[\Omega]$  resistors are in series, which yields an equivalence of  $R_{eq,10} = 1,188/47$   $[\Omega]$ . We also recognize the  $36/13$  and  $24/13$   $[\Omega]$  resistors exist in parallel, yielding an equivalence of
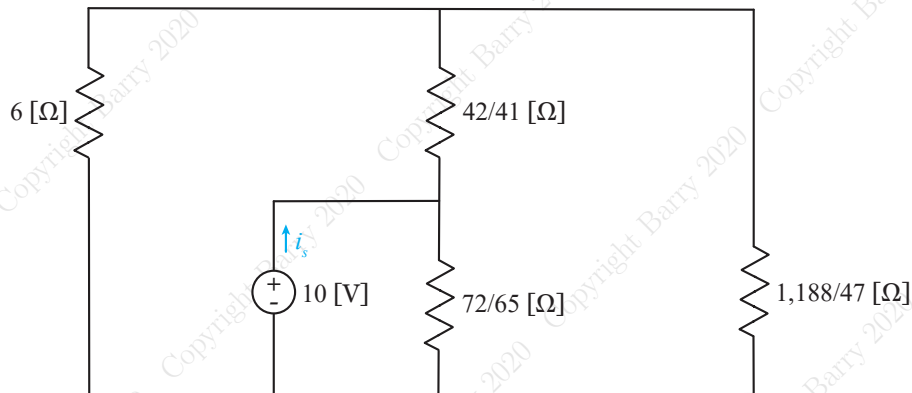
$$R_{eq,11} = \frac{(36/13 [\Omega])(24/13 [\Omega])}{(36/13 + 24/13) [\Omega]} = 72/65 [\Omega]$$




The  $6$  and  $1,188/47$   $[\Omega]$  resistors are in parallel, yielding an equivalence of
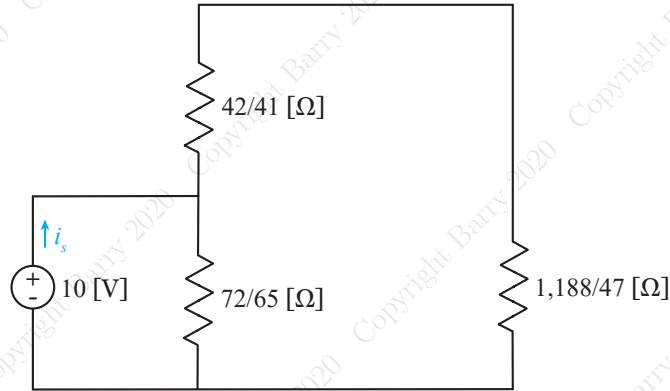
$$R_{eq,12} = \frac{(6 [\Omega])(1,188/47 [\Omega])}{(6 + 1,188/47) [\Omega]} = 1,188/245 [\Omega]$$



The  $42/41$  and  $1,188/47 \text{ } [\Omega]$  resistors are in series, with an equivalent resistance of  $R_{eq,13} = 58,998/10,045 \text{ } [\Omega]$ . This equivalence is in parallel with the  $72/65 \text{ } [\Omega]$  resistor, which yields an equivalence of
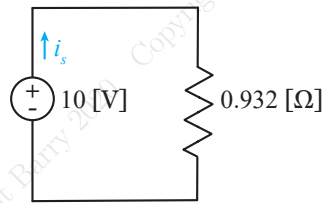
$$R_{eq,14} = \frac{(42/41 \text{ } [\Omega])(58,998/10,045 \text{ } [\Omega])}{(42/41 + 58,998/10,045) \text{ } [\Omega]} \approx 0.932 \text{ } [\Omega]$$



Thus, the source current is

$$i = \frac{10 \text{ } [V]}{0.932 \text{ } [\Omega]} = 10.73 \text{ } [A]$$