

Homework #4


MEMS 0031 - Electrical Circuits

Assigned: May 28th, 2020

Due: June 3rd, 2020 at 11:59 pm

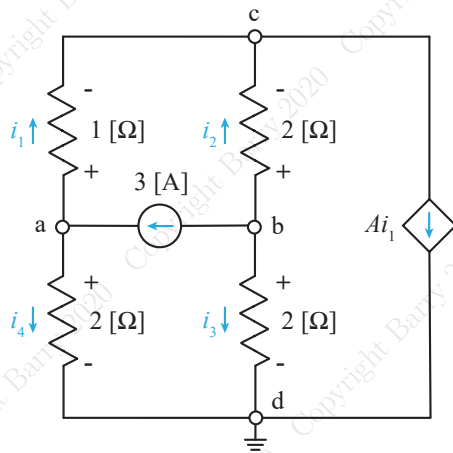Problem #1

Using Node Voltage Analysis (NVA), determine the currents i_1 and i_2 , and the voltages at nodes a, b and c, given $A = 4$. Note: if you use any other method than NVA to determine branch currents, i.e. currents through the resistors, your answer will be marked incorrect.



Step 1: Assign nodes (N) and leg currents to all branches/elements: $N = 4$ and we define i_3 and i_4 as shown.

Step 2: Assign voltage potential consistent with PSC: Voltage potentials assigned as shown.

Step 3: $N-1$ KCL equations, applied at non-zero nodes:

KCL at node a:

$$i_1 + i_4 = 3 \text{ [A]}$$

KCL at node b:

$$i_2 + i_3 = -3 \text{ [A]}$$

KCL at node c:

$$i_1 + i_2 = 4i_1 \implies -3i_1 + i_2 = 0$$

Step 4: Apply Ohm's law in terms of node voltages:

KCL at node a:

$$\frac{V_a - V_c}{1 [\Omega]} + \frac{V_a}{2 [\Omega]} = 3 \text{ [A]} \implies 3V_a - 2V_c = 6 \text{ [A]} \quad (1)$$

KCL at node b:

$$\frac{V_b - V_c}{2 [\Omega]} + \frac{V_b}{2 [\Omega]} = -3 \text{ [A]} \implies 2V_b - V_c = -6 \text{ [A]} \quad (2)$$

KCL at node c:

$$-3 \left(\frac{V_a - V_c}{1 [\Omega]} \right) + \frac{V_b - V_c}{2 [\Omega]} = 0 \implies -6V_a + V_b + 5V_c = 0 \quad (3)$$


Putting eqns. 1-3 in matrix form:

$$\begin{bmatrix} 3 & 0 & -2 \\ 0 & 2 & -1 \\ -6 & 1 & 5 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 6 \\ -6 \\ 0 \end{bmatrix} \implies \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 8.6 \\ 2 \\ 10 \end{bmatrix}$$

Units are taken as [V]. The calculation of the currents is provided in the MATLAB script.

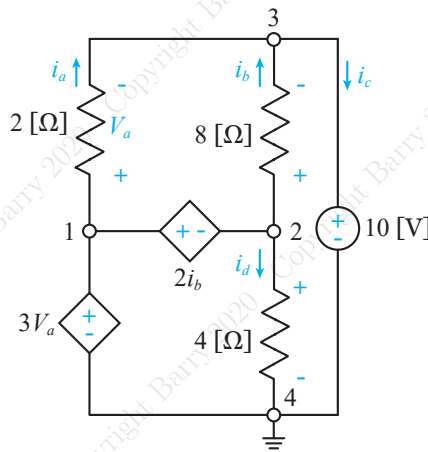Problem #2

Using Node Voltage Analysis (NVA), determine the currents i_b and i_c , and the voltages potential V_a . Note: if you use any other method than NVA to determine branch currents, i.e. currents through the resistors, your answer will be marked incorrect.



Step 1: Assign nodes (N) and leg currents to all branches/elements: $N = 4$ and we define i_a through i_d as shown.

Step 2: Assign voltage potential consistent with PSC: Voltage potentials assigned as shown.

Step 3: $N - 1 - \#VS$ KCL equations: We need zero KCL equations. The voltages sources provide enough information to solve the problem. We will apply Step 4 as we formulate our VS expressions in terms of node voltages:

VCES:

$$V_1 = 3V_a \Rightarrow V_1 = 3(V_1 - V_3) \Rightarrow 2V_1 - 3V_3 = 0 \quad (4)$$

CCVS:

$$V_1 - V_2 = 2i_b \Rightarrow V_1 - V_2 = 2\left(\frac{V_2 - V_3}{8[\Omega]}\right) \Rightarrow 4V_1 - 5V_2 + V_3 = 0 \quad (5)$$

Independent VS:

$$V_3 = 10 [\text{V}] \quad (6)$$


Putting eqns. 4-6 in matrix form:

$$\begin{bmatrix} 2 & 0 & -3 \\ 4 & -5 & 1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 10 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 14 \\ 10 \end{bmatrix}$$

Units are taken as [V]. The calculation of the currents is provided in the MATLAB script.

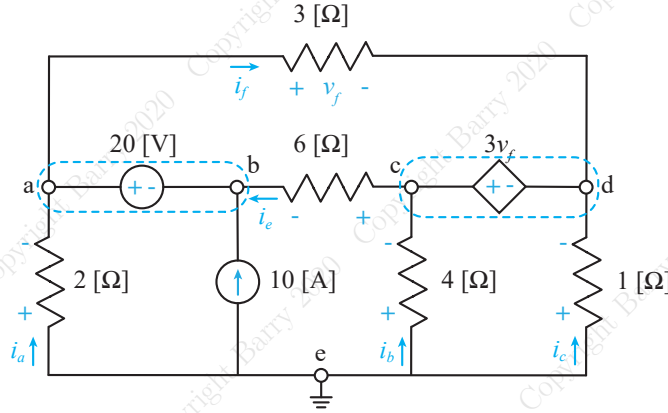Problem #3

Using Node Voltage Analysis (NVA), determine the currents i_a through i_g . Note: if you use any other method than NVA to determine branch currents, i.e. currents through the resistors, your answer will be marked incorrect.



Step 1: Assign nodes (N) and leg currents to all branches/elements: $N = 5$ and we have our branch currents already defined as shown.

Step 2: Assign voltage potential consistent with PSC: Voltage potentials assigned as shown.

Step 3: $N - 1 - \#VS$ KCL equations, applied at non-zero nodes:

Left supernode equation:

$$V_a - V_b = 20 \quad (7)$$

Right supernode equation:

$$V_c - V_d = 3V_f \implies V_c - V_d - 3(V_a - V_d) = 0 \implies 3V_a - V_c - 2V_d = 0 \quad (8)$$

KCL at left supernode:

$$i_a + 10 \text{ [A]} + i_e - i_f = 0$$

KCL at right supernode:

$$i_b + i_c + i_f - i_e = 0$$

Step 4: Apply Ohm's law in terms of node voltages:

KCL at left supernode:

$$\frac{0 - V_a}{2 \text{ [}\Omega\text{]}} + \frac{V_c - V_b}{6 \text{ [}\Omega\text{]}} - \frac{V_a - V_d}{3 \text{ [}\Omega\text{]}} = -10 \text{ [A]} \quad (9)$$

KCL at right supernode:

$$\frac{0 - V_c}{4 \text{ [}\Omega\text{]}} + \frac{0 - V_d}{1 \text{ [}\Omega\text{]}} + \frac{V_a - V_d}{3 \text{ [}\Omega\text{]}} - \frac{V_c - V_b}{6 \text{ [}\Omega\text{]}} = 0 \quad (10)$$


Putting eqns. 7-10 in matrix form:

$$\begin{bmatrix} 1 & -1 & 0 & 0 \\ 3 & 0 & -1 & -2 \\ -5/6 & -1/6 & 1/6 & 1/3 \\ 1/3 & 1/6 & -5/12 & -4/3 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ -10 \\ 0 \end{bmatrix} \implies \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 26.6667 \\ 6.6667 \\ 173.3333 \\ -46.6667 \end{bmatrix}$$

Units are taken as [V]. The calculation of the currents is provided in the MATLAB script.

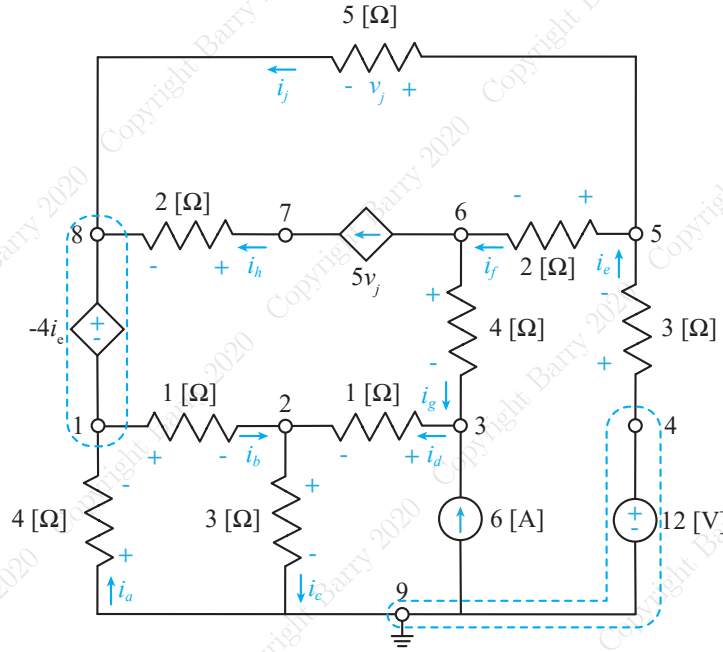Problem #4

Using Node Voltage Analysis (NVA), determine the currents i_a through i_j . Note: if you use any other method than NVA to determine branch currents, i.e. currents through the resistors, your answer will be marked incorrect.



Step 1: Assign nodes (N) and leg currents to all branches/elements: $N = 9$ and we have our branch currents already defined as shown.

Step 2: Assign voltage potential consistent with PSC: Voltage potentials assigned as shown.

Step 3: $N - 1 - \#VS$ KCL equations, applied at non-zero nodes:

Supernode:

$$V_8 - V_1 = -4i_e$$

Independent VS:

$$V_4 = 12 [V]$$

KCL at supernode:

$$i_a - i_b + i_h + i_j = 0$$

KCL at node 2:

$$i_b - i_c + i_d = 0$$

KCL at node 3:

$$-i_d + i_g = -6 [A]$$

KCL at node 5:

$$i_e - i_f - i_j = 0$$

KCL at node 6:

$$i_f - i_g - 5v_j = 0$$

KCL at node 7:

$$5v_j - i_h = 0$$

Step 4: Apply Ohm's law in terms of node voltages:

Supernode:

$$V_8 - V_1 = -4 \left(\frac{V_4 - V_5}{3} \right) \Rightarrow 3V_1 - 4V_4 + 4V_5 - 3V_8 = 0 \quad (11)$$

Independent VS:

$$V_4 = 12 \quad (12)$$

KCL at supernode:

$$\frac{0 - V_1}{4 [\Omega]} - \frac{V_1 - V_2}{1 [\Omega]} + \frac{V_7 - V_8}{2 [\Omega]} + \frac{V_5 - V_8}{5 [\Omega]} = 0 \Rightarrow -25V_1 + 20V_2 + 4V_5 + 10V_7 - 14V_8 = 0 \quad (13)$$

KCL at node 2:

$$\frac{V_1 - V_2}{1 [\Omega]} - \frac{V_2}{3 [\Omega]} + \frac{V_3 - V_2}{1 [\Omega]} = 0 \Rightarrow 3V_1 - 7V_2 + 3V_3 = 0 \quad (14)$$

KCL at node 3:

$$-\frac{V_3 - V_2}{1 [\Omega]} + \frac{V_6 - V_3}{4 [\Omega]} = -6 [A] \Rightarrow 4V_2 - 5V_3 + V_6 = -24 \quad (15)$$

KCL at node 5:

$$\frac{V_4 - V_5}{3[\Omega]} - \frac{V_5 - V_6}{2[\Omega]} - \frac{V_5 - V_8}{5[\Omega]} = 0 \implies 10V_4 - 31V_5 + 15V_6 + 6V_8 = 0 \quad (16)$$

KCL at node 6:

$$\frac{V_5 - V_6}{2[\Omega]} - \frac{V_6 - V_3}{4[\Omega]} - 5(V_5 - V_8) = 0 \implies V_3 - 18V_5 - 3V_6 + 20V_8 = 0 \quad (17)$$

KCL at node 7:

$$5(V_5 - V_8) - \frac{V_7 - V_8}{2[\Omega]} = 0 \implies 10V_5 - V_7 - 9V_8 = 0 \quad (18)$$


Putting eqns. 11-18 in matrix form:

$$\begin{bmatrix} 3 & 0 & 0 & -4 & 4 & 0 & 0 & -3 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ -25 & 20 & 0 & 0 & 4 & 0 & 10 & -14 \\ 3 & -7 & 3 & 0 & 0 & 0 & 0 & 0 \\ 0 & 4 & -5 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 10 & -31 & 15 & 0 & 6 \\ 0 & 0 & 1 & 0 & -18 & -3 & 0 & 20 \\ 0 & 0 & 0 & 0 & 10 & 0 & -1 & -9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \\ 0 \\ -24 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Units are taken as [V]. The calculation of the currents is provided in the MATLAB script.

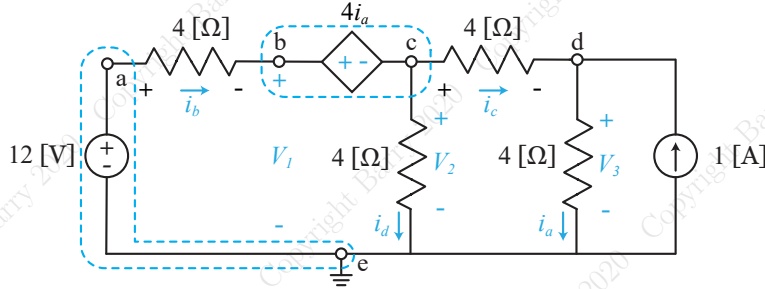Problem #5

Using Node Voltage Analysis (NVA), determine the voltage potentials V_1 through V_3 . Note: if you use any other method than NVA to determine branch currents, i.e. currents through the resistors, your answer will be marked incorrect.



Step 1: Assign nodes (N) and leg currents to all branches/elements: $N = 5$ and we have our branch currents already defined as shown.

Step 2: Assign voltage potential consistent with PSC: Voltage potentials assigned as shown.

Step 3: $N - 1 - \#VS$ KCL equations, applied at non-zero nodes:

Independent VS:

$$V_a = 12 \text{ [V]} \quad (19)$$

Supernode:

$$V_b - V_c = 4i_a$$

KCL at supernode:

$$i_b - i_c - i_d = 0$$

KCL at node d:

$$i_c - i_a = -1 \text{ [A]}$$

Step 4: Apply Ohm's law in terms of node voltages:

Supernode:

$$V_b - V_c - 4\left(\frac{V_d}{4}\right) = 0 \implies V_b - V_c - V_d = 0 \quad (20)$$

KCL at supernode:

$$\frac{V_a - V_b}{4[\Omega]} - \frac{V_c - V_d}{4[\Omega]} - \frac{V_c}{4[\Omega]} = 0 \implies V_a - V_b - 2V_c + V_d = 0 \quad (21)$$

KCL at node d:

$$\frac{V_c - V_d}{4[\Omega]} - \frac{V_d}{4[\Omega]} = -1 \text{ [A]} \implies V_c - 2V_d = -4 \quad (22)$$


Putting eqns. 19-22 in matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & -1 & -1 \\ 1 & -1 & -2 & 1 \\ 0 & 0 & 1 & -2 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \\ -4 \end{bmatrix} \implies \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 12 \\ 8 \\ 4 \\ 4 \end{bmatrix}$$

Units are taken as [V]. The calculation of the currents is provided in the MATLAB script.

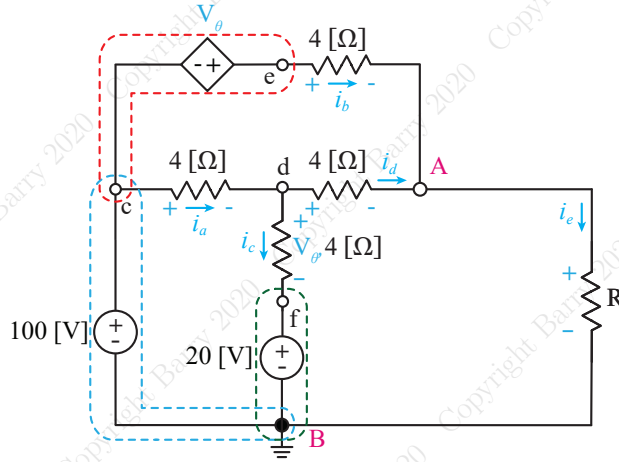Problem #6

Using Node Voltage Analysis (NVA), determine the voltage potential V_θ given $R = 6\ [\Omega]$. Note: if you use any other method than NVA to determine branch currents, i.e. currents through the resistors, your answer will be marked incorrect.



Step 1: Assign nodes (N) and leg currents to all branches/elements: $N = 6$ and we have our branch currents already defined as shown.

Step 2: Assign voltage potential consistent with PSC: Voltage potentials assigned as shown.

Step 3: $N - 1 - \#VS$ KCL equations, applied at non-zero nodes. Note: the combination of the 100 [V] source and VCVS consolidates to one VS equation, and thus we will apply KCL at two non-source nodes.

Independent 100 [V] VS:

$$V_c = 100\text{ [V]} \quad (23)$$

Independent 20 [V] VS:

$$V_f = 20\text{ [V]} \quad (24)$$

VCVS:

$$V_e - V_c = V_\theta$$

KCL at node d:

$$i_a - i_c - i_d = 0$$

KCL at node a:

$$i_b + i_d - i_e = 0$$

Step 4: Apply Ohm's law in terms of node voltages:

VCVS:

$$V_e - V_c = V_d - V_f \implies V_c + V_d - V_e - V_f = 0 \quad (25)$$

KCL at node d:

$$\frac{V_c - V_d}{4\ [\Omega]} - \frac{V_d - V_f}{4\ [\Omega]} - \frac{V_d - V_a}{4\ [\Omega]} = 0 \implies V_a + V_c - 3V_d + V_f = 0 \quad (26)$$

KCL at node a:

$$\frac{V_e - V_a}{4\ [\Omega]} + \frac{V_d - V_a}{4\ [\Omega]} - \frac{V_a}{6\ [\Omega]} = 0 \implies -8V_a + 3V_d + 3V_e = 0 \quad (27)$$

Putting eqns. 23-27 in matrix form:

$$\begin{bmatrix} 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & -1 & -1 \\ 1 & 1 & -3 & 0 & 1 \\ -8 & 0 & 3 & 3 & 0 \end{bmatrix} \begin{bmatrix} V_a \\ V_c \\ V_d \\ V_e \\ V_f \end{bmatrix} = \begin{bmatrix} 100 \\ 20 \\ 0 \\ 0 \\ 0 \end{bmatrix} \implies \begin{bmatrix} V_a \\ V_c \\ V_d \\ V_e \\ V_f \end{bmatrix} \neq \begin{bmatrix} 100 \\ 20 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$