


Homework #7

MEMS 0031 - Electrical Circuits

Assigned: June 29th, 2020
Due: July 1st, 2020 at 11:59 pm

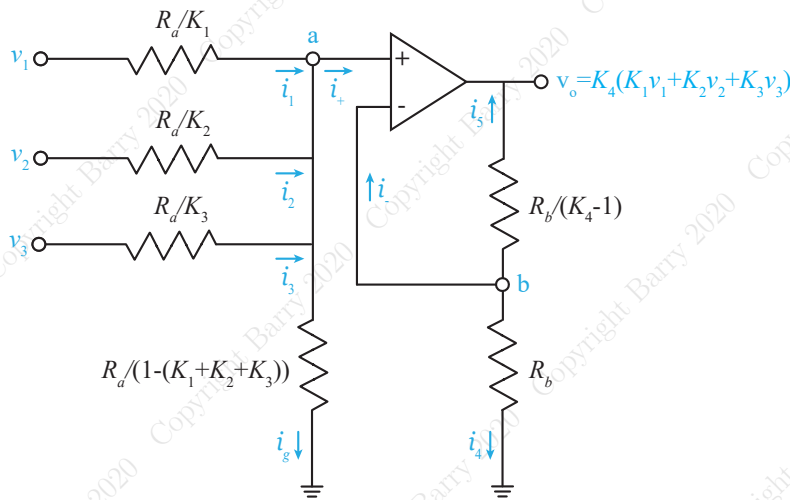Problem #1

Given the summing Op-amp as shown in Fig. 6.5-1 e) of the text, prove the equation as provided in Lecture 20 on Slide 8 is equal to that provided in the text.



We start by applying KCL at node a:

$$i_1 + i_2 + i_3 = 0 + i_g$$

Applying Ohm's law:

$$\frac{V_1 - V_a}{\left(\frac{R_a}{K_1}\right)} + \frac{V_2 - V_a}{\left(\frac{R_a}{K_2}\right)} + \frac{V_3 - V_a}{\left(\frac{R_a}{K_3}\right)} = \frac{V_a}{\left(\frac{R_a}{1 - (K_1 + K_2 + K_3)}\right)}$$

Grouping like terms:

$$V_1 \left(\frac{K_1}{R_a}\right) + V_2 \left(\frac{K_2}{R_a}\right) + V_3 \left(\frac{K_3}{R_a}\right) = V_a \left\{ \left(\frac{1 - (K_1 + K_2 + K_3)}{R_a}\right) + \frac{K_1}{R_a} + \frac{K_2}{R_a} + \frac{K_3}{R_a} \right\}$$

$$\Rightarrow V_1 \left(\frac{K_1}{R_a}\right) + V_2 \left(\frac{K_2}{R_a}\right) + V_3 \left(\frac{K_3}{R_a}\right) = \frac{V_a}{R_a} \Rightarrow V_a = (V_1 K_1 + V_2 K_2 + V_3 K_3)$$

Knowing $V_b = V_a$, we can then apply KCL at node b:

$$0 = i_4 + i_5$$

Applying Ohm's law:

$$\frac{V_b}{R_b} + \frac{V_b - V_o}{\left(\frac{R_b}{K_4 - 1}\right)} = 0$$

Solving for V_o

$$\frac{V_b}{R_b} + \frac{V_b(K_4 - 1)}{R_b} = \frac{V_o(K_4 - 1)}{R_b} \Rightarrow V_o = V_b \left(\frac{K_4}{K_4 - 1} \right)$$

Substituting in the expression for V_a for V_b

$$V_o = (V_1 K_1 + V_2 K_2 + V_3 K_3) \left(\frac{K_4}{K_4 - 1} \right) = V_1 \left(\frac{K_1 K_4}{K_4 - 1} \right) + V_2 \left(\frac{K_2 K_4}{K_4 - 1} \right) + V_3 \left(\frac{K_3 K_4}{K_4 - 1} \right)$$

For there to be equal weights on the inputs, with a value of unity, we need

$$\frac{K_1 K_4}{K_4 - 1} = \frac{K_2 K_4}{K_4 - 1} = \frac{K_3 K_4}{K_4 - 1} = 1$$

Therefore, we shall set $K_1 = K_2 = K_3 = K$. Additionally, we need the weight on R_b between node b and the output to be n the number of input

$$\frac{1}{K_4 - 1} = n \Rightarrow K_4 = 1 + \frac{1}{n}$$

Therefore,

$$\frac{K K_4}{K_4 - 1} = 1 \Rightarrow \frac{K \left(1 + \frac{1}{n} \right)}{\left(1 + \frac{1}{n} \right) - 1} = 1 \Rightarrow n K \left(1 + \frac{1}{n} \right) = 1 \Rightarrow K(n + 1) = 1 \Rightarrow K = \frac{1}{n + 1}$$

The selection of K and K_4 then yields

$$\frac{K K_4}{K_4 - 1} = \frac{\left(\frac{1}{n + 1} \right) \left(1 + \frac{1}{n} \right)}{\left(1 + \frac{1}{n} \right) - 1} = \frac{n}{n + 1} + \frac{1}{n + 1}$$

This expression is equal to 1 for all n . Thus, the output is

$$V_o = V_1 + V_2 + V_3$$

We can verify our solution using the Symbolics toolbox in MATLAB:

```
clear all
close all
clc

syms i1 i2 i3 i4 i5 ig V1 V2 V3 Va Vo Ra Rb K K1 K2 K3 K4 n

% Making assumptions to reduce the expression
K = 1/(n+1);
K1 = K;
K2 = K;
K3 = K;
K4 = (1 + (1/n));

% Branch currents for KCL at a
i1 = (V1 - Va)/(Ra/K1);
i2 = (V2 - Va)/(Ra/K2);
i3 = (V3 - Va)/(Ra/K3);
ig = Va/(Ra/(1 - (K1 + K2 + K3)));

KCL_a = i1 + i2 + i3 == ig;

Va_expr = expand(solve(KCL_a, Va));
```

```

% We know Vb = Va. Branch currents for KCL at b
i4 = Va_expr/Rb;
i5 = (Va_expr - Vo)/(Rb/(K4-1));


KCL_b = i4 + i5 == 0;

Vo_expr = expand(solve(KCL_b,Vo));
disp(Vo_expr)

```

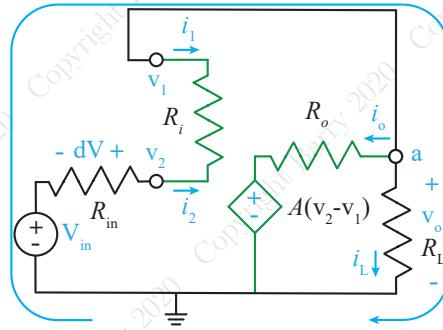Problem #2

Reconsider Example #2 from Lecture 21. Repeat this problem to determine the ratio of the output voltage to the input voltage, V_o/V_{in} , using the given resistances and gain, however, you are to *not* ignore i_1 .



Start by applying KCL at node as:

$$i_1 + i_o + i_L = 0$$

Apply Ohm's law, assuming the internal resistance R_i of the device behaves linearly:

$$\frac{V_o - V_{in}}{R_{in} + R_i} + \frac{V_o - A(V_2 - V_1)}{R_o} + \frac{V_o}{R_L} = 0$$

Solving in terms of $\Delta V = V_2 - V_1$

$$\Delta V = \frac{V_o}{A} \left(1 + \frac{R_o}{R_L} \right) + \frac{R_o(V_o - V_{in})}{R_{in} + R_i}$$

Applying KVL around the loop:

$$-V_{in} - dV + \Delta V + V_o = 0 \implies -V_{in} - \left(\frac{V_o - V_{in}}{R_{in} + R_i} \right) R_{in} + \frac{V_o}{A} \left(1 + \frac{R_o}{R_L} \right) + \frac{R_o(V_o - V_{in})}{R_{in} + R_i} + V_o = 0$$

Solving for the ratio V_o/V_{in} :

$$\frac{V_o}{V_{in}} = \frac{\left(1 - \frac{R_{in}}{R_{in} + R_i} + \frac{R_o}{R_{in} + R_i} \right)}{\left(1 - \frac{R_{in}}{R_{in} + R_i} + \frac{1}{A} \left(1 + \frac{R_o}{R_L} \right) + \frac{R_o}{R_{in} + R_i} \right)}$$

Substituting in $R_{in}=1$ [kΩ], $R_L=10$ [kΩ], $R_i=100$ [kΩ], $R_o=100$ [Ω] and $A=10^5$

$$\frac{V_o}{V_{in}} = 0.999989$$

In comparison to our previous solution, this reflects a 9.08e-6 percent difference.