

Chapter 6 - The Operational Amplifier

Lecture 18

Sections 6.2-6.3

Learning Objectives

6.2 The Operational
Amplifier

6.3 The Ideal
Op-amp

Summary

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 6 - The
Operational
Amplifier

At the end of the lecture, students should be able to:

- ▶ Understand the operation of an operational amplifier
- ▶ Understand and apply the two main assumptions when modeling operational amplifiers, as well as the three requirements for an operational amplifier to operate in the linear range

MEMS 0031

Learning Objectives


6.2 The Operational Amplifier

6.3 The Ideal Op-amp

Summary



Op-amp

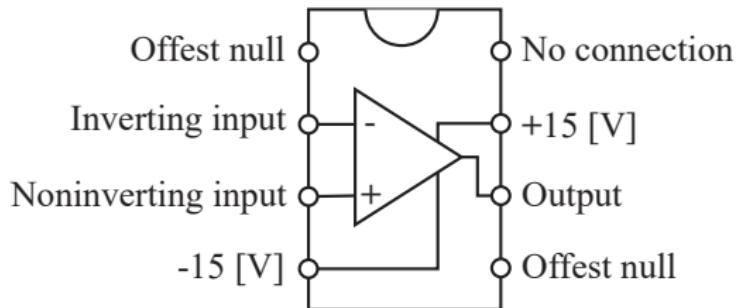

Learning Objectives

6.2 The Operational Amplifier

6.3 The Ideal Op-amp


Summary



Op-amp Anatomy

Chapter 6 - The
Operational
Amplifier

MEMS 0031

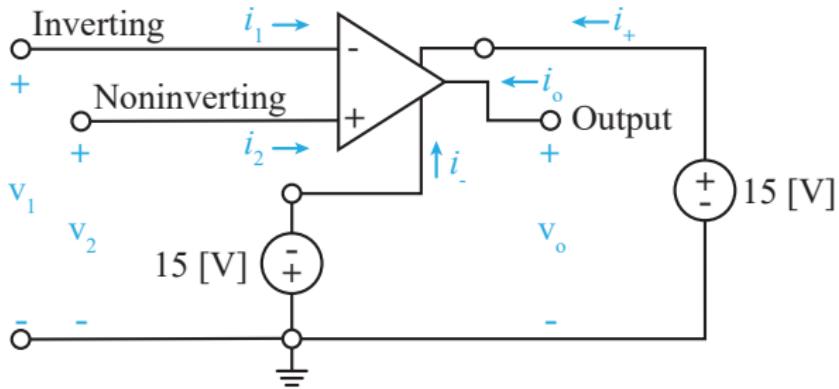

Learning Objectives


6.2 The Operational Amplifier

6.3 The Ideal Op-amp

Summary



Ideal Op-amp

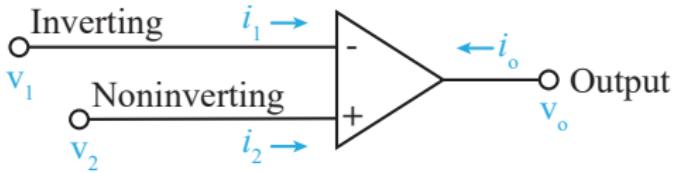

Learning Objectives

6.2 The Operational Amplifier

6.3 The Ideal Op-amp


Summary



Ideal Op-amp Cont'd

Chapter 6 - The
Operational
Amplifier

MEMS 0031

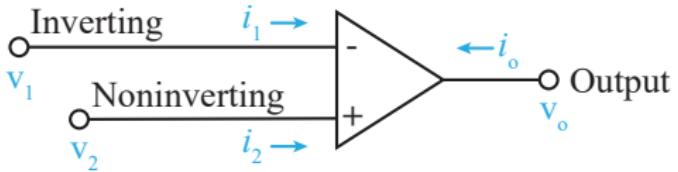

Learning Objectives

6.2 The Operational Amplifier


6.3 The Ideal Op-amp

Summary



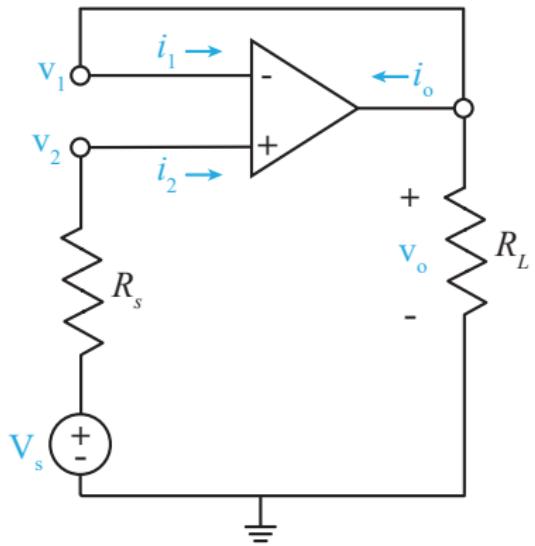Example #1

- Solve for v_o and i_o given $V_s=10$ [V] and $R_L=20$ [$k\Omega$]



Learning Objectives

6.2 The Operational Amplifier


6.3 The Ideal Op-amp

Summary



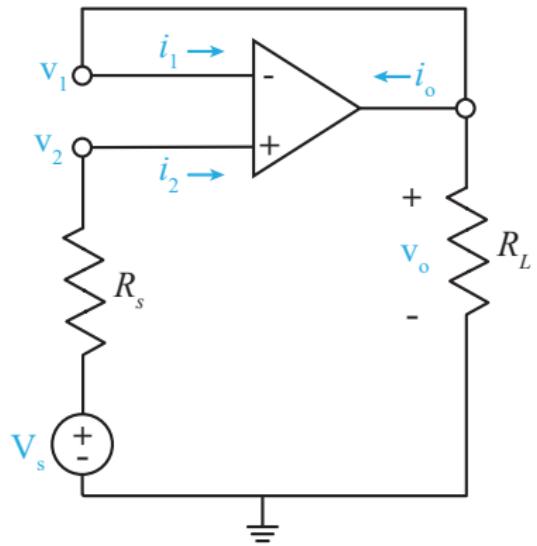Example #2

- Given $V_{sat}=14$ [V], $i_{sat}=2$ [mA] and SR=0.5 [V/ μ s], determine if the operation is ideal



Learning Objectives

6.2 The Operational Amplifier


6.3 The Ideal Op-amp

Summary



Example #3

- ▶ Find v_o , assuming ideal behavior

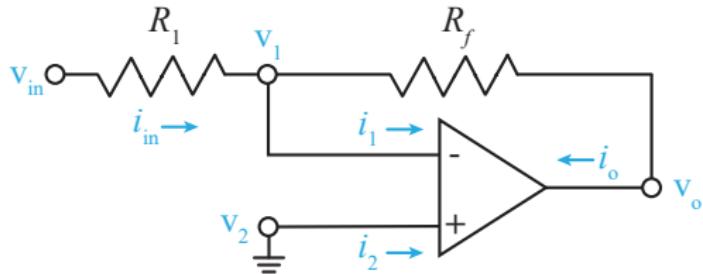

Learning Objectives

6.2 The Operational Amplifier


6.3 The Ideal Op-amp

Summary



Example #4

- ▶ Find v_o , assuming ideal behavior

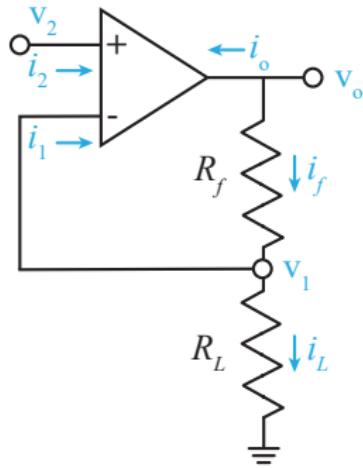

Learning Objectives

6.2 The Operational Amplifier

6.3 The Ideal Op-amp

Summary



Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Understand the operation of an operational amplifier
 - ▶ An Op-amp is able to manipulate an input signal (amplify or attenuate).
- ▶ Understand and apply the two main assumptions when modeling operational amplifiers, as well as the three requirements for an operational amplifier to operate in the linear range
 - ▶ It is assumed the input currents into the inverting and non-inverting terminals is zero, and that the potential at said terminals is the same. For linear behavior, the output voltage and current must be less than the saturation, and the time-rate-of-change of the output voltage must be less than the slew rate.



Suggested Problems

Chapter 6 - The
Operational
Amplifier

- ▶ 6.3-1, 6.3-2, 6.3-3, 6.3-6, 6.3-7, 6.3-8, 6.3-10, 6.3-15

MEMS 0031

Learning Objectives

6.2 The Operational
Amplifier

6.3 The Ideal
Op-amp

Summary

