

Chapter 2 - Circuit Elements

Lecture 2

Sections 2.1-2.5

Learning Objectives

2.1 Introduction

2.2 Engineering and
Linear Models

2.4 Resistors

2.5 Independent
Sources

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 2 - Circuit Elements

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Identify active and passive circuit elements
- ▶ Understand the constraints for an element to be considered linear
- ▶ Understand the formulation of electrical resistance and how it relates to resistors
- ▶ Understand and be able to apply Ohm's Law
- ▶ Calculate power dissipated in elements (Joule heating)
- ▶ Identify and verify ideal current and voltage source

Learning Objectives

2.1 Introduction

2.2 Engineering and Linear Models

2.4 Resistors

2.5 Independent Sources



Circuit Elements

Chapter 2 - Circuit
Elements

MEMS 0031

- ▶ There are many circuit elements we will analyze in this course, and they are broken down into two categories:

Passive Elements

- ▶ Resistors (R)
- ▶ Inductors (L)
- ▶ Capacitors (C)
- ▶ Diodes
- ▶ We will first focus our attention on resistors, and voltage and current sources

Active Elements

- ▶ Voltage sources
- ▶ Current sources
- ▶ Controlled sources
- ▶ Op-amps

Learning Objectives

2.1 Introduction

2.2 Engineering and Linear Models

2.4 Resistors

2.5 Independent Sources



- ▶ **Linear circuit** elements satisfy the properties of **superposition** and **homogeneity**, and exhibit linear behavior
- ▶ **Superposition** states that the total response of a component with multiple stimuli is the sum of the responses of individual stimuli acting on the component
- ▶ **Homogeneity** states the dimensions of each contributing term are consistent

Learning Objectives

2.1 Introduction

2.2 Engineering and Linear Models



2.4 Resistors

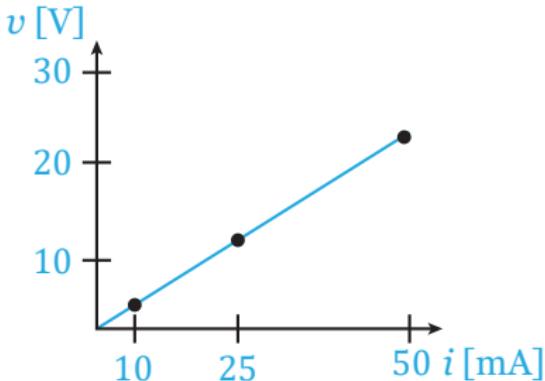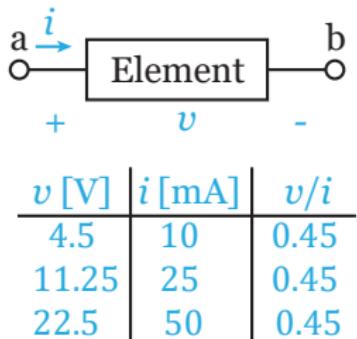2.5 Independent Sources



Linear Circuit Elements

- ▶ Is the element depicted below behaving linearly?




- ▶ What would non-linear behavior look like?



- ▶ **Resistance** (R , [Ω], [V/A]) is the physical property of an element or device that impedes the flow of current
- ▶ R expressed in terms of the electrical resistivity ρ , which is dependent upon the valence electrons and free electrons, length of the element L , and cross-sectional area of the element A such that

$$R = \frac{\rho L}{A}$$

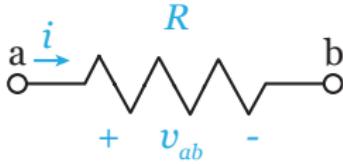- ▶ The resistor will be represented by the following symbol



Example #1

- ▶ What is the resistance of a 30 [m] length of copper ($\rho=1.68 \cdot 10^{-8}$ [$\Omega \cdot \text{m}$]) wire, if the wire were:
 - ▶ 12-gage ($A=3.31$ [mm^2])
 - ▶ 10-gage ($A=5.26$ [mm^2])

Learning Objectives

2.1 Introduction

2.2 Engineering and
Linear Models


2.4 Resistors

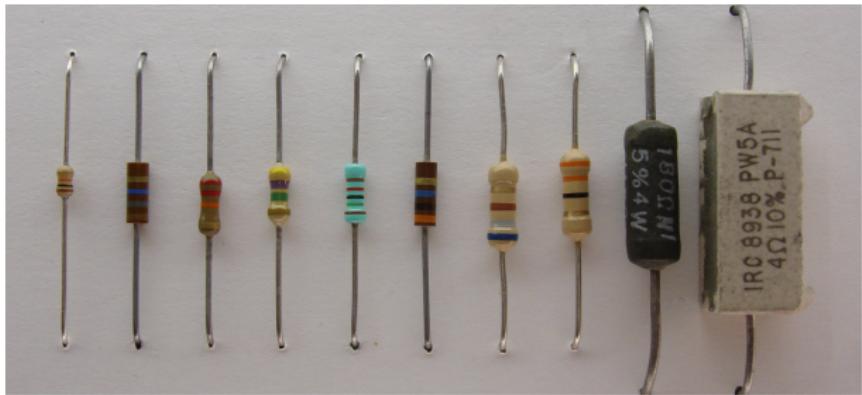2.5 Independent
Sources



Resistors

- ▶ Resistors come in all shapes and sizes, and are made from a variety of material to satisfy design requirements




- ▶ Resistors have voltage and current ratings, and subsequently maximum power ratings
- ▶ The **bands** tell you the nominal resistance value and tolerance



- ▶ **Ohm's law** states the voltage potential across a resistor is proportional to the current through it, and is related by the constant of proportionality, resistance, such that

$$V = iR$$

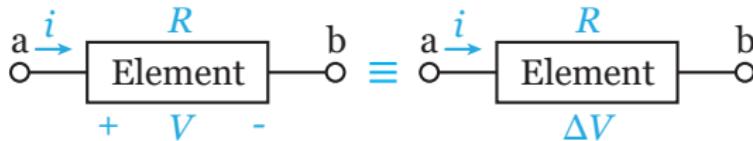- ▶ That is, a potential is needed across an element to drive a current through it:




- ▶ This is commonly expressed as:

$$\Delta V = iR$$

- ▶ We will drop the ΔV convention, and indicate the potential via + and - signs



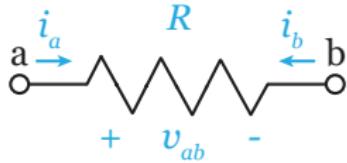- ▶ Consider the resistor shown below, with a voltage potential v_{ab} driving i_a through R



- ▶ We can express i_a in terms of i_b

$$i_a = -i_b$$

- ▶ Applying Ohm's law consistent with the PSC:

$$V_{ab} = i_a R$$

- ▶ Substituting $-i_b$ for i_a

$$V_{ab} = -i_b R \implies V_{ba} = i_b R$$

- ▶ The potential is dependent upon the direction of i



Linear Resistors

- ▶ An important assumption made is that the resistor is operating within a region of linear behavior
- ▶ Linearity implies $v = f(i) = iR$, that is voltage will be a function of current, where R is independent of both voltage and current
- ▶ Given an element with resistance R , and currents i_1 and i_2 flowing through the element, with corresponding voltages $V_1=Ri_1$ and $V_2=Ri_2$ imposed across the element to drive currents i_1 and i_2 , the total voltage applied would be:

$$V = R(i_1 + i_2) = V_1 + V_2$$

Learning Objectives

2.1 Introduction

2.2 Engineering and Linear Models

2.4 Resistors

2.5 Independent Sources



Power Dissipated

- ▶ The power dissipated by a resistor can be determined using Ohm's law. The potential is:

$$V = iR$$

We recall power is current times voltage

$$P = Vi$$

Substituting in V expressed by Ohm's law into the power equation

$$P = (iR)i = i^2 R$$

This is known as **Joule heating**, which is also expressed as

$$P = \frac{V^2}{R}$$

Learning Objectives

2.1 Introduction

2.2 Engineering and Linear Models


2.4 Resistors

2.5 Independent Sources



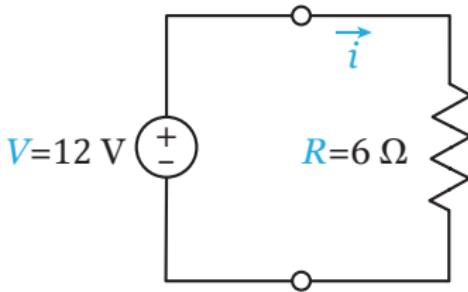Example #2

- ▶ Compute a) the current through the resistor and
b) the power dissipated by the resistor



Learning Objectives

2.1 Introduction

2.2 Engineering and Linear Models



2.4 Resistors

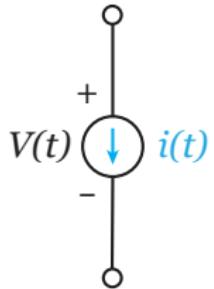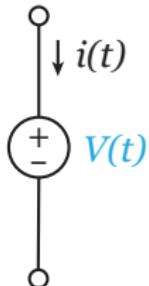2.5 Independent Sources



Independent Sources

- ▶ There are two types of independent sources



Learning Objectives

2.1 Introduction

2.2 Engineering and
Linear Models


2.4 Resistors

2.5 Independent
Sources



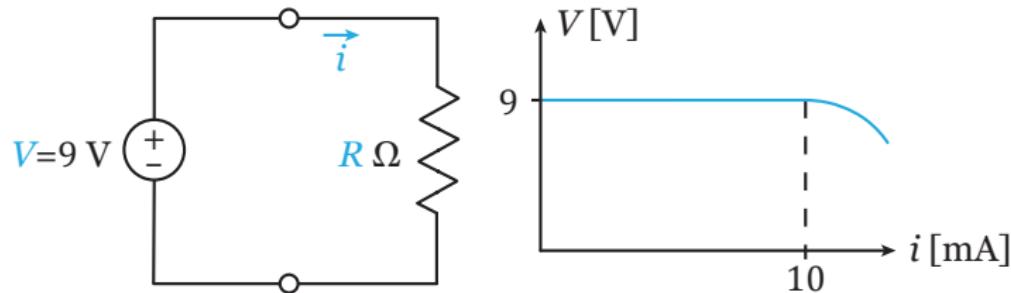Example #3

- Given the true power characteristics of a 9 [V] battery:



- If $R=100 \ [\Omega]$, does the voltage source behave ideally?
- If $R=1,000 \ [\Omega]$, does the voltage source behave ideally?

