


# Op-amps, Inductors and Capacitors Worksheet

MEMS 0031 - Electrical Circuits

June 24<sup>th</sup>, 2020
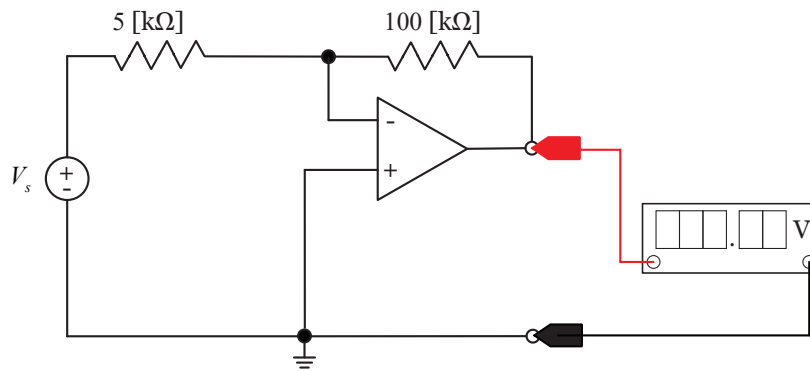
## Problem #1

Given the Op-amp shown below, and using the Finite Gain model, determine the ratio of the output to input voltages, given an input resistance of  $500 \text{ [k}\Omega\text{]}$ , an output resistance of  $5 \text{ [k}\Omega\text{]}$  and a gain of  $300,000$ .



## Problem #2

There are various devices that use capacitors as proximity switches. When the switch is activated, the button can be represented as a set of parallel capacitors; two capacitors in series, in parallel with the original capacitor. The capacitors in series are connected to a node that is connected to ground. Given the system below, where  $C = 25$  [pF] for all capacitors, determine the output voltage when the button is and is not activated.

