

MEMS 0031 - Electrical Circuits
Quiz #4

Name: _____

Problem #1

Determine the branch currents i_a , i_b and i_c using NVA.

