


# Op-amps, Inductors and Capacitors Worksheet

MEMS 0031 - Electrical Circuits

June 24<sup>th</sup>, 2020
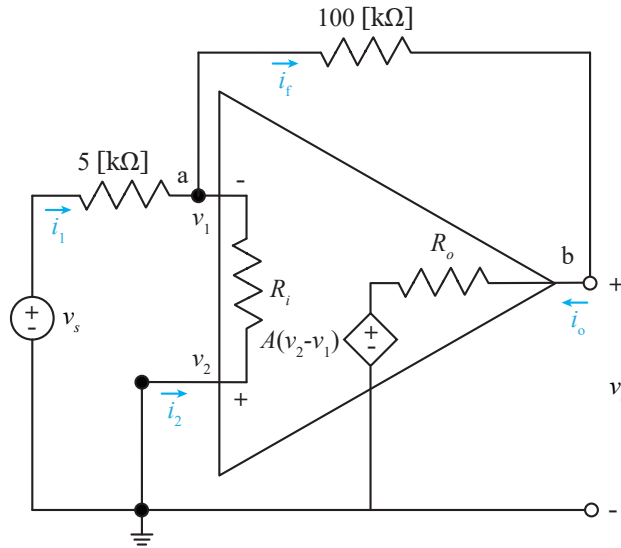
## Problem #1

Given the Op-amp shown below, and using the Finite Gain model, determine the ratio of the output to input voltages, given an input resistance of 500 [kΩ], an output resistance of 5 [kΩ] and a gain of 300,000. How does this compare to an ideal op-amp?



Let us start by constructing an equation that relates the input to output voltages, i.e. KCL at node a:

$$i_i + i_2 = i_f$$

We will denote the 5 [kΩ] resistor as  $R_s$  and the 100 [kΩ] resistor as  $R_f$ . Applying Ohm's law

$$\frac{V_s - V_a}{R_s} + \frac{V_2 - V_a}{R_i} = \frac{V_a - V_o}{R_f} \quad (1)$$

We need a second KCL equation to account for the VCCS - we will apply KCL at node b:

$$i_f = i_o$$

Applying Ohm's law to express this in terms of node voltages:

$$\frac{V_a - V_o}{R_f} = \frac{V_o - A(-V_a)}{R_o} \quad (2)$$

We have two equations and three unknowns, but recall we are interested in the quantity  $V_o/V_s$ , which consolidates two unknowns into one. Therefore, we will express eqn. 1 as:

$$V_a \underbrace{\left( \frac{1}{R_s} + \frac{1}{R_i} + \frac{1}{R_f} \right)}_{\text{term 1}} = V_s \underbrace{\frac{1}{R_s}}_{\text{term 2}} + V_o \underbrace{\frac{1}{R_f}}_{\text{term 3}} \quad (3)$$

Eqn. 2 can be expressed as:

$$V_a \underbrace{\left( \frac{1}{R_f} - \frac{A}{R_o} \right)}_{\text{term 4}} = V_o \underbrace{\left( \frac{1}{R_o} + \frac{1}{R_f} \right)}_{\text{term 5}} \quad (4)$$

Equating  $V_a$  to solve for the ratio of  $V_o/V_s$ :

$$\frac{V_o}{V_s} = \frac{\text{term 2}}{\left( \frac{(\text{term 5})(\text{term 1})}{\text{term 4}} \right) - \text{term 3}} = -19.9985$$

To treat this as an ideal op-amp, we would apply KCL at node a, not consider the current running through the internal resistor:


$$i_1 = i_f$$

In terms of node voltages:

$$\frac{V_s - \overset{0}{V_a}}{5 \text{ [k}\Omega\text{]}} = \frac{\overset{0}{V_a} - V_o}{100 \text{ [k}\Omega\text{]}} \implies \frac{V_o}{V_s} = -\frac{100 \text{ [k}\Omega\text{]}}{5 \text{ [k}\Omega\text{]}} = -20$$
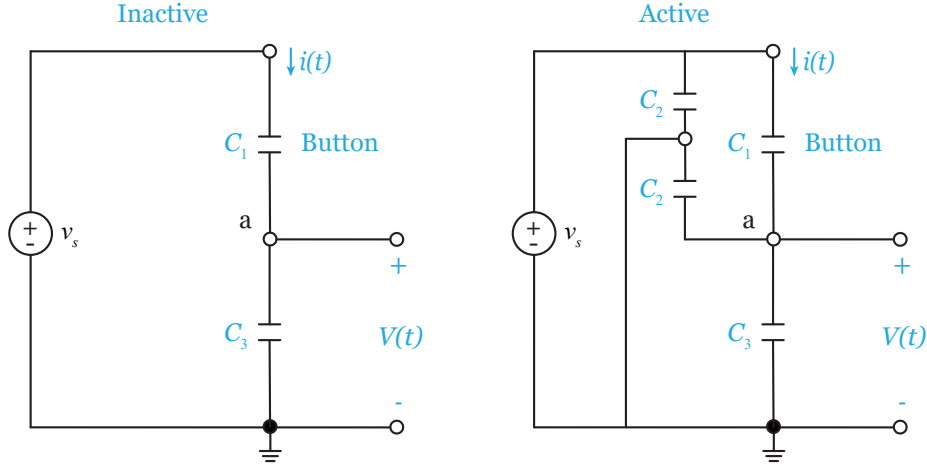
## Problem #2

There are various devices that use capacitors as proximity switches. When the switch is activated, the button can be represented as a set of parallel capacitors; two capacitors in series, in parallel with the original capacitor. The capacitors in series are connected to a node that is connected to ground. Given the system below, where  $C = 25$  [pF] for all capacitors, determine the output voltage when the button is and is not activated.



Let us consider the first situation when the button is inactive. The same current  $i(t)$  is running through both currents, so if we apply KCL at node a, and expressing the currents in terms of capacitance and time rate of change of voltage:

$$C_1 \frac{d(V_s - V(t))}{dt} = C_3 \frac{dV(t)}{dt}$$

Solving for the output voltage:

$$\frac{dV(t)}{dt} = \left( \frac{C_1}{C_1 + C_3} \right) \frac{dV_s}{dt}$$

Integrate with respect to time:

$$V(t) = \left( \frac{C_1}{C_1 + C_3} \right) V_s + V_o(t)$$

The leading coefficient of  $V_s$  is one-half. The initial voltage  $V_o(t)$  would be zero for steady-state operation. Therefore:

$$V(t) = 0.5V_s$$

Now, when the switch is activated, current has the ability to run through  $C_2$  and to ground, as well as  $C_1$  and  $C_3$ . Applying KCL at node a, and expressing the currents in terms of capacitance and time rate of change of voltage:

$$C_2 \frac{d(-V(t))}{dt} + C_1 \frac{d(V_s - V(t))}{dt} = C_3 \frac{dV(t)}{dt}$$

Solving for the output voltage:

$$\frac{dV(t)}{dt} = \left( \frac{C_1}{C_1 + C_2 + C_3} \right) \frac{dV_s}{dt}$$

Integrate with respect to time:

$$V(t) = \left( \frac{C_1}{C_1 + C_2 + C_3} \right) V_s + V_o(t)$$

The leading coefficient of  $V_s$  is one-third. The initial voltage  $V_o(t)$  would be zero for steady-state operation. Therefore:

$$V(t) = 0.3V_s$$