

Chapter 2 - Circuit Elements

Lecture 3

Sections 2.6-2.7

Learning Objectives

2.6 Meters

2.7 Dependent
Sources

Summary

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 2 - Circuit Elements

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Understand the underlying assumptions made when using voltmeters and ammeters
- ▶ Identify dependent sources and understand the four types (CCVS, VCVS, VCCS, CCCS) and their associated gains

[Learning Objectives](#)

[2.6 Meters](#)

[2.7 Dependent Sources](#)

[Summary](#)



Circuit Elements

- ▶ We don't always model voltage potential and currents, we measure them using **voltmeters** and **ammeters**, respectively
- ▶ Often times, these are one-in-the same and are referred to as a **multimeter**



Learning Objectives

2.6 Meters


2.7 Dependent Sources

Summary



Ammeter

- ▶ An **ammeter** measures current:

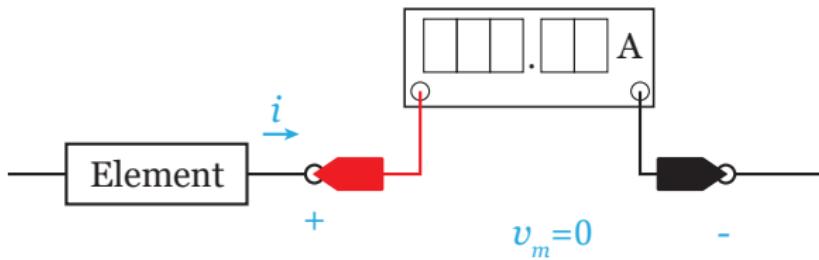

Learning Objectives

2.6 Meters


2.7 Dependent Sources

Summary



Voltmeter

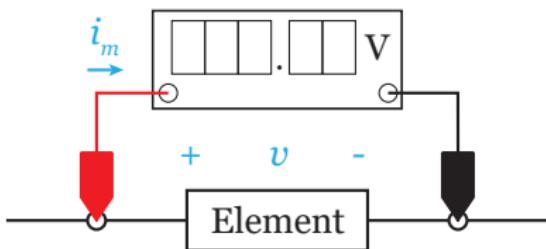- ▶ A **voltmeter** measures voltage potential:



Learning Objectives

2.6 Meters

2.7 Dependent Sources

Summary



Dependent Sources





- ▶ Current-Controlled Voltage Source (CCVS):
- ▶ Voltage-Controlled Voltage Source (VCVS):
- ▶ Voltage-Controlled Current Source (VCCS):
- ▶ Current-Controlled Current Source (CCCS):

Learning Objectives

2.6 Meters


2.7 Dependent Sources

Summary

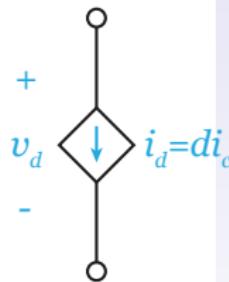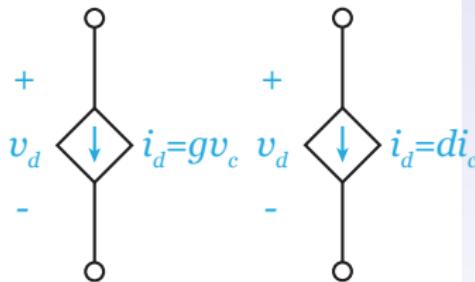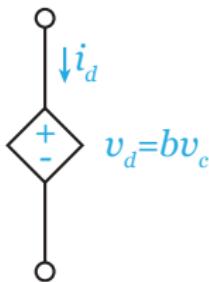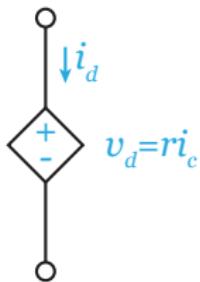

Example #1

- ▶ Determine the gain of the VCVS:

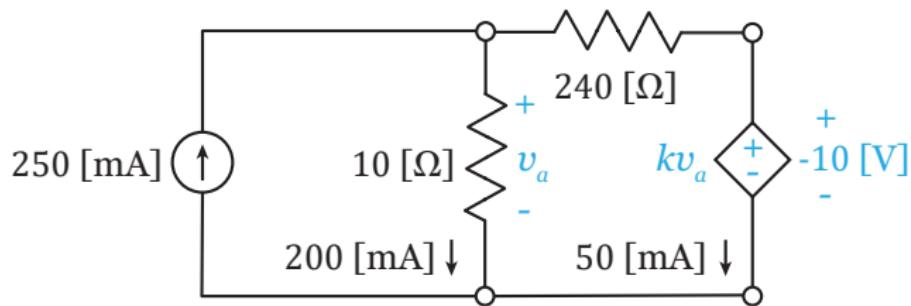

Learning Objectives

2.6 Meters


2.7 Dependent Sources

Summary



Example #2

- Determine the gain of the CCCS:

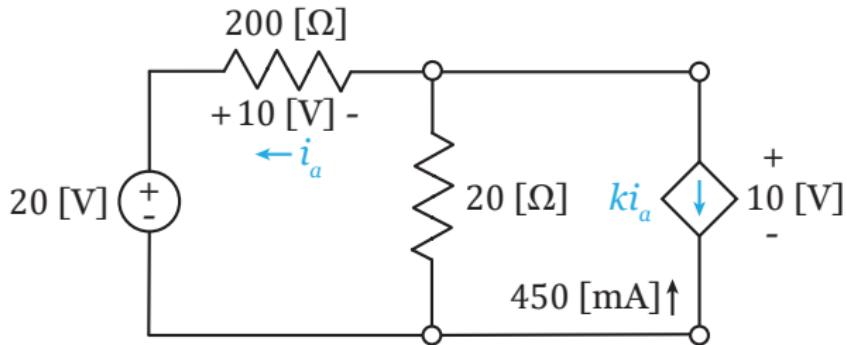

Learning Objectives

2.6 Meters


2.7 Dependent Sources

Summary



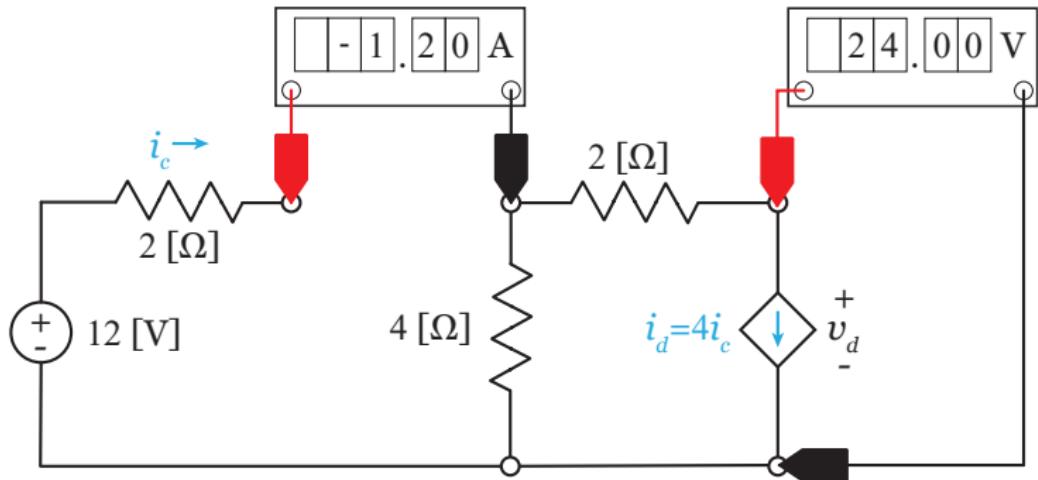Example #3

- Determine the power absorbed by the CCCS:



Learning Objectives


2.6 Meters

2.7 Dependent Sources

Summary



Example #3

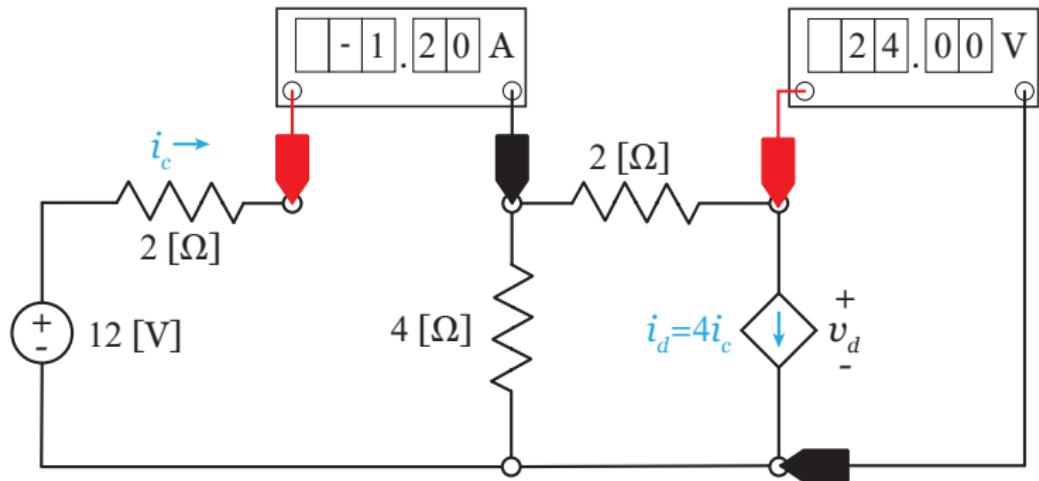

Learning Objectives

2.6 Meters


2.7 Dependent Sources

Summary



Example #4

- ▶ Determine the gain of the CCVS:

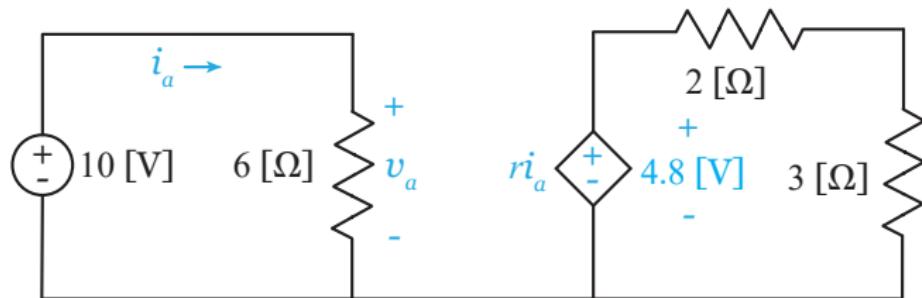

Learning Objectives

2.6 Meters

2.7 Dependent Sources

Summary



Student Learning Objectives

Chapter 2 - Circuit Elements

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Understand the underlying assumptions made when using voltmeters and ammeters
 - ▶ A voltmeter is assumed to have infinite resistance, such that current does not flow through it. The terminals of a voltmeter are placed across an element, measuring the voltage drop - open circuit.
 - ▶ An ammeter is assumed to have zero resistance, such that it does not effect the current running through the element. An ammeter is placed in-line with the circuit element, such that it measures the current through the element - short circuit.

[Learning Objectives](#)

[2.6 Meters](#)

[2.7 Dependent Sources](#)

[Summary](#)



Student Learning Objectives

Chapter 2 - Circuit Elements

MEMS 0031

- ▶ Identify dependent sources and understand the four types (CCVS, VCVS, VCCS, CCCS) and their associated gains
 - ▶ CCVS - current controlled voltage source - the voltage output is proportional to a designated current within the circuit. Gain has units of $[\Omega]$.
 - ▶ VCVS - voltage controlled voltage source - the voltage output is proportional to a designated voltage potential within the circuit. Gain is dimensionless.

[Learning Objectives](#)

[2.6 Meters](#)

[2.7 Dependent Sources](#)

[Summary](#)



Student Learning Objectives

Chapter 2 - Circuit Elements

MEMS 0031

- ▶ Identify dependent sources and understand the four types (CCVS, VCVS, VCCS, CCCS) and their associated gains
 - ▶ VCCS - voltage controlled current source - the current output is proportional to a designated voltage potential within the circuit. Gain has units of $[\Omega^{-1}]$.
 - ▶ CCCS - current controlled current source - the current output is proportional to a designated current within the circuit. Gain is dimensionless.

Learning Objectives

2.6 Meters

2.7 Dependent Sources

Summary



Suggested Problems

Chapter 2 - Circuit
Elements

MEMS 0031

- ▶ 2.6-1, 2.6-2, 2.6-3, 2.6-4, 2.7-1, 2.7-2, 2.7-3, 2.7-5

Learning Objectives

2.6 Meters

2.7 Dependent
Sources

Summary

