

Chapter 3 - Resistive Circuits

Lecture 5

Section 3.2

Learning Objectives

3.2 Kirchoff's Laws

Summary

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 3 -
Resistive Circuits

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Draw a circuit network and understand the principle of equivalent
- ▶ Understand and apply Kirchoff's Current Law (KCL)
- ▶ Understand and apply Kirchoff's Voltage Law (KVL)


[Learning Objectives](#)

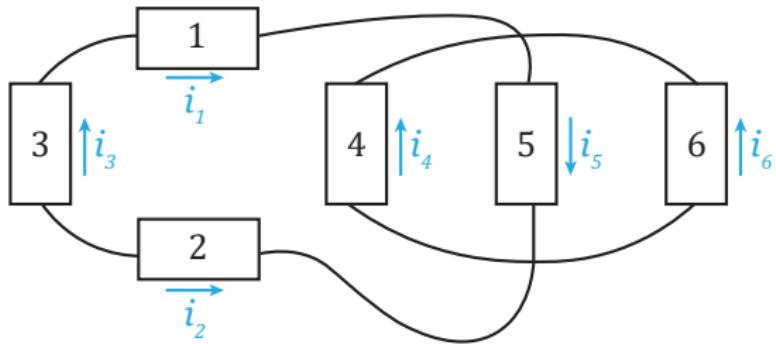[3.2 Kirchoff's Laws](#)

[Summary](#)



- There are a variety of ways to draw circuits:




Learning Objectives

3.2 Kirchoff's Laws

Summary



- ▶ Then there is the correct way:

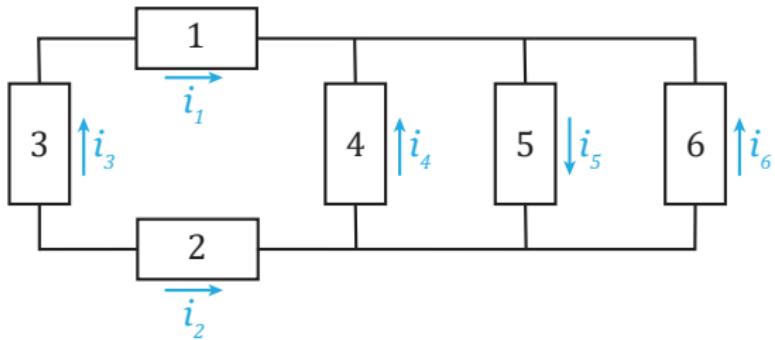

Learning Objectives

3.2 Kirchoff's Laws

Summary



Equivalence

- ▶ For two electrical circuits to be equivalent, the following have to be satisfied:
 1. Same number of nodes
 2. Same number of elements
 3. Same nodes connect same elements

Learning Objectives


3.2 Kirchoff's Laws

Summary



Equivalence

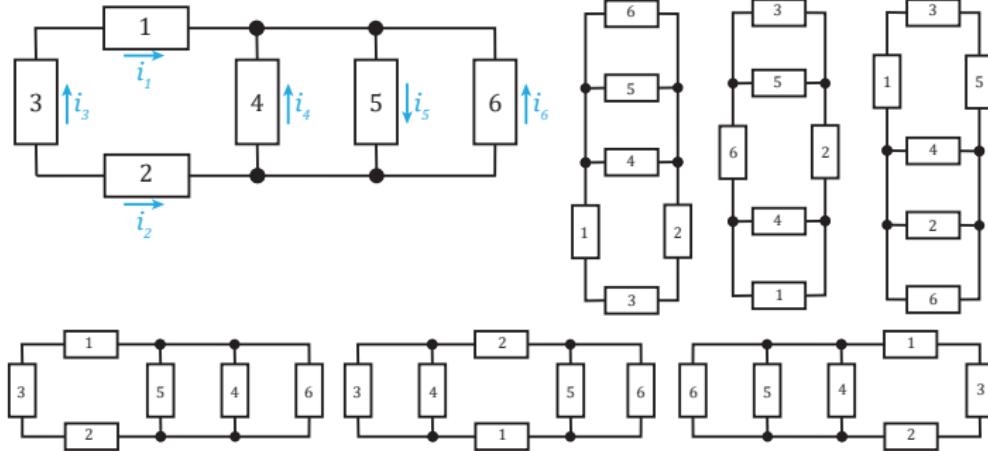- Which of the following circuits are equivalent?



Learning Objectives

3.2 Kirchoff's Laws

Summary



- ▶ **Kirchoff's Current Law (KCL)** states the sum of all currents flowing into or out of a node must equal zero:

$$\sum i_{\text{in}} = \sum i_{\text{out}}$$

- ▶ **Kirchoff's Voltage Law (KVL)** states the sum of all voltages around a loop equals zero:

$$\sum V_{\text{drop}} = \sum V_{\text{rise}}$$

Learning Objectives

3.2 Kirchoff's Laws

Summary




Example #1

- ▶ Find the power supplied by element C and the power received by element D

Learning Objectives


3.2 Kirchoff's Laws

Summary

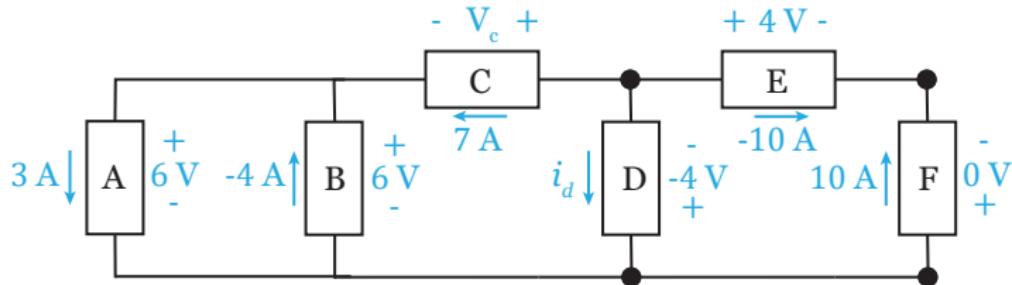

Example #1

► Solution:

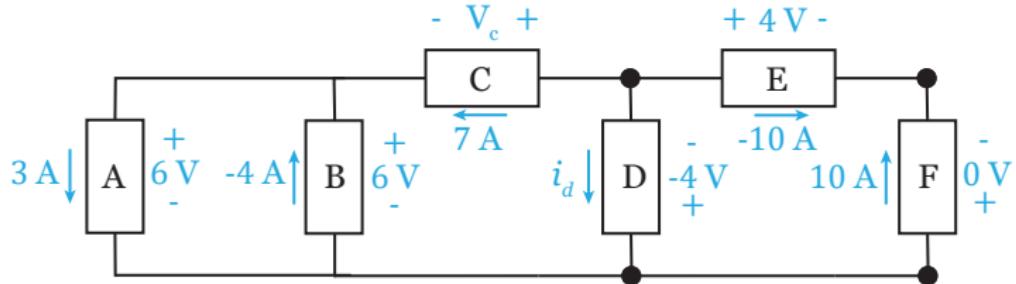

Learning Objectives


3.2 Kirchoff's Laws

Summary



Example #1

► Solution:

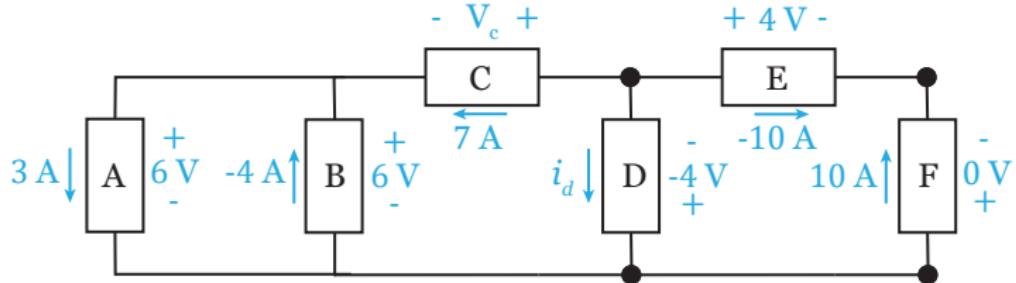

Learning Objectives

3.2 Kirchoff's Laws

Summary




Learning Objectives

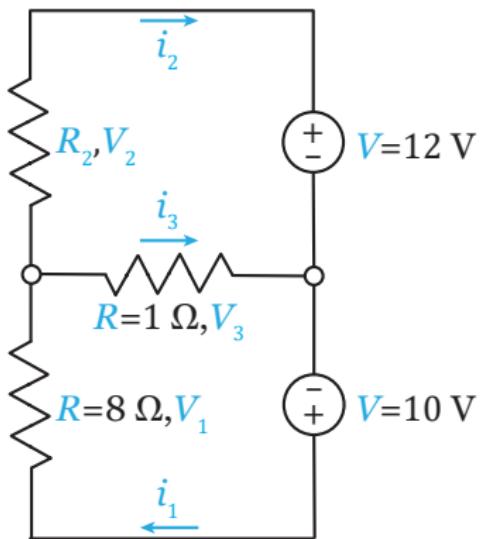3.2 Kirchoff's Laws


Summary

- Find the currents through each resistor as well as the value of R_2 given $i_3=2$ [A]



Example #2

► Solution:

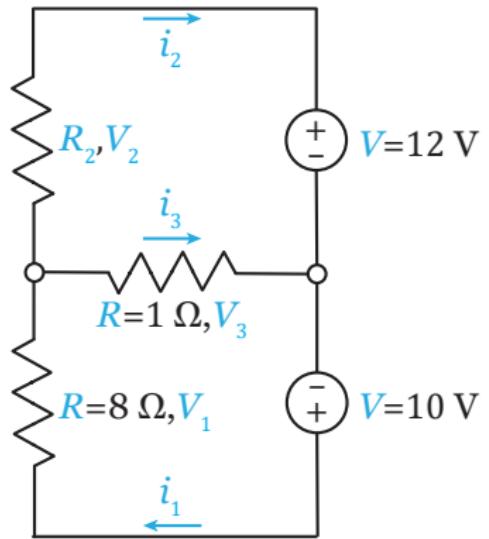

Learning Objectives


3.2 Kirchoff's Laws

Summary



Example #2

► Solution:

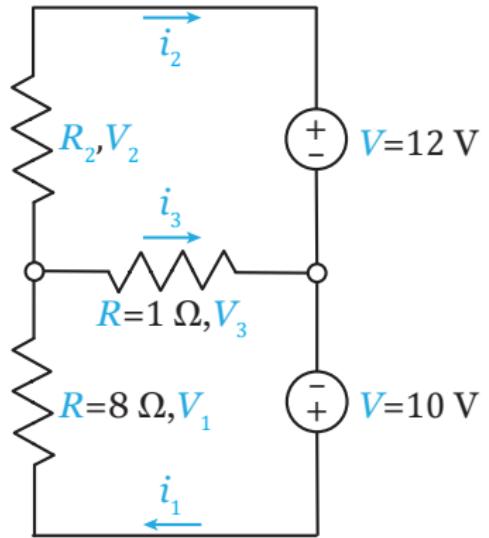

Learning Objectives


3.2 Kirchoff's Laws

Summary



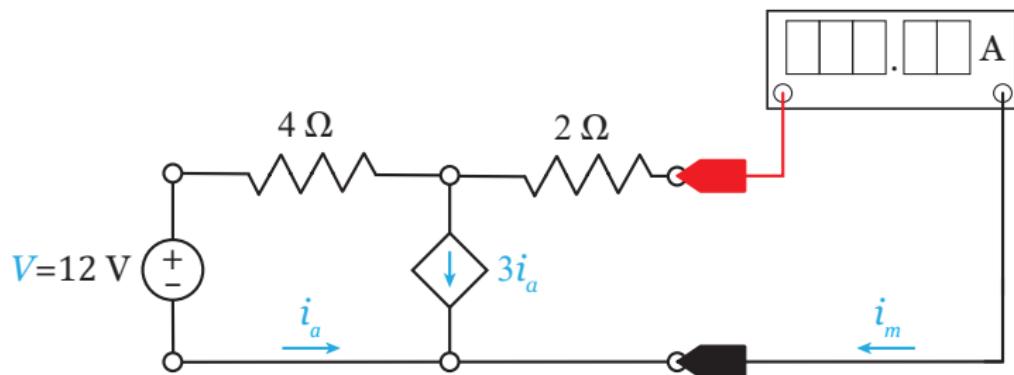Example #3

- ▶ What is the current measured by the ammeter?



Learning Objectives


3.2 Kirchoff's Laws

Summary



Example #3

► Solution:

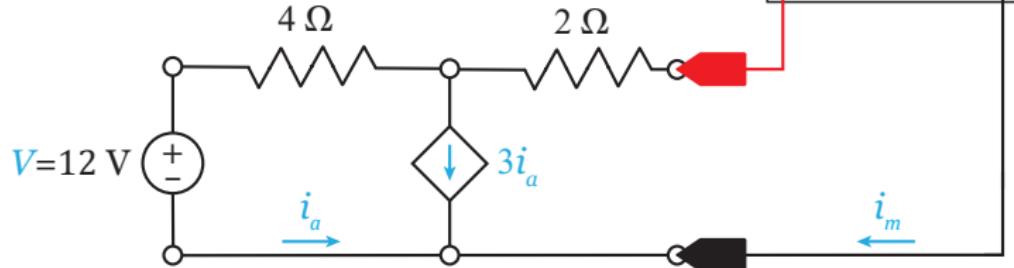

Learning Objectives


3.2 Kirchoff's Laws

Summary



Example #3

► Solution:

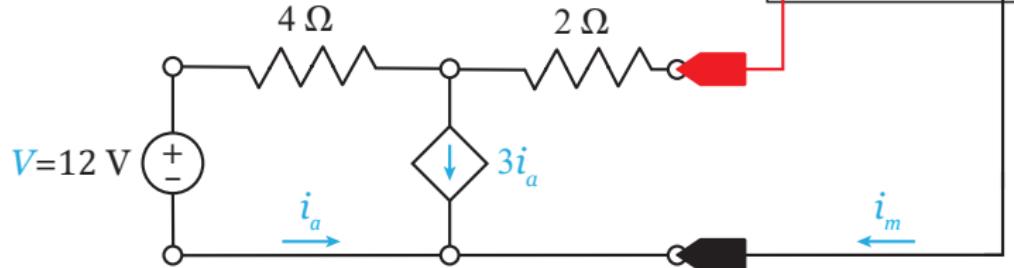

Learning Objectives

3.2 Kirchoff's Laws

Summary



Student Learning Objectives

At the end of the lecture, students should be able to:

- ▶ Draw a circuit network and understand the principle of equivalent
 - ▶ The principle of equivalence states that two circuits are equivalent if they have the same number of nodes and elements, and the same nodes connect the same elements.
- ▶ Understand and apply Kirchoff's Current Law (KCL)
 - ▶ KCL states the sum of currents entering a node must be the sum of currents exiting a node. This is equivalent to the continuity equation in Fluid Mechanics.

[Learning Objectives](#)

[3.2 Kirchoff's Laws](#)

[Summary](#)



Student Learning Objectives

Chapter 3 -
Resistive Circuits

MEMS 0031

- ▶ Understand and apply Kirchoff's Voltage Law (KVL)
 - ▶ KVL states the sum of voltage potentials around a loop must equal zero. That is, the potential provided by a source must be dissipated by a sink - there can be no net potential.

Learning Objectives

3.2 Kirchoff's Laws

Summary



Suggested Problems

Chapter 3 -
Resistive Circuits

MEMS 0031

- ▶ 3.2-1, 3.2-2, 3.2-3, 3.2-5, 3.2-6, 3.2-7, 3.2-12, 3.2-21

Learning Objectives

3.2 Kirchoff's Laws

Summary

