

# Chapter 8 - The Complete Response of RL and RC Circuits

## Lecture 28

### Sections 8.6 & 8.7

## MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department  
University of Pittsburgh



# Student Learning Objectives

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Solve for the response of  $RL$  and  $RC$  circuits with step-function sources

Learning Objectives

8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary



- ▶ Consider the voltage output of the system taking the form

$$v(t) = \begin{cases} 1 & t \leq t_0 \\ 1 & t > t_0 \end{cases}$$

- ▶ We will call  $v(t)=u(t-t_0)$ , i.e. the unit step forcing function
- ▶ This allows us to define the voltage as


$$v(t) = V_0 u(t - t_0)$$

- ▶  $V_0$  is the voltage at  $t_0$



# Step Source $RL$

- ▶ Consider the  $RL$  circuit

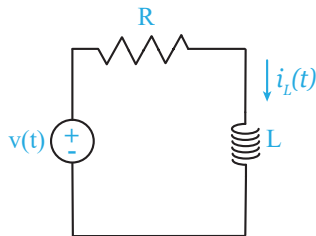

- ▶ Applying KVL

$$v = iR + L \frac{di}{dt}$$

- ▶ Separating terms

$$\frac{di}{dt} = \frac{-iR + v}{L}$$

- ▶ Grouping  $i$  and  $t$

$$\frac{di}{i - (v/R)} = \frac{-R}{L} dt$$


- ▶ Integrating

$$\frac{i(t) - (v/R)}{i_0 - (v/R)} = e^{-\frac{t}{\tau}} \implies i(t) = \frac{v}{R} + \left(i_0 - \frac{v}{R}\right) e^{-\frac{t}{\tau}}$$



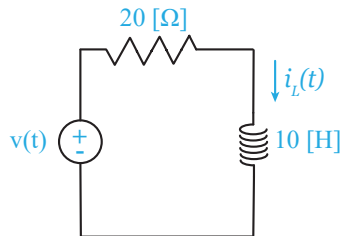
# Example #1

- If  $v(t)=4-8u(t)$  [V], determine the current through the inductor as a function of time



# Example #1

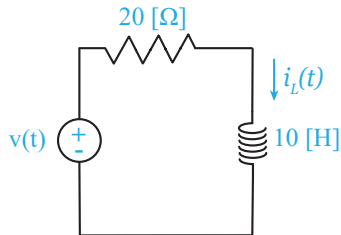

## Learning Objectives


8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary



# Example #1

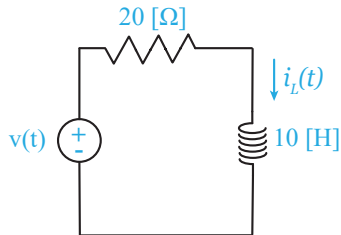

## Learning Objectives

8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary



# Step Source $RC$


## Learning Objectives

8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary

- ▶ Consider the  $RC$  circuit

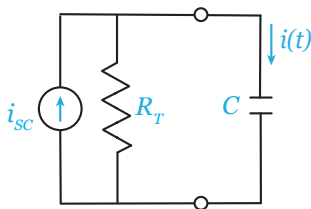

- ▶ Applying KCL

$$i_{sc} = \frac{v}{R} + C \frac{dv}{dt}$$

- ▶ Dividing by  $C$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{i_{sc}}{C}$$

- ▶ This solution is of the same form as we saw with the  $RL$  circuit, thus

$$v(t) = i_{sc}R + (v_0 - i_{sc}R)e^{-\frac{t}{\tau}}$$


- ▶ Thus, we have the same solution methodology for  $RC$  circuits as  $RL$





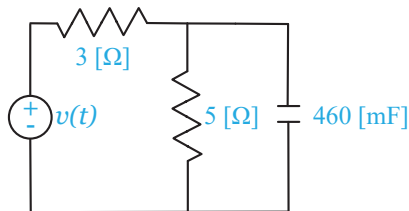
## Example #2

- If  $v(t)=7-14u(t)$  [V], determine the voltage across the capacitor as a function of time



## Example #2

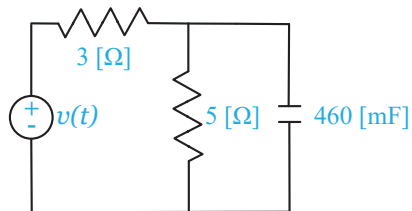

- ▶ The reader is referred to page 335 of the text; we shall not cover this.

Learning Objectives

8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary



# Student Learning Objectives

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

At the end of the lecture, students should be able to:

- ▶ Solve for the response of  $RL$  and  $RC$  circuits with step-function sources
  - ▶ The unit step-function allows us to solve for the current in an  $RL$  circuit and voltages in a  $RC$  circuit, which differed from our conventional representation. This method is comparable to sequential switching with constant sources.

Learning Objectives

8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary



# Suggested Problems

Chapter 8 - The  
Complete Response  
of RL and RC  
Circuits

MEMS 0031

► 8.6-1, 8.6-2, 8.6-5, 8.6-6, 8.6-9, 8.7-1, 8.7-3, 8.7-5

Learning Objectives

8.6 - The Unit Step  
Source

8.7 - Non-Constant  
Sources

Summary

