

MEMS 0031 - Electrical Circuits
Quiz #2

Name: _____

Problem #1

Determine the resistance R that results in a current greater than 80 [mA] to be drawn, ensuring the power dissipated by the resistor is less than 2 [W], given $V_s=10$ [V].

