

MEMS 0031 - Electrical Circuits

Quiz #1

May 15<sup>th</sup>, 2019

90 points

Name: \_\_\_\_\_

**Problem #1**

(5 pts.) Given that current is the time-rate-of-change of charge, and that  $i(t)=5\cdot\sin(3t)$  [A], determine the charge  $q(t)$  for  $t \geq 0$ :

**Problem #2**


(5 pts.) Given  $q(t)=e^{-10t}$ , determine the current  $i(t)$  for  $t \geq 0$ :

**Problem #3**

(5 pts.) Given  $i(t)=3t^3$  and  $v(t)=3t^{-2}$ , determine  $P(t)$  for  $t \geq 0$ :

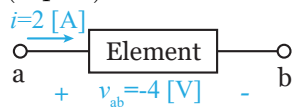
**Problem #4**

(5 pts.) Given the schematic below, determine the power **supplied**:


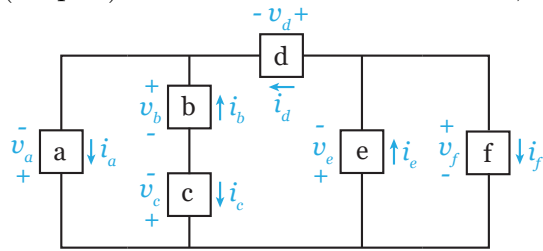
## Problem #5


(40 pts.) Given the schematic below, does the circuit satisfy the Conservation of Power?



Element	Voltage [kV]	Current [mA]
a	-3	-250
b	4	-400
c	1	400
d	1	150
e	-4	200
f	4	50
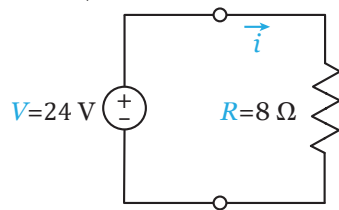
## Problem #6

(15 pts.) Give the schematic below, determine a) the current flowing through the resistor and b) the power dissipated by the resistor.



## Problem #7

(15 pts.) Give the schematic below, determine a) the resistance of the resistor and b) the power dissipated by the resistor.

