

MEMS 0031 - Electrical Circuits

Quiz #1

May 15th, 2019

90 points

Name: Solutions

Problem #1

(5 pts.) Given that current is the time-rate-of-change of charge, and that $i(t)=5\cdot\sin(3t)$ [A], determine the charge $q(t)$ for $t \geq 0$:

$$i = \frac{dq}{dt} \implies dq = i dt \implies q = \int_0^t i dt = \frac{5}{3} \left(1 - \cos(3t) \right)$$

Problem #2

(5 pts.) Given $q(t)=e^{-10t}$, determine the current $i(t)$ for $t \geq 0$:

$$i = \frac{dq}{dt} = \frac{d}{dt}(e^{-10t}) = -10e^{-10t}$$


Problem #3

(5 pts.) Given $i(t)=3t^3$ and $V(t)=3t^{-2}$, determine $P(t)$ for $t \geq 0$:

$$P(t) = V(t)i(t) = (3t^3)(3t^{-2}) = 9t$$

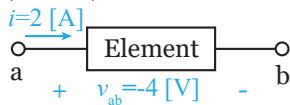Problem #4

(5 pts.) Given the schematic below, determined the power **supplied**:




The circuit depicted adheres to the PSC, however, the voltage potential across terminals a and b is negative. Switching the polarity of the voltage potential, the circuit then adheres to the ASC

$$P = Vi = (4 \text{ [V]})(2 \text{ [A]}) = 8 \text{ [W]}$$

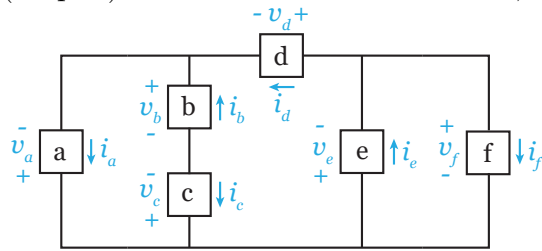Problem #5

(40 pts.) Given the schematic below, does the circuit satisfy the Conservation of Power?




Element	Voltage [kV]	Current [mA]	Active or Passive?	Power Dissipated [W]
a	-3	-250	Active	-750
b	4	-400	Passive	1,600
c	1	400	Active	-400
d	1	150	Passive	150
e	-4	200	Active	-800
f	4	50	Passive	200
			Sum:	0

Yes, this circuit conserves power.

Problem #6

(15 pts.) Give the schematic below, determine a) the current flowing through the resistor and b) the power dissipated by the resistor.

The current is calculated via Ohm's law:

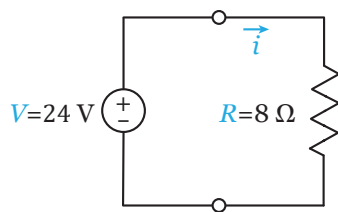

$$i = \frac{V}{R} = \frac{24 [\text{V}]}{8 [\Omega]} = 3 [\text{A}]$$


The power dissipated is current-squared times resistance:

$$P_{diss} = i^2 R = (3 [\text{A}])^2 (8 [\Omega]) = 72 [\text{W}]$$

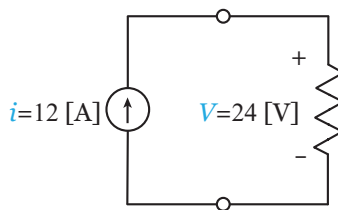Problem #7

(15 pts.) Give the schematic below, determine a) the resistance of the resistor and b) the power dissipated by the resistor.

The resistance is calculated via Ohm's law:



$$R = \frac{V}{i} = \frac{24 [\text{V}]}{12 [\text{A}]} = 2 [\Omega]$$

The power dissipated is current-squared times resistance:

$$P_{diss} = i^2 R = (12 [\text{A}])^2 (2 [\Omega]) = 288 [\text{W}]$$