

MEMS 0031 - Electrical Circuits

Quiz #5


June 2th, 2019

90 points

Name: _____

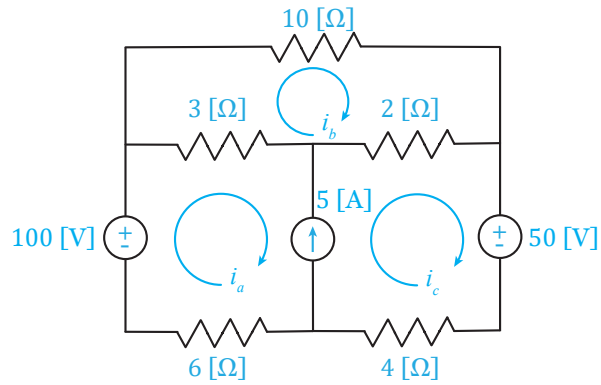Problem #1

(30 pts) Determine mesh currents i_a , i_b and i_c using MCA.



Problem #2

Using Mesh Current Analysis (MCA), determine the mesh currents i_1 through i_5 , given $R = 3\ [\Omega]$.

