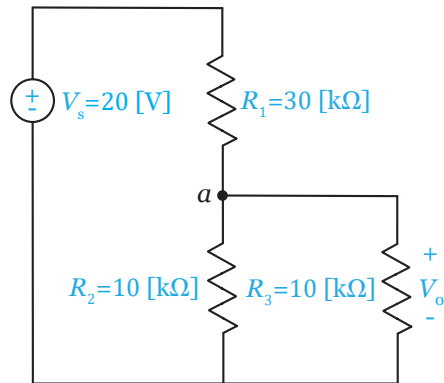


MEMS 0031 - Electrical Circuits  
Quiz #3

Name: \_\_\_\_\_

**Problem #1**

Given the potentiometer shown below, determine the output voltage  $V_o$ .



Solution:

There are two 10 [kΩ] resistors in parallel, which creates an equivalent of

$$R_{eq,1} = \frac{(10 \text{ [k}\Omega]) \cdot (10 \text{ [k}\Omega])}{(10 \text{ [k}\Omega]) + (10 \text{ [k}\Omega])} = 5 \text{ [k}\Omega]$$

Those two 10 [kΩ] resistors have the same voltage potential, therefore  $V_o$  is simply voltage division of the the 30 [kΩ] and  $R_{eq,1}$  resistors

$$V_o = \frac{5 \text{ [k}\Omega]}{30 \text{ [k}\Omega] + 5 \text{ [k}\Omega]} 20 \text{ [V]} = 2.86 \text{ [V]}$$