


Series and Parallel Resistors and Sources

MEMS 0031 - Electrical Circuits

June 4, 2020

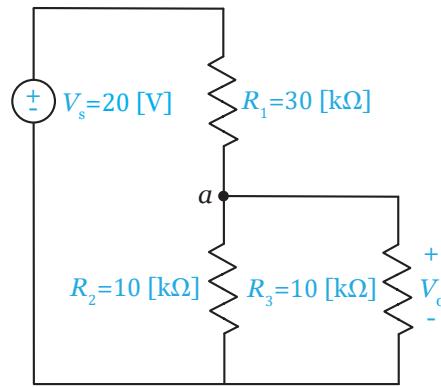Problem #1 - Lectures 6 & 7

Given the potentiometer shown below, determine the output voltage V_o .



There are two $10 \text{ [k}\Omega\text{]}$ resistors in parallel, which creates an equivalent of


$$R_{eq,1} = \frac{(10 \text{ [k}\Omega\text{]})(10 \text{ [k}\Omega\text{]})}{(10 \text{ [k}\Omega\text{]}) + (10 \text{ [k}\Omega\text{]})} = 5 \text{ [k}\Omega\text{]}$$

Those two $10 \text{ [k}\Omega\text{]}$ resistors have the same voltage potential, therefore V_o is simply voltage division of the the $30 \text{ [k}\Omega\text{]}$ and $R_{eq,1}$ resistors

$$V_o = \left(\frac{5 \text{ [k}\Omega\text{]}}{30 \text{ [k}\Omega\text{]} + 5 \text{ [k}\Omega\text{]}} \right) (20 \text{ [V]}) = 2.86 \text{ [V]}$$

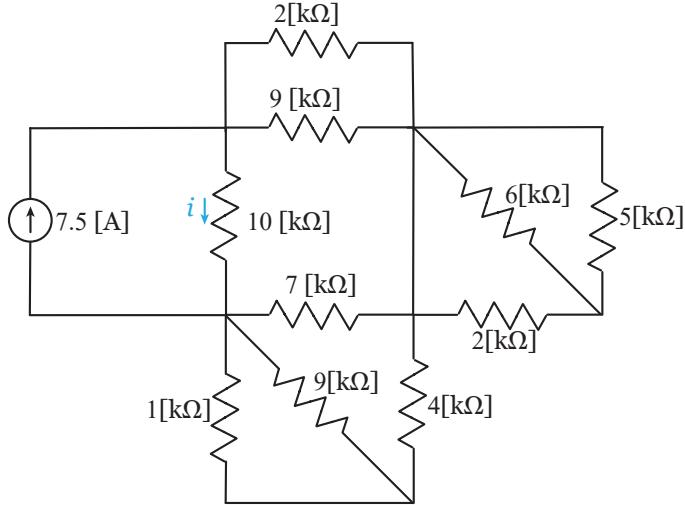Problem #2 - Lectures 6 & 7

Find the voltage drop across the $10 \text{ [k}\Omega\text{]}$ resistor.





Let us start by color-coding the nodes. Our first step (Step 1) will be calculating the parallel resistance of the $2 \text{ [k}\Omega\text{]}$ and $9 \text{ [k}\Omega\text{]}$ resistors:

$$R_{eq} = \frac{(2 \text{ [k}\Omega\text{]})(9 \text{ [k}\Omega\text{]})}{(2 + 9) \text{ [k}\Omega\text{]}} = 1.63 \text{ [k}\Omega\text{]}$$

Our second step (Step 2) will be calculating the parallel resistance of the $1 \text{ [k}\Omega\text{]}$ and $9 \text{ [k}\Omega\text{]}$ resistors:

$$R_{eq} = \frac{(1 \text{ [k}\Omega\text{]})(9 \text{ [k}\Omega\text{]})}{(1 + 9) \text{ [k}\Omega\text{]}} = 0.9 \text{ [k}\Omega\text{]}$$

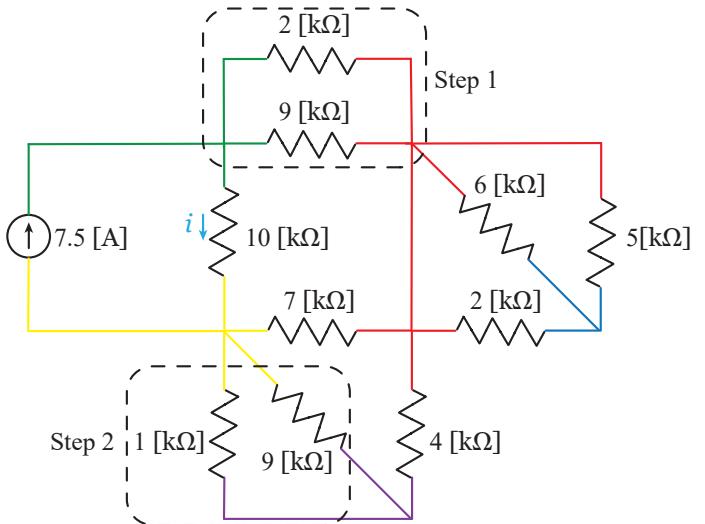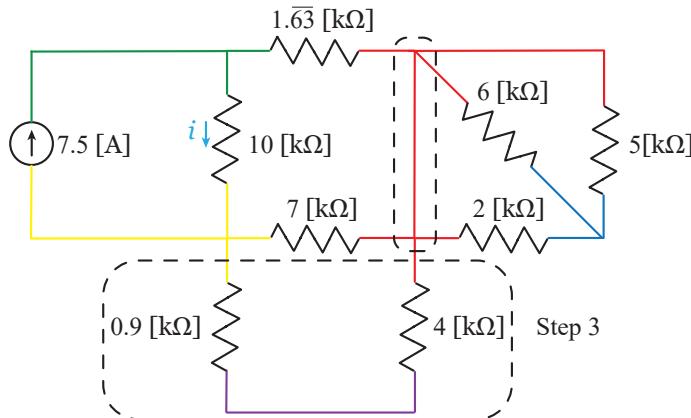Let us redraw the circuit to better see what is in parallel and what is in series.




We note that the short, as highlighted, means all current will bypass the 2 , 6 and $5 \text{ [k}\Omega\text{]}$ resistors. Although the 2 , 6 and $5 \text{ [k}\Omega\text{]}$ resistors are in parallel, their equivalent resistance is of no consequence.

Next we can proceed to Step 3, where the 0.9 and $4 \text{ [k}\Omega\text{]}$ resistors are in series, giving an equivalent of $4.9 \text{ [k}\Omega\text{]}$. This equivalent is in parallel with the $7 \text{ [k}\Omega\text{]}$ resistor:

$$R_{eq} = \frac{(4.9 \text{ [k}\Omega\text{]})(7 \text{ [k}\Omega\text{]})}{(4.9 + 7) \text{ [k}\Omega\text{]}} \approx 2.882 \text{ [k}\Omega\text{]}$$


We see the $2.88 \text{ [k}\Omega\text{]}$ and $1.63 \text{ [k}\Omega\text{]}$ resistors are in series, resulting in an equivalent of approximately $4.512 \text{ [k}\Omega\text{]}$. Thus, the $10 \text{ [k}\Omega\text{]}$ and $4.512 \text{ [k}\Omega\text{]}$ resistors are in parallel, and the current through the $10 \text{ [k}\Omega\text{]}$ resistor is found via current division:
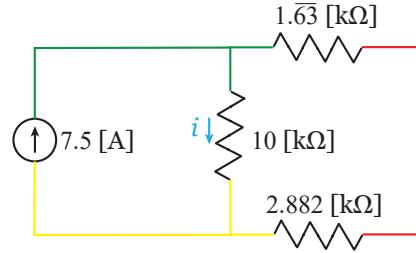
$$i = \left(\frac{4.512 \text{ [k}\Omega\text{]}}{14.512 \text{ [k}\Omega\text{]}} \right) (7.5 \text{ [A]}) = 2.33 \text{ [A]}$$



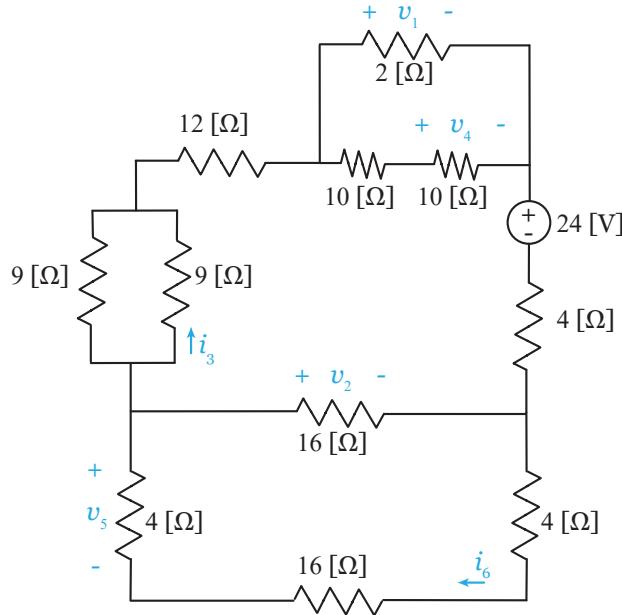Problem #3 - Lectures 6 & 7

Determine the values of v_1 , v_2 , i_3 , v_4 , v_5 , and i_6 in the circuit shown below.



Let us start by color-coding the nodes. Then, we will begin to simply all the parallel and series resistors such that we can determine our source current from the 24 [V] source. We see in Step 1 the two 10 [Ω] resistors are in series, and their equivalent is in parallel with the 2 [Ω] resistor:



$$R_{eq} = \frac{(2 [\Omega])(20 [\Omega])}{(2 + 20) [\Omega]} = 1.81 [\Omega]$$

In Step 2, the two 9 [Ω] resistors are in parallel:

$$R_{eq} = \frac{(9 [\Omega])(9 [\Omega])}{(9 + 9) [\Omega]} = 4.5 [\Omega]$$

In Step 3, the 4, 16 and 4 [Ω] resistors are in series, having an equivalent of 24 [Ω]. This equivalence is in parallel with the 16 [Ω] resistor:
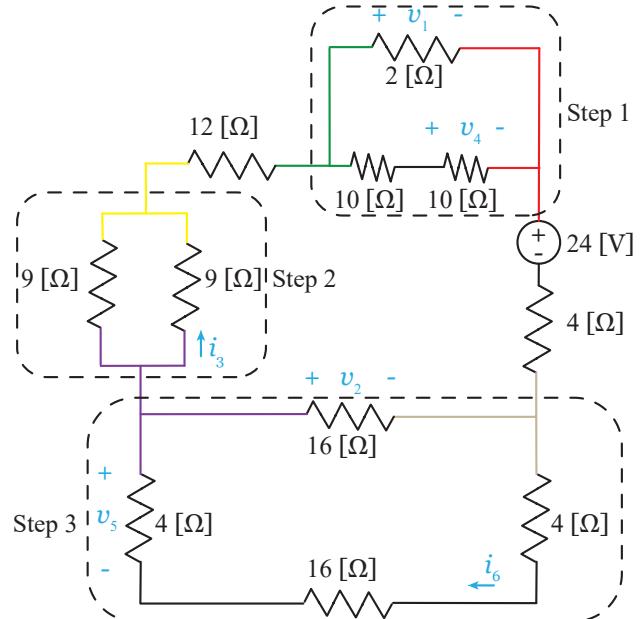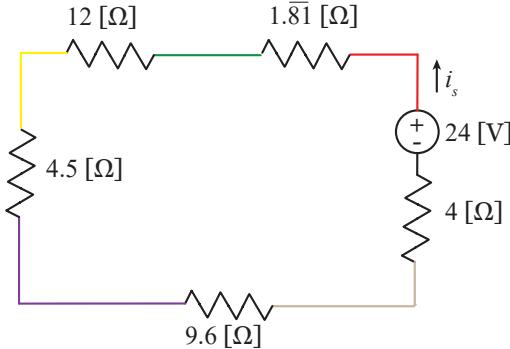
$$R_{eq} = \frac{(16 [\Omega])(24 [\Omega])}{(16 + 24) [\Omega]} = 9.6 [\Omega]$$



With the reduced circuit, we can calculate the source current:

$$i = \frac{24 [V]}{31.91 [\Omega]} = 0.752 [A]$$

Now, we will look at the original circuit and use the concepts of voltage and current division to find the properties of interest.

To determine v_1 , we recognize there is current division between the 2 and the two 10 [Ω] resistors:

$$i_{2[\Omega]} = \left(\frac{20[\Omega]}{22[\Omega]} \right) (0.752[A]) \approx 0.684[A]$$

Thus, the voltage drop across the 2 [Ω] resistor is:


$$v_1 = -(0.684[A])(2[\Omega]) = -1.368[V]$$

The current running through the two 10 [Ω] resistors in series is:

$$i_{20[\Omega]} = \left(\frac{2[\Omega]}{22[\Omega]} \right) (0.752[A]) \approx 0.0684[A]$$

Thus, the voltage drop across the 10 [Ω] resistor is:
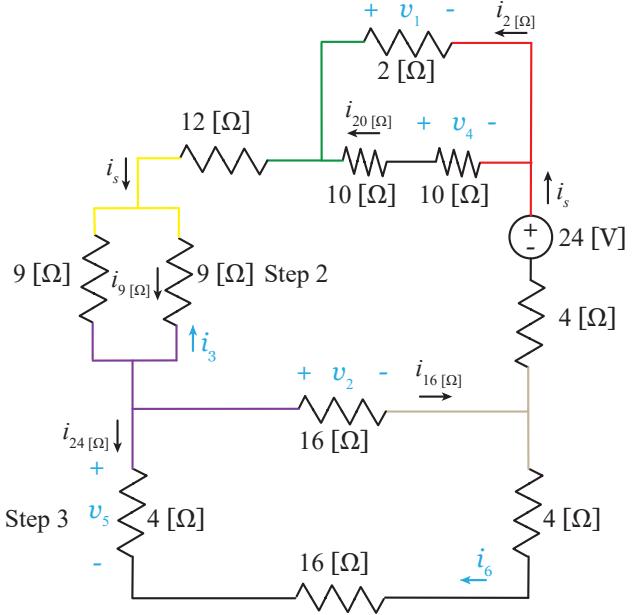
$$v_4 = -(0.0684[A])(10[\Omega]) = -0.684[V]$$



The current running through the 9 [Ω] resistor is found via current division:

$$i_9[\Omega] = \left(\frac{9[\Omega]}{18[\Omega]} \right) (0.752[A]) \approx 0.376[A]$$

The current i_3 is opposing the current running through the 9 [Ω] resistor:

$$i_3 = -0.376[A]$$

The current running through the 16 [Ω] resistor is solved for via current division:

$$i_{16}[\Omega] = \left(\frac{24[\Omega]}{40[\Omega]} \right) (0.752[A]) \approx 0.4512[A]$$

Thus, the voltage drop across the 16 [Ω] resistor is:

$$v_2 = (0.4512[A])(16[\Omega]) = 7.219[V]$$

The current running through the 4, 16 and 4 [Ω] resistors in series is solved for via current division:

$$i_{16}[\Omega] = \left(\frac{16[\Omega]}{40[\Omega]} \right) (0.752[A]) \approx 0.301[A]$$

The current i_6 is opposing the current running through the 4, 16, and 4 [Ω] series resistors:

$$i_6 = -0.301[A]$$

Thus, the voltage drop across the 4 [Ω] resistor is:

$$v_5 = (0.301[A])(4[\Omega]) = 1.204[V]$$