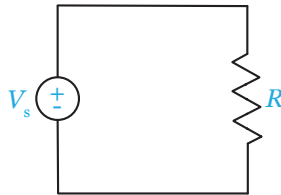


MEMS 0031 - Electrical Circuits
Quiz #2

Name: Solutions

Problem #1

Determine the resistance R that results in a current greater than 80 [mA] to be drawn, ensuring the power dissipated by the resistor is less than 2 [W], given $V_s=10$ [V].



The current must be greater than 80 [mA]. Applying Ohm's law to solve for the resistance:

$$V = iR \implies i = \frac{10 \text{ [V]}}{R} > 80 \text{ [mA]} \implies R < \frac{10 \text{ [V]}}{80 \text{ [mA]}} \implies R < 125 \text{ [\Omega]}$$

The power dissipated must be less than 2 [W]. Using our power equation:

$$P = i^2 R < 2 \text{ [W]} \implies R < \frac{w \text{ [W]}}{(80 \text{ [mA]})^2} \implies R < 312.5 \text{ [\Omega]}$$

Well, this doesn't tell us much because R must be less than 125 as dictated by Ohm's law. Using the expression for power based upon voltage:

$$P = \frac{V^2}{R} < 2 \text{ [W]} \implies R > \frac{(10 \text{ [V]})^2}{2 \text{ [W]}} \implies R > 50 \text{ [\Omega]}$$

Therefore

$$50 < R \text{ [\Omega]} < 125$$