

Chapter 5 - Methods of Analysis of Resistive Circuits

Lecture 15
Sections 5.2-5.3

MEMS 0031

Learning Objectives

5.2 Source
Transformations

5.3 Superposition
with Independent
Sources

Summary

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 5 -
Methods of Analysis
of Resistive Circuits

At the end of the lecture, students should be able to:

- ▶ Able to transform voltage and current sources to current and voltage sources, respectively
- ▶ Apply the superposition principle to sources to analyze the behavior of circuits

MEMS 0031

Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources

Summary





Ideal vs. Nonideal Sources

Chapter 5 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

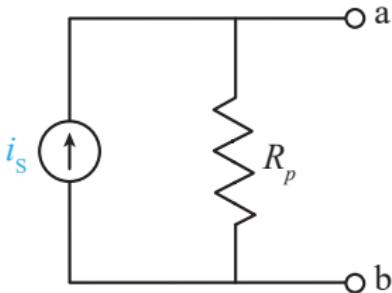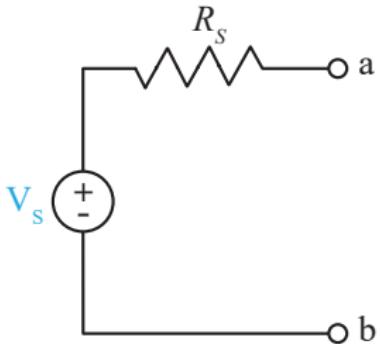- ▶ A real, independent source exhibits a decrease in voltage or current as power drawn is increased
- ▶ This behavior can be represented by placing a resistor, R_s , in series with a V_S , or a resistor, R_p , in parallel with a current source



Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources

Summary




Source Transformation

Chapter 5 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

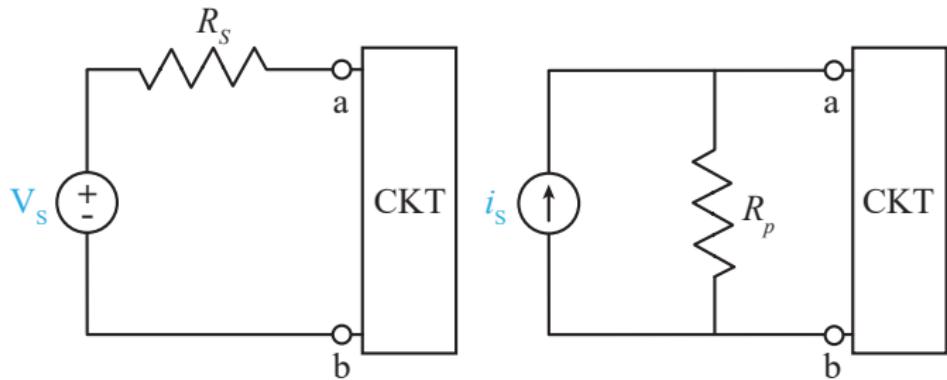- Under some circumstances, the non-ideal V_S and i_s are equivalent



- When a “source transformation” occurs from one to another, CKT behaves exactly the same

Learning Objectives

5.2 Source Transformations


5.3 Superposition with Independent Sources

Summary



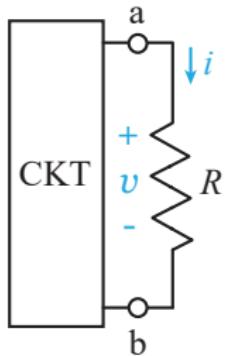Example #1

- ▶ Imagine you are analyzing the following circuit, with the following data. Can you construct an expression for the behavior?



R [kΩ]	0	1	2	5	10	20	50	∞
i [mA]	3	2.667	2.4	1.846	1.33	0.857	0.414	0
V [V]	0	2.667	4.8	9.231	13.33	17.143	20.69	24

Learning Objectives

5.2 Source Transformations


5.3 Superposition with Independent Sources

Summary



Thevenin Equivalent

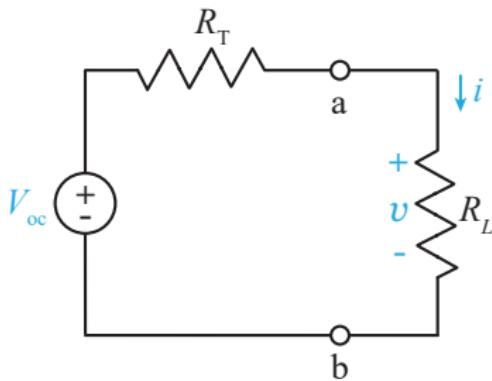- We can form an equivalent circuit with non-ideal $V_S = V_{oc}$ which is in series to R_T attached to a load R



Learning Objectives

5.2 Source Transformations


5.3 Superposition with Independent Sources

Summary



Norton Equivalent

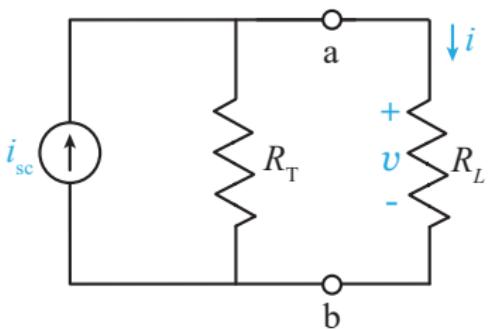- ▶ Alternatively, we could form an equivalent, non-ideal current source setting $i_s = i_{sc}$ in parallel with R_t attached to a load R



Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources


Summary



Source Equivalency

Chapter 5 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

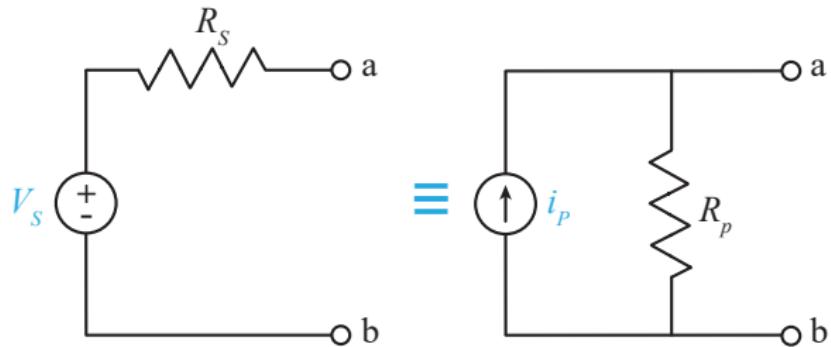


- ▶ When converting from i_P, R_p to V_S, R_S :

- ▶ When converting from V_S, R_S to i_P, R_p :



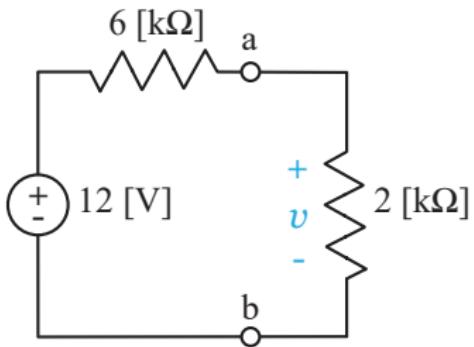Example #2

- Determine the Norton equivalent and determine the voltage drop across the $2 \text{ [k}\Omega\text{]}$ resistor.



Learning Objectives

5.2 Source Transformations


5.3 Superposition with Independent Sources

Summary



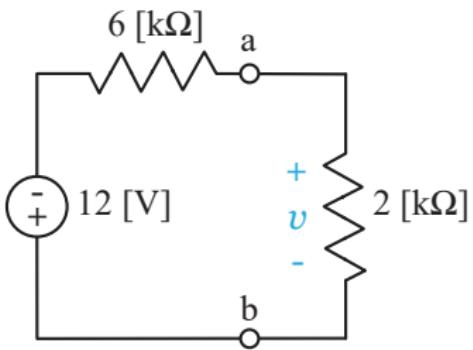Example #3

- ▶ How does the solution change if the polarity of the voltage source is switched?



Learning Objectives

5.2 Source Transformations



5.3 Superposition with Independent Sources

Summary



Example #4

- ▶ Solve for unknown parameters:

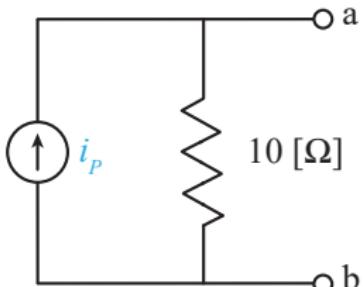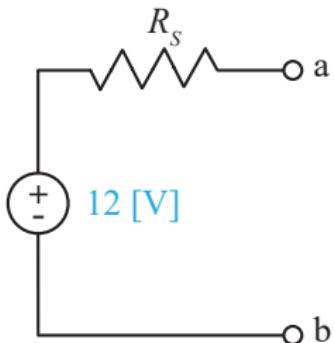

Learning Objectives

5.2 Source Transformations



5.3 Superposition with Independent Sources

Summary



Example #5

- ▶ Solve for unknown parameters:

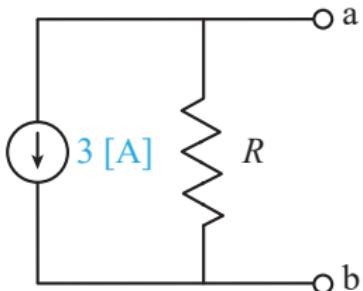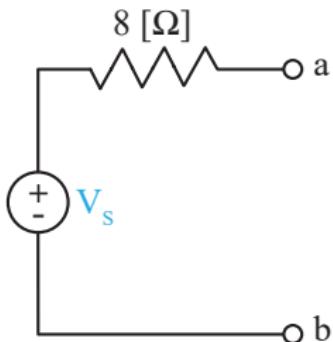

Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources

Summary



Superposition

- ▶ The total response is the sum of the responses of each independent source
- ▶ Short-circuit voltage sources
- ▶ Open-circuit current sources

Learning Objectives

5.2 Source Transformations


5.3 Superposition with Independent Sources

Summary



Example #6

► Find V_a

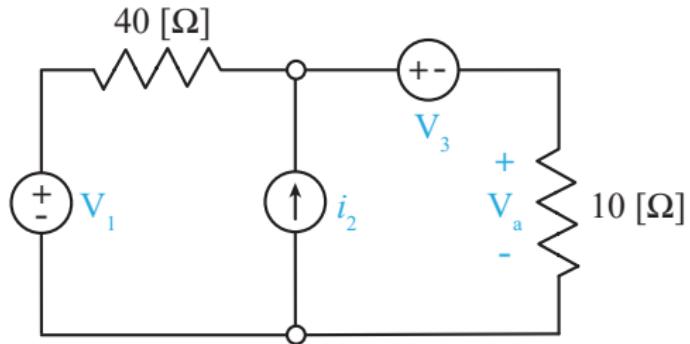

Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources

Summary




Example #6

Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources

Summary

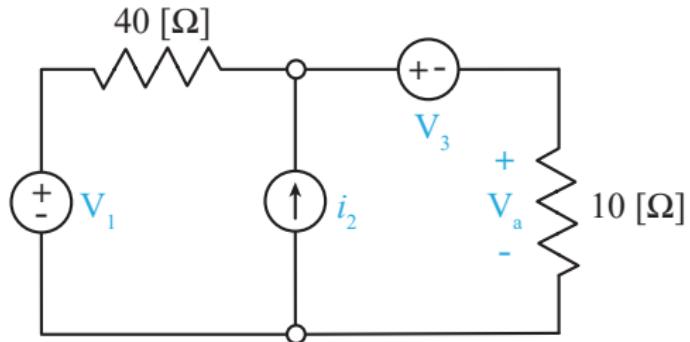

Student Learning Objectives

Chapter 5 -
Methods of Analysis
of Resistive Circuits

At the end of the lecture, students should be able to:

- ▶ Able to transform voltage and current sources to current and voltage sources, respectively
 - ▶ We use Ohm's law to convert between a voltage and current source, or a current and voltage source, using the constant of proportionality, i.e. R , which is kept invariant
- ▶ Apply the superposition principle to sources to analyze the behavior of circuits
 - ▶ When determining the behavior of a circuit using superposition, we consider one independent source at a time. To do such, we short the voltage sources and open the current sources.

MEMS 0031

Learning Objectives

5.2 Source Transformations

5.3 Superposition with Independent Sources

Summary



Suggested Problems

Chapter 5 -
Methods of Analysis
of Resistive Circuits

- ▶ 5.2-1, 5.2-2, 5.2-3, 5.2-4, 5.2-7, 5.3-1, 5.3-5, 5.3-7

MEMS 0031

Learning Objectives

5.2 Source
Transformations

5.3 Superposition
with Independent
Sources

Summary

