

MEMS 0031 - Electrical Circuits
Quiz #3

Name: _____

Problem #1

Given the potentiometer shown below, determine the output voltage V_o .

