

MEMS 0031 - Electrical Circuits
Quiz #5

Name: _____

Problem #1

Determine the mesh currents i_a , i_b and i_c using MCA.

