

Chapter 4 - Methods of Analysis of Resistive Circuits

Lecture 11 Section 4.4

MEMS 0031 Electrical Circuits

Mechanical Engineering and Materials Science Department
University of Pittsburgh



Student Learning Objectives

Chapter 4 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

Learning Objectives

4.4 Node Voltage
Analysis with
Independent
Voltage Sources

Summary

At the end of the lecture, students should be able to:

- ▶ Apply Node Voltage Analysis (NVA) to circuits with dependent sources



NVA with Independent VS

Chapter 4 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

Learning Objectives

4.4 Node Voltage
Analysis with
Independent
Voltage Sources

Summary


- ▶ By adding an dependent source, we must express behavior (voltage) in terms of node voltages.
- ▶ The number of KCL equations still holds as:

$$\# \text{ KCL Eqns.} = N - \# \text{ VS} - 1$$

- ▶ “Supernode” formulation is still valid




Example #1

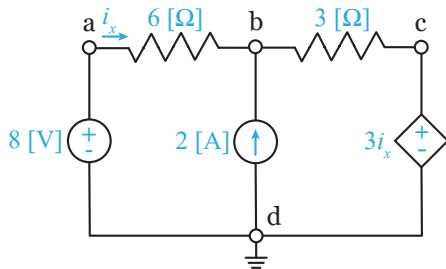

► Use NVA to determine the node voltages:



Example #1

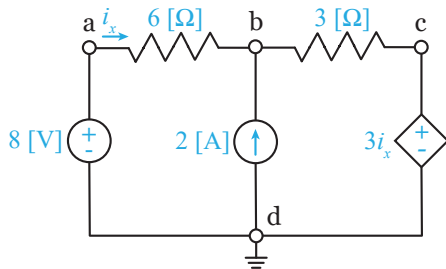

► Solution:


Learning Objectives

4.4 Node Voltage
Analysis with
Independent
Voltage Sources

Summary




Example #2

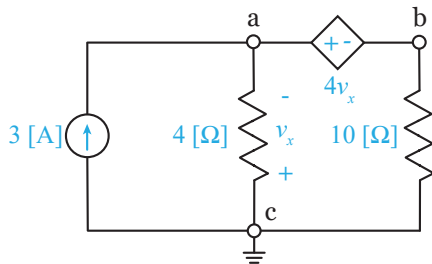

► Determine the voltage at a and b :




Example #2

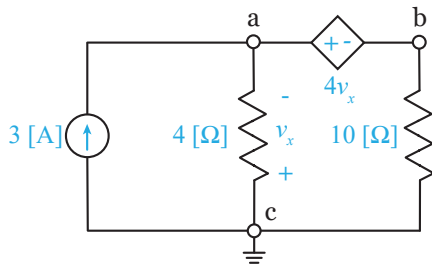

► Solution:




Example #3

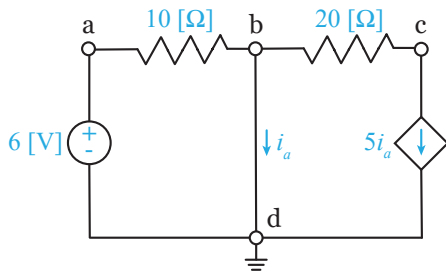

► Determine all unknowns:



Example #3

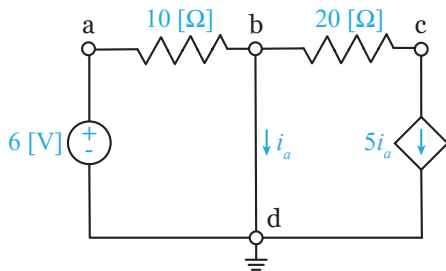

► Solution:



Student Learning Objectives

Chapter 4 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

Learning Objectives

4.4 Node Voltage
Analysis with
Independent
Voltage Sources

Summary

At the end of the lecture, students should be able to:

- ▶ Apply Node Voltage Analysis (NVA) to circuits with independent current sources
 - ▶ NVA requires the sole use of KCL. We construct $N - 1 - \#VS$ KCL equations, applied at non-zero and non-specified, and relate the currents to voltages using Ohm's law.
 - ▶ A voltage source (independent and dependent) between two non-zero nodes creates a supernode, i.e. an equation that relates two node voltages - apply KCL here!
 - ▶ A voltage source between a non-zero and zero-voltage nodes specifies the non-zero node voltage.



Suggested Problems

Chapter 4 -
Methods of Analysis
of Resistive Circuits

MEMS 0031

Learning Objectives

4.4 Node Voltage
Analysis with
Independent
Voltage Sources

Summary

At the end of the lecture, students should be able to:

- ▶ 4.4-1, 4.4-2, 4.4-3, 4.4-4, 4.4-5, 4.4-6, 4.4-7, 4.4-13, 4.4-14

