


Op-amp Worksheet

MEMS 0031 - Electrical Circuits

June 17th, 2020

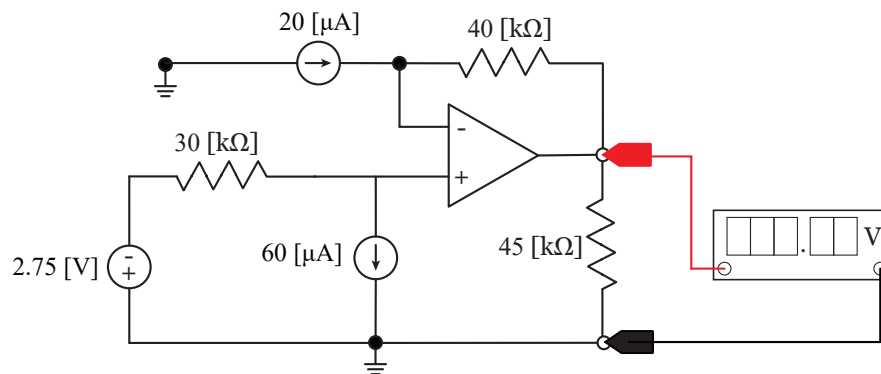Problem #1

Determine the reading of the voltmeter in the circuit shown below.



Problem #2

In the circuit shown below, determine the current i_o . Assume that the operational amplifiers are ideal.

